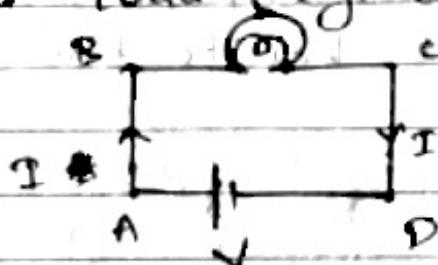


DC Circuit

Source of power is battery or d.c. power supply, conductors used to carry the current and load (e.g. lamp, heater, motor)




A closed path followed by a direct current dc is called as dc ckt.

- Load for dc ckt is usually a resistance.
 - Depending upon load / resistances connected in series, parallel or series-parallel fashion dc ckt's are classified as:
- Series ckt
 - Parallel ckt
 - Series-parallel

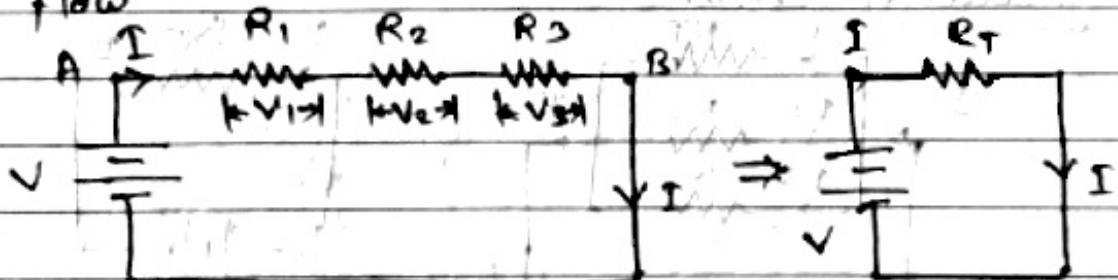1) Series ckt :-

Resistances are connected end to end so that there is only one path for the current to flow



$$R_T = R_1 + R_2 + R_3$$

As per Ohm's Law

voltage drop across resi. R_1 , $V_1 = IR_1$

~~$V_1 = IR_1 - R_2$~~ , $V_2 = IR_2$

~~$V_2 = IR_2 - R_3$~~ , $V_3 = IR_3$

For series ckt, sum of voltage drops = Applied volg

$$\therefore V = V_1 + V_2 + V_3$$

$$= IR_1 + IR_2 + IR_3$$

$$= I(R_1 + R_2 + R_3)$$

$$\frac{V}{I} = R_1 + R_2 + R_3$$

$\frac{V}{I}$ = Total resi.

$$R_T = R_1 + R_2 + R_3$$

for series dc ckt:

- Current flowing thr' each resistance is same
- Applied volg = sum of different volg. drops
- Every resistor of ckt, has its own volg. drop.

Voltage divider rule:-


Voltage drop across the resistances can be obtained as:

$$V_1 = IR_1 = \frac{V}{R_T} R_1 \quad (\because I = \frac{V}{R_T})$$

$$V_2 = IR_2 = \frac{V}{R_T} R_2$$

$$V_3 = IR_3 = \frac{V}{R_T} R_3$$

Parallel circuit

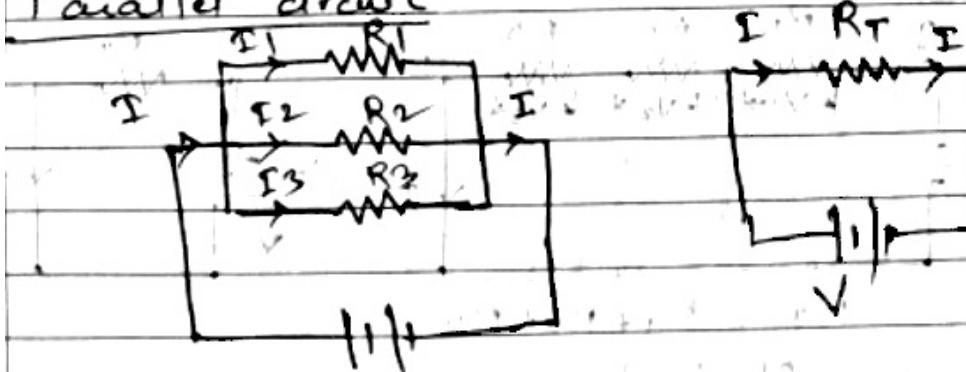

ckt in which one end of each resistance is joined to a common point and the other end of each resi. is joined to another

common point, so that there are many paths for current flow as the number of resistances is called a parallel circuit.

Total current I is divided into three parts

I_1 flowing thr' R_1 , I_2 flowing thr' R_2 and
 I_3 flowing thr' R_3 etc.

Voltage across each resistance is same.

By Ohm's Law we find

$$\text{Current thr' resi. } R_1, I_1 = \frac{V}{R_1}$$

$$\text{thr' } R_2, I_2 = \frac{V}{R_2}$$

$$\text{thr' } R_3, I_3 = \frac{V}{R_3}$$

For parallel ckt sum of the branch currents is equal to total current

$$I = I_1 + I_2 + I_3$$

$$= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$= V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$\frac{I}{V} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{1}{R_T} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

For parallel ckt

- Voltage drop across each resi. is same
- Total current = sum of branch currents
- Every resi. has its own current

Current divider rule:

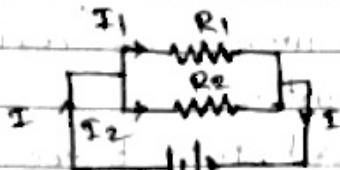

In a parallel circuit, two resistances R_1 and R_2 are connected in parallel across a battery of V volt. Current I is divided into two parts: I_1 flowing thru' R_1 and I_2 flowing thru' R_2 .

Total equivalent resi. R_T is given as

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$
$$= \frac{R_1 + R_2}{R_1 R_2}$$

$$\text{so, } R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$V = I R_T = I \frac{R_1 R_2}{R_1 + R_2}$$

Current thru' R_1 is

$$I_1 = \frac{V}{R_1}$$
$$= I \frac{R_1 R_2}{R_1 + R_2}$$
$$= \frac{I R_2}{R_1 + R_2}$$


$$I_1 = I \frac{R_2}{R_1 + R_2}$$

current thru' R_2 is

$$I_2 = \frac{V}{R_2}$$

$$I_2 = \frac{R_1}{R_1 + R_2}$$

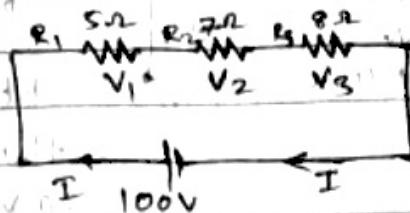1 Determine the current thr' and the voltages across three resistances of ohmic values 5Ω , 7Ω and 8Ω connected in series across 100V.



$$\text{Total resi.} = R_T = 5 + 7 + 8 = 20\Omega$$

$$I = \frac{V}{R_T} = \frac{100}{20} = 5A$$

$$\text{Voltage across } 5\Omega \text{ resi.} = 5I = 25V$$


$$\text{+1 } 7\Omega \text{ resi.} = 7I = 35V$$

$$\text{+1 } 8\Omega \text{ resi.} = 8I = 40V$$

$$V = V_1 + V_2 + V_3$$

$$= 100V$$

2

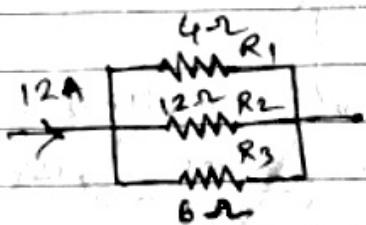

3 resistances are connected in parallel as shown in the dia.
If total current is 12A,
how is this current divided among the various resistors?

$$\text{Equivalent total Resi.} = R_{eq} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\therefore \frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{12} + \frac{1}{6} = \frac{3+1+2}{12} = \frac{6}{12} = 0.5\Omega$$

$$\therefore R_{eq} = 2\Omega$$

$$\text{Voltage across all} = V = IR_{eq} = 12 \times 2 = 24V$$


$$\text{Current thr' } 4\Omega \text{ resi.} = \frac{V}{R_1} = \frac{24}{4} = 6A$$

$$\text{current thr' } 12\Omega \text{ resi.} = \frac{V}{R_2} = \frac{24}{12} = 2A$$

$$\text{current thr' } 6\Omega \text{ resi.} = \frac{V}{R_3} = \frac{24}{6} = 4A$$

Sums on Resistance for series + parallel ca.

1.

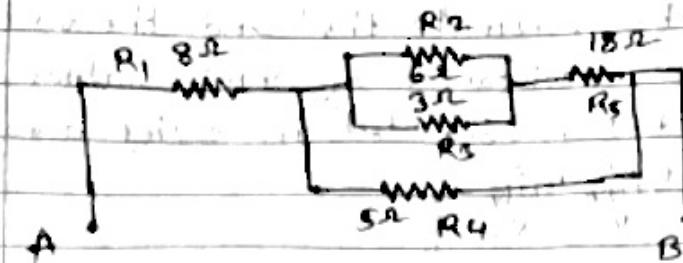

Calculate


effective
resi of the
det and cu

the 8Ω resi

60V is applic
betw pts. A &


$$R_2 = 6\Omega, R_3 = 3\Omega$$
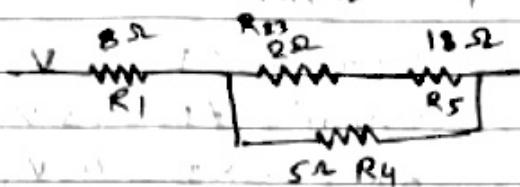
$$R_2 // R_3 = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \times 3}{9} = 2\Omega$$




R_{23} & R_5 are in series, so get added.

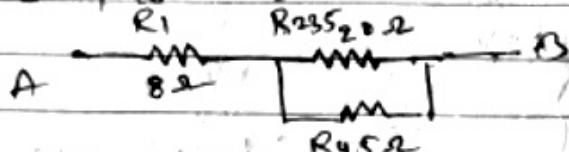
$$R_{235} = 2\Omega + 18\Omega = 20\Omega$$


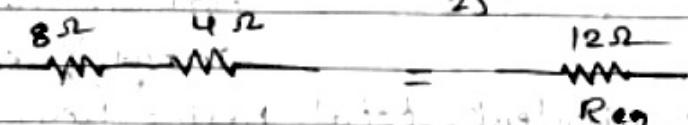
$$\text{Now } R_{235} // R_4 \therefore R_{2354} = \frac{20\Omega \times 5\Omega}{25\Omega} = \frac{20 \times 5}{25} = 4\Omega$$




$$\text{Req.} = 12\Omega$$

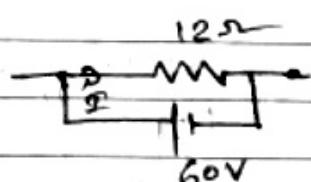


$$\therefore I = \frac{V}{R} = \frac{60}{12} = 5 \text{Amp.}$$


\therefore Current thro' 8Ω resi = 5Amp.

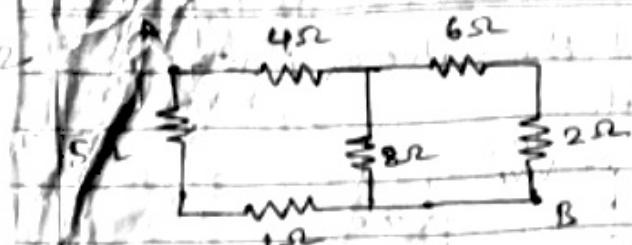

Naming the nodes for the given circuit

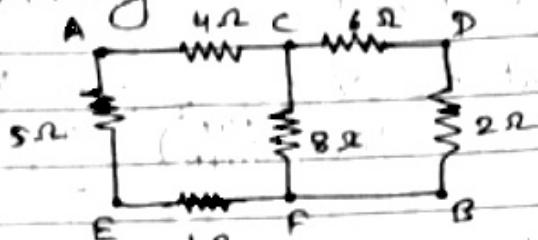


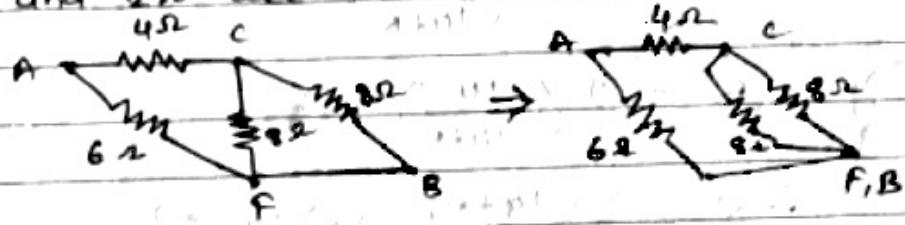Resistors 5Ω and 1Ω are in series. Also resistors 6Ω and 2Ω are in series. So new circuit will be




$$8\Omega \parallel 8\Omega = \frac{8 \times 8}{8+8} = \frac{64}{16} = 4\Omega$$

Now circuit will be

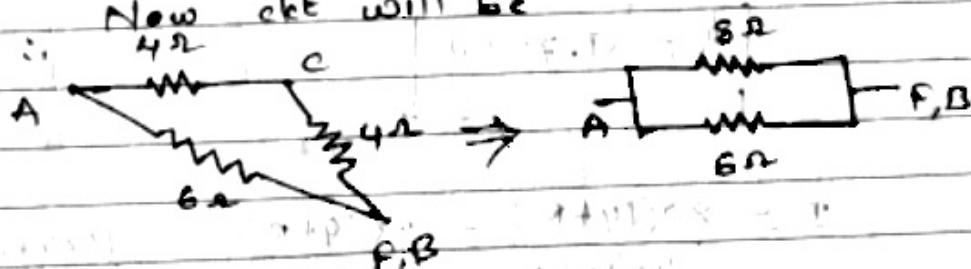


$$6\Omega \parallel 8\Omega = \frac{6 \times 8}{6+8} = \frac{48}{14} = 3.43\Omega$$

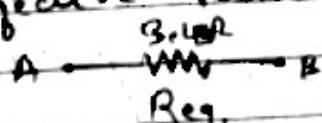∴ Effective resistance between nodes A & B is


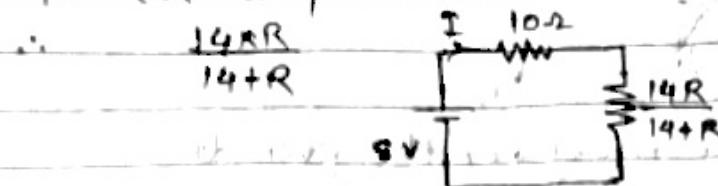
#2 In the ckt shown, find the value of R .
 $14\Omega + R$ in parallel.



$$\text{Total circuit current } I = \frac{V}{10 + \left(\frac{14R}{14+R} \right)} = \frac{80(14+R)}{140 + 24R} \quad (1)$$

By current division rule, I_1 can be calculated as

$$I_1 = I \left(\frac{14}{14+R} \right)$$

$$3 = I \left(\frac{14}{14+R} \right)$$

$$\therefore I = \frac{3(14+R)}{14} \quad (2)$$

Solving eq's (1) & (2)

$$R = 9.722\Omega$$

$$I = \frac{80(14+R)}{140 + 24R} = \frac{3(14+R)}{14} \quad \frac{1120 + 80R}{140 + 24R} = \frac{42 + 3R}{14}$$

$$= 80 \times 14 = 3(140 + 24R) \quad 14(1120 + 80R) =$$

$$= 112 = 140 + 24R$$

11

$$(42 + 3R) \times 14 =$$




$$15680 + 1120R =$$

$$5880 + 1008R + 480R + 72R^2$$

Source Transformation




Case I

A voltage source with a series resistance can be converted into equivalent current source with parallel resi.

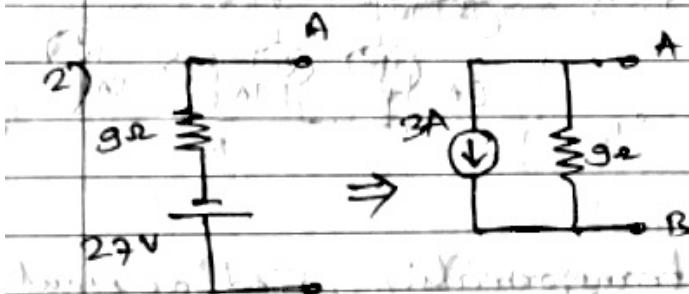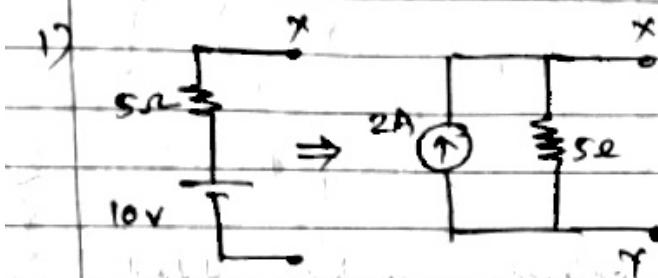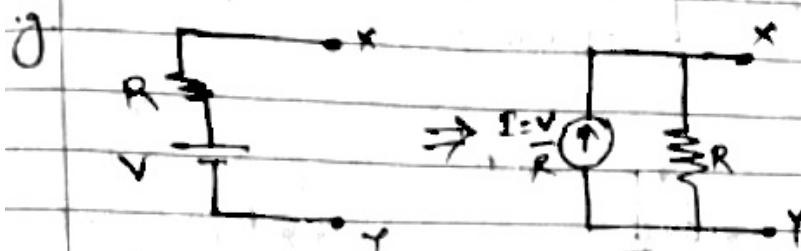

Case II

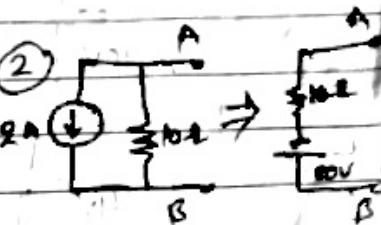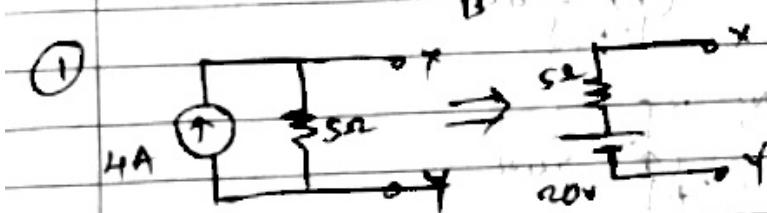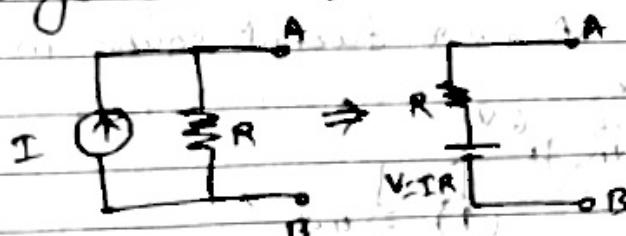A current source with a parallel resistance can be converted into an equivalent voltage source with series resistance.




Conver.
equi.


case III

Series voltage sources can be added.

①

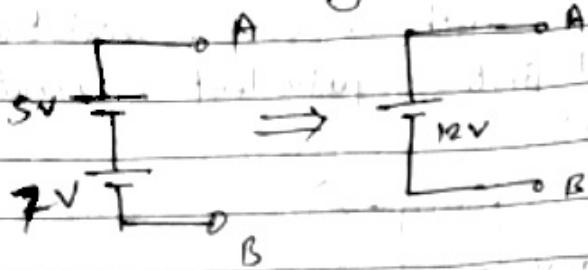


②

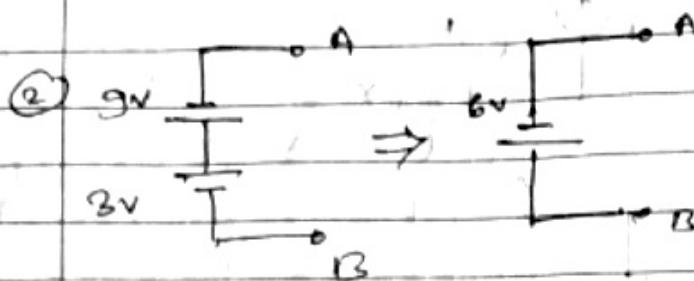


Case IV

Parallel current sources can be added


①

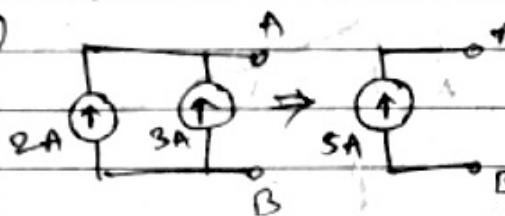



②

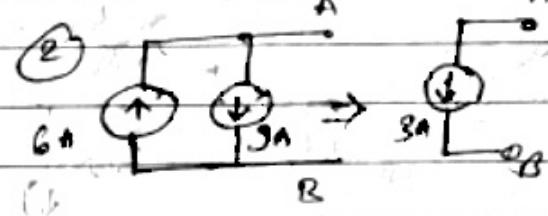

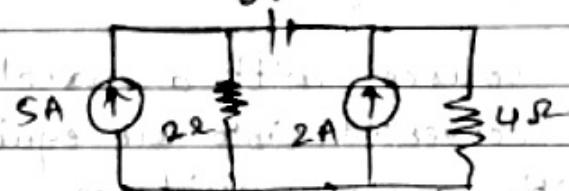
#1 Using source transformation, find current in 4Ω res^{CV} in foll. given ckt.



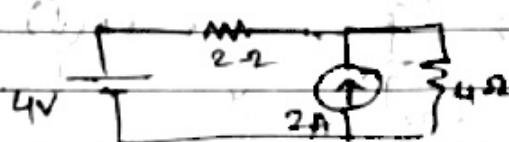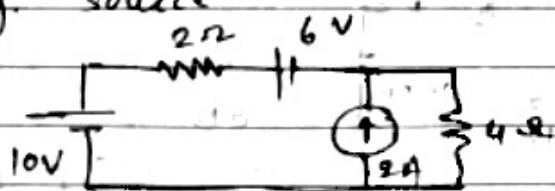Converting 5A & 2Ω current source in equi. volg. source



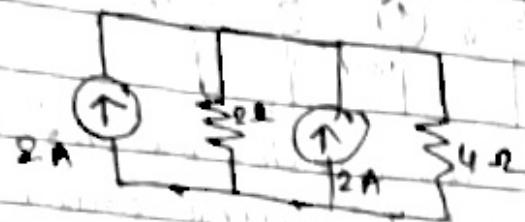Converting 4V in series with 2Ω resⁿ into equivalent current source, we get



Adding two parallel current sources




By current division method current in 4Ω resistⁿ can be found as

$$I_2 = 4 \frac{2}{2+4}$$

$$I_2 = 1.33A$$

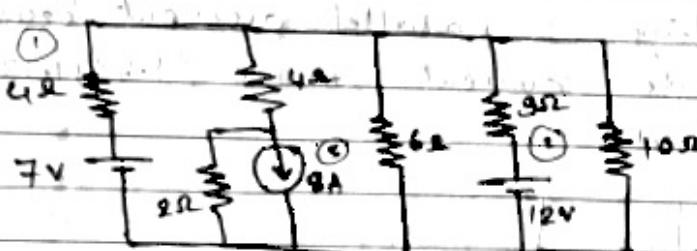
2 By source transformation, find current in 10Ω resistor in the circuit shown:




Converting 2 volg. sources into current source and one current source into eqw. voltage source



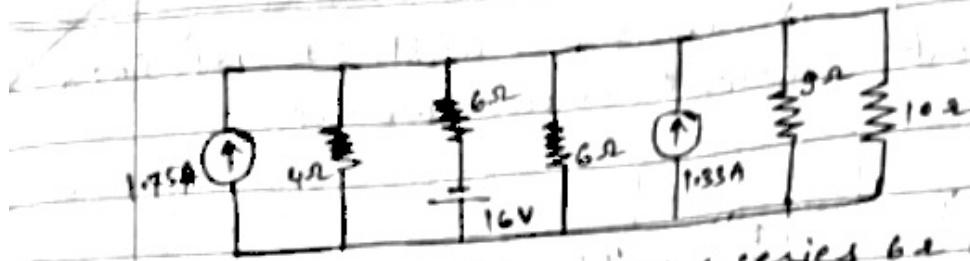For volg. source ③ two series resistors can be added



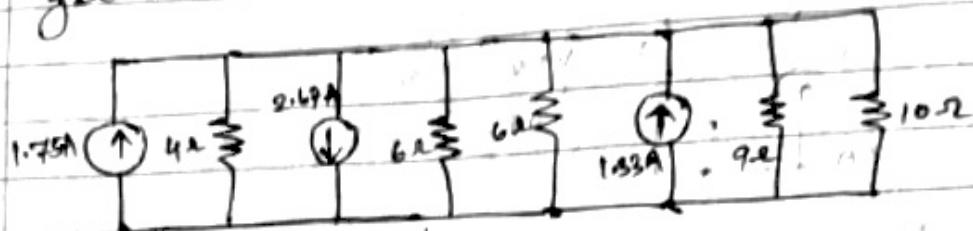Now converting 16V series voltage source into equivalent current source we get



Converting parallel resistors into equivalent single re.


$$\frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{6} + \frac{1}{6} + \frac{1}{9}$$

$$= \frac{1}{4} + \frac{1}{3} + \frac{1}{9} = \frac{9+12+4}{36} = \frac{25}{36}$$


$$\therefore R_{eq} = 1.44\Omega$$

Converting 3 parallel current sources in single current source ($1.75 + 1.33 - 2.69A$)

$$= 0.41A$$

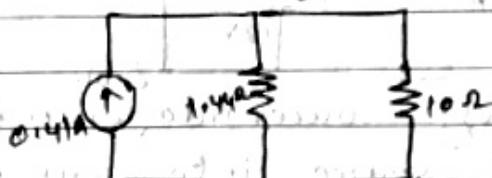

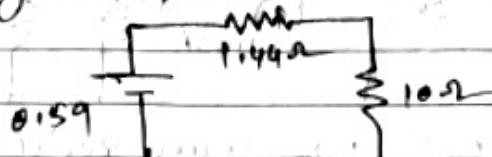Now, converting current source into eq. volg source



Using Ohm's law,


current in 10Ω resistor can be given as

$$I = \frac{V}{R}$$

$$R = (1.44 + 10)\Omega$$

$$= \frac{0.59}{1.44 + 10}$$

$$I = 0.0516 A$$

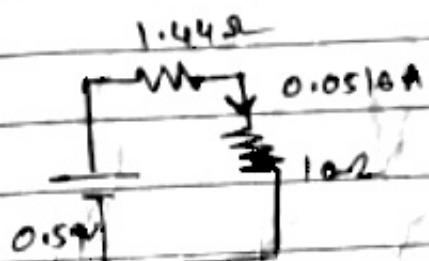


Elements of Electrical and Electronics Engineering

Module 1 DC Circuits

Electric Energy Sources

Classification:

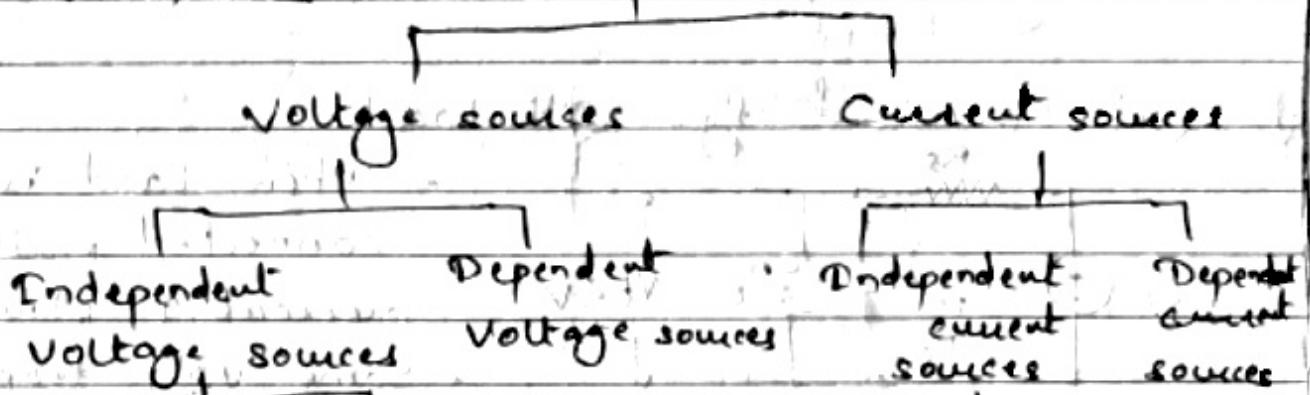


Ideal Volt. sources Practical

Independent Voltage sources: Ideal Practical

Terminal voltage of the source is not dependent on any other voltage source or current source.

Ideal voltage sources:-


Symbol:

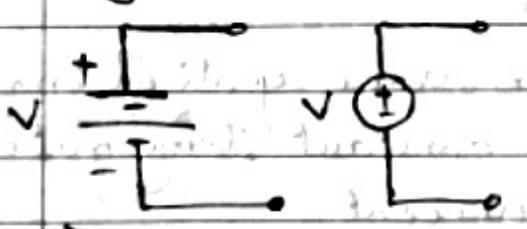

* Source resistance is zero

* Constant terminal volt. = V without load ($R_L = \infty$)


* or with load,

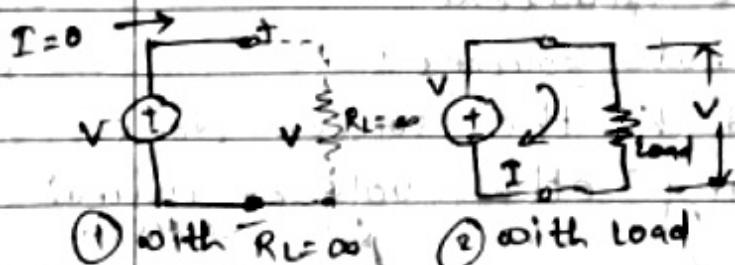

* Terminal volg. is independent of load.


Practical voltage source :-

Symbol

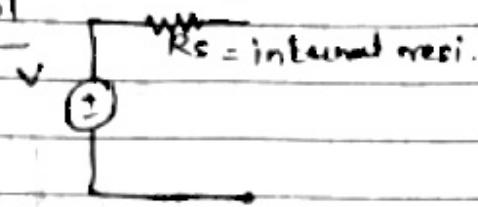

- 2 cases • With internal series resistance R_s .


(a)

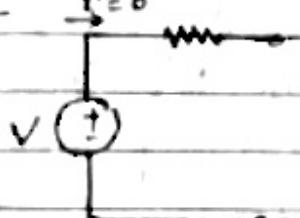

• Terminal voltage $V_t = V$ with no load or $R_L = \infty$

• $I = 0$, so no drop across R_s , so terminal volg $V_t = V$

- (b) Terminal volg with load

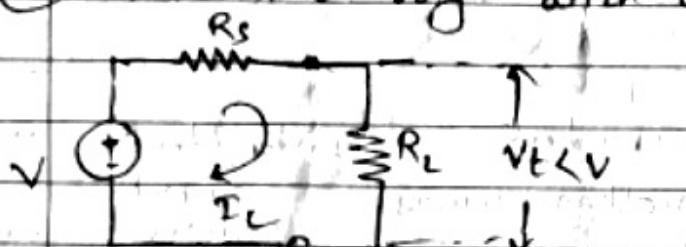

• When load is connected, finite load current I flows.

• Some volg. drop across R_s

• So terminal volg. $V_t < V$

• With increase in load current I_L , terminal volg. decreases.

$$\text{as } V_t = V - I R_s$$

Current Sources :- In some applications it is reqd. to have constant time rate of es or constant current.

Independent Current sources :-

Current supplied by the source does not depend on any other volg or current source.



2 Types:-

1) Ideal current source

2) Practical current source

Ideal current source

Symbol

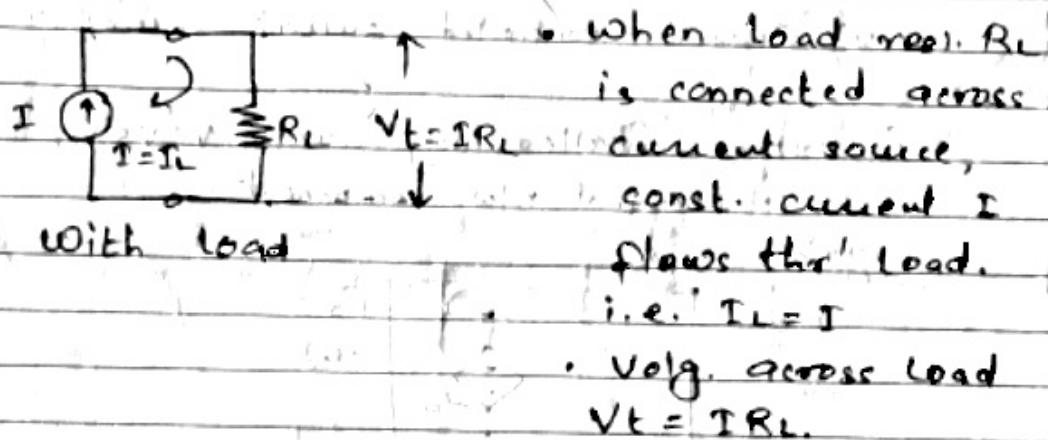
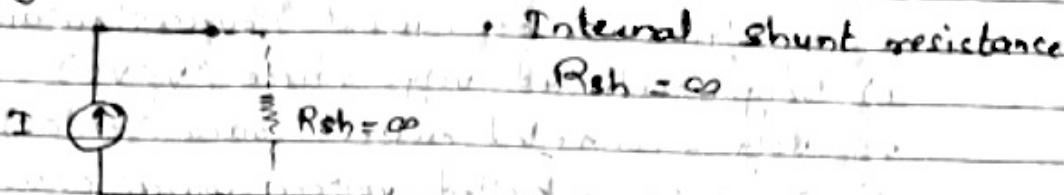


Practical current source

Symbol

R_{sh} = Internal shunt resistance

, finite internal shunt resi.

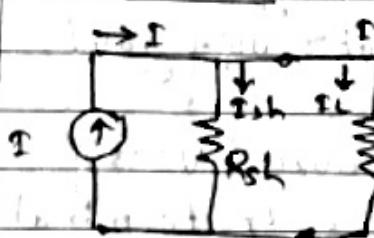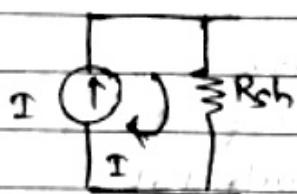

When load R_L is connected load current I_L will start flowing thr' it.

But due to internal R_{sh} source current I gets divided bet' R_{sh} & R_L .

Current thr' R_L is less than

I

$$I_L = I - I_{sh} \quad I_L < I$$

Dependent Sources

If volg. or current of a source depends upon some other volg. or current, it is called as dependent or controlled source.


4 types: Depending on whether the control variable is volg. or current and controlled source is a volg. source or current source, there are 4 types

- 1) Volg.-controlled volg. source (Vcvs)
- 2) Volg.-controlled current source (Vccs)
- 3) Current-controlled voltage source (Ccvs)
- 4) Current-controlled current source (Cccs)

① Voltage-controlled volg. source (Vcvs)

- 4 terminal n/w component -

Symbol

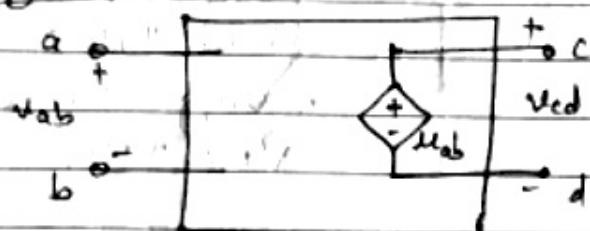

. It establishes a volg. v_{cd} bet' two points c and d in the ckt that is proportional to volg. v_{ab} bet' two points a and b.


component as a volg. source.

$$v_{cd} = \mu v_{ab}$$

v_{cd} depends upon control volg. v_{ab} .

μ - dimensionless constant, volg. gain.

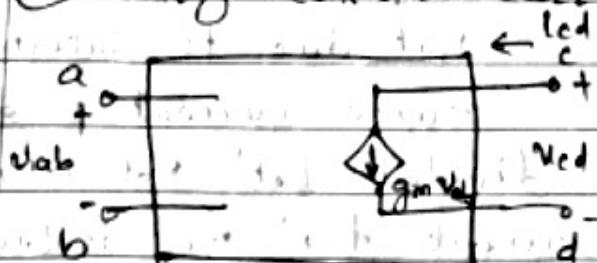② Voltage-controlled current source (Vccs)



- 4 terminal n/w

component that establishes a current i_{cd} in

a branch of the ckt that is proportional


to the voltage v_{ab} bet' two points a and b.

$$i_{cd} = g_m v_{ab}$$

g_m - transconductance

i_{cd} depends only
on control volt. and const. (unit is A/V or Siemens)
 g_m . dimensionless

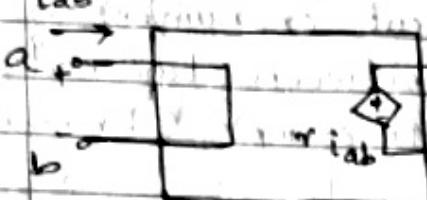③ Current-controlled voltage source (CCVS)




$$v_{cd} = r_{ab}$$

r - transresistance
or mutual resistance
It is constant and
has unit V/Amp or ohm.

4 terminal nw component that establishes a voltage v_{cd} between two points c and d in the circuit that

i_{ab} in some branch of the ckt.

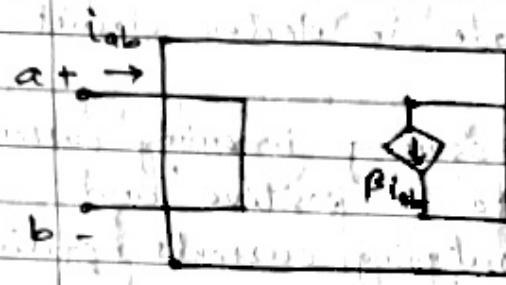④ Current-controlled current source (CCCS)



4 terminal nw component that establishes a current i_{cd} in one branch of a circuit that is proportional to the current i_{ab} in some branch of the network.

$$i_{cd} = \beta i_{ab}$$

Current i_{cd} depends only on the control current i_{ab} and dimensionless const. β
 β - current gain



Kirchhoff's Laws

- Useful for analysis of electric circuit.

Terms used.

1) Node :- It is a junction where two or more circuit elements are connected together. In above ckt, A, B, C, D are nodes.


2) Branch :- An element or number of elements connected between two nodes constitutes a branch. For example, 3 branches BAP, BCP and BD

3) Loop :- Any closed part of the circuit.
ABDA, BCDB, ABCDA

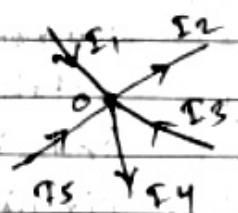4) Mesh :- Elementary form of a loop & cannot be

Kirchhoff's Current Law (KCL)

The algebraic sum of currents meeting at a junction or node in electric circuit is zero.



Assuming incoming currents to be positive and outgoing currents negative

$$I_1 + (-I_2) + I_3(-I_4) + I_5 = 0$$

$$I_1 + I_3 + I_5 = I_2 + I_4$$

The sum of currents flowing towards any junction in an electric circuit = sum of currents flowing away from the junction
 Incoming currents | Outgoing currents

Kirchhoff's Voltage Law: (KVL)

- Related to electromotive forces and voltage drops in a circuit.

KVL is stated as:

In any closed circuit or mesh, the algebraic sum of the electromotive forces and the voltage drops is equal to zero.

Sign Conventions

- Rise in potential can be assumed positive while a fall in potential can be considered negative.
 - Going from positive terminal of source to negative terminal is a fall in potential so emf is assigned -ve sign.

$$\begin{array}{c} E_1 \\ \text{---} \\ + \quad | \quad - \\ \text{---} \end{array} \Rightarrow -E_1$$

- Going from negative terminal of source to positive terminal, there is a rise in potential so emf is given positive sign.


$$\begin{array}{c} E_2 \\ \text{---} \\ - \quad | \quad + \\ \text{---} \end{array} \Rightarrow +E_2$$

- When current flows through a resistor, there is a voltage drop across it. If we go through mesh in the same direction as the current, there is a fall in the potential & so for potential drop sign is -ve

$$\begin{array}{c} \text{---} \\ \rightarrow V_{R1} \\ I_1 \quad R_1 \\ \text{---} \end{array} \quad \begin{array}{c} \text{---} \\ \leftarrow V_{R2} \\ R_2 \quad I_2 \\ \text{---} \end{array}$$

Voltage drop = $-I_1 R_1 + I_2 R_2$

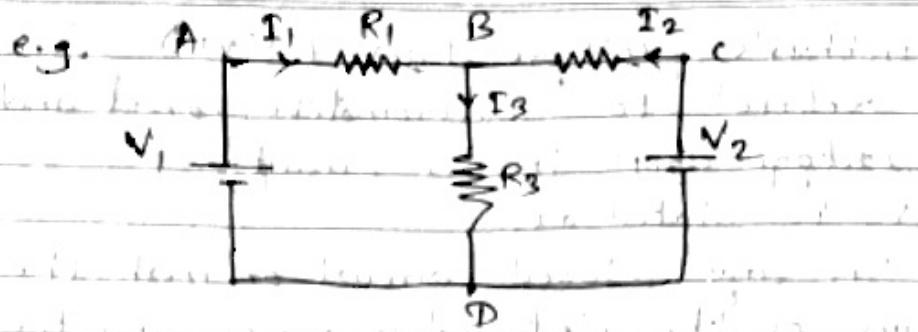If we go opposite to current direction there is rise in pot. so sign is +ve.



Applying KVL to above ckt


For loop ABDA

$$V_1 - I_1 R_1 - I_3 R_3 = 0$$

Applying KVL to Loop ABCDA

$$V_1 - I_1 R_1 + I_2 R_2 - V_2 = 0$$

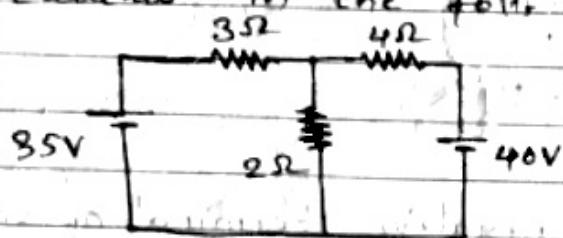
1 Using Kirchhoff's laws, calculate the branch currents in the foll. ckt.



Steps

1. In the given ckt name the nodes.

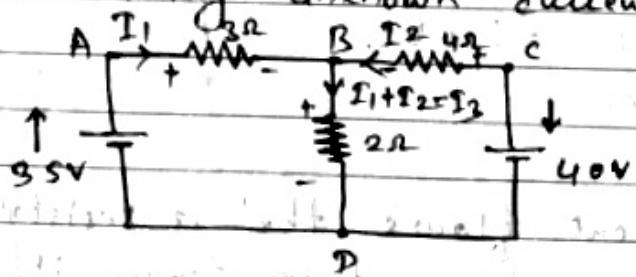2. Assuming unknown currents, ckt will be



Applying KVL to Loop ABDA

$$35 - 3I_1 - 2(I_1 + I_2) = 0 \quad \text{--- (1)}$$

$$35 - 3I_1 - 2I_1 - 2I_2 = 0$$

$$35 = 5I_1 + 2I_2 \quad \text{--- (1)}$$

$$5I_1 + 2I_2 = 35 \quad \text{--- (2)}$$

Applying KVL to Loop ABCDA

$$35 - 3I_1 + 4I_2 - 40 = 0$$

$$3I_1 - 4I_2 = -5 \quad \text{--- (3)}$$

From eq's (2) and (3) we get

$$I_1 = 5A$$


$$I_2 = 5A$$

$$I_3 = I_1 + I_2$$

$$I_3 = 10A$$


$$\therefore I_1 = I_2 = 5A, I_3 = 10A$$

2

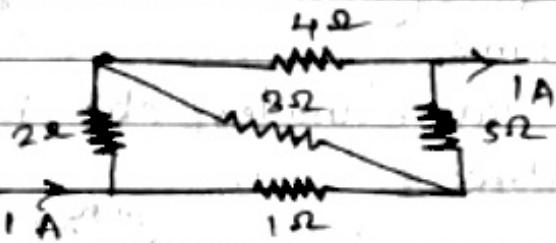

Using Kirchhoff's laws

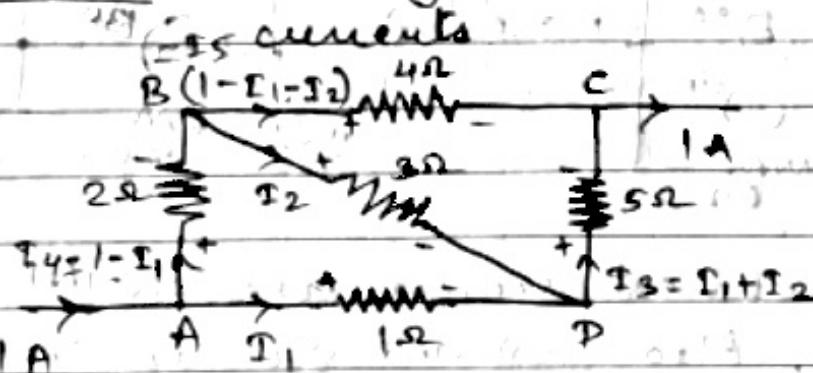Step 1 Naming nodes & assuming unknown currents



Step 2 Applying KVL to loop ABDA

$$I_1 - 2(1 - I_1) - 3I_2 = 0$$

$$\therefore 3I_1 - 3I_2 = 2 \quad \text{--- (1)}$$

Applying KVL to loop BCDB

$$-4(1 - I_1 - I_2) + 5(I_1 + I_2) + 3I_2 = 0$$

$$-4 + 4I_1 + 4I_2 + 5I_1 + 5I_2 + 3I_2 = 0$$

$$9I_1 + 12I_2 = 4 \quad \text{--- (2)}$$

Solving eq's ① and ② we get

$$I_1 = 0.571 \text{ A}$$


$$I_2 = -0.0952 \text{ A}$$

$$I_1 + I_2 = I_3 = 0.495 \text{ A}$$

$$-I_1 = I_4 = 0.429 \text{ A}$$


$$-I_1 - I_2 = I_5 = 0.524 \text{ A}$$

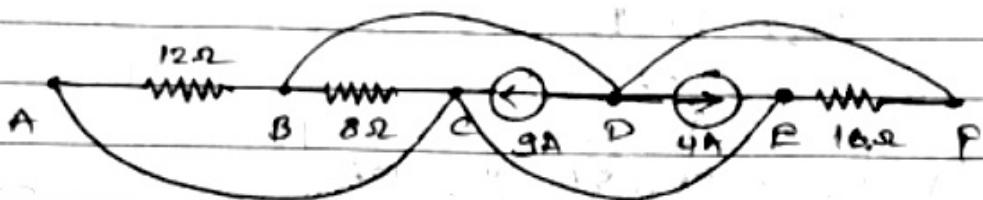3 Calculate the power dissipation in each resistor in the network shown:



Nodes A, C and F are same. Also nodes B, D and F are same.

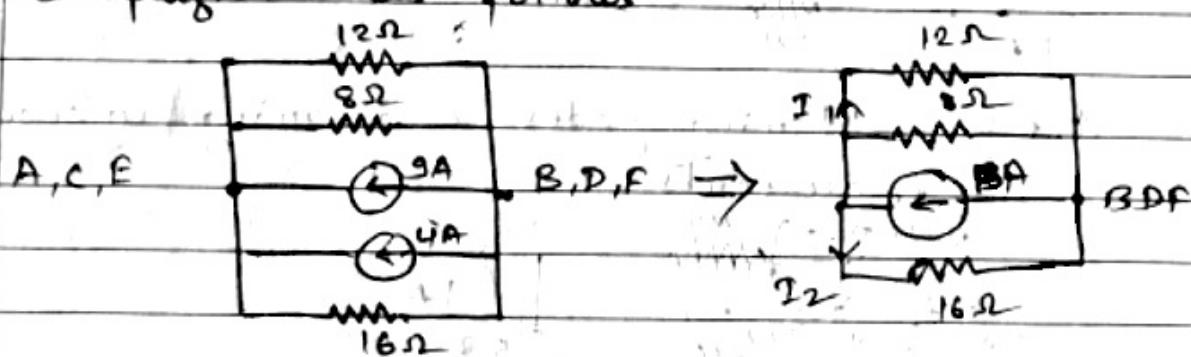
By joining the same nodes, ckt is simplified as follows



Both the current sources are in || so get added. Also 12Ω and 8Ω are in ||.

$$\therefore 12\Omega \parallel 8\Omega = \text{Req} = \frac{12 \times 8}{12+8} = \frac{96}{20} = 4.8\Omega$$

∴ Ckt will become

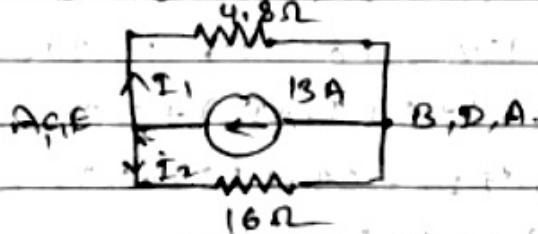

13A total current is divided in the circuit as $I_1 + I_2$ shown in the fig.

By current division rule

$$I_1 = \frac{13 \times 16}{16 + 4.8} = 10A$$

$$I_2 = \frac{13 \times 4.8}{16 + 4.8} = 3A$$

current I_1 is divided in two resistors 12Ω & 8Ω .

∴ By current divi

current in 8Ω res will be

$$I_{8\Omega} = \frac{10}{R_1 + R_2} I_1 = \frac{10 \times 12}{8 + 12} = 6A$$

$$I_{12\Omega} = \frac{I_1 R_2}{R_1 + R_2} = \frac{10 \times 8}{8 + 12} = 4A$$


Power dissipation in $res = I^2 R$

$$\therefore \text{Power dissipation in } 12\Omega \text{ res} = (I_{12\Omega})^2 \times 12 \\ = 4^2 \times 12 \\ = 192W$$


$$\text{Power dissipation in } 8\Omega \text{ res} = (I_{8\Omega})^2 \times 8 \\ = (6)^2 \times 8 \\ = 288W$$

$$\text{Power dissipation in } 16\Omega \text{ res} = (I_{16\Omega})^2 \times 16 \\ = (3)^2 \times 16 \\ = 144W$$

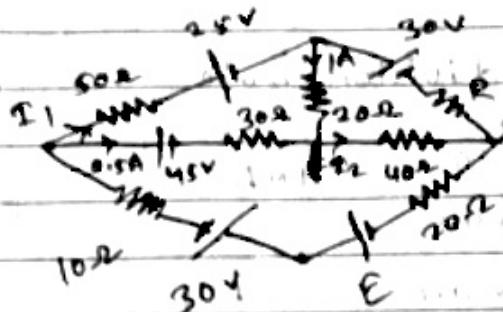4. For the network shown, determine (1) I_1 , I_2 and I_3
 (2) resistance R and (3) value of emf E



After naming the nodes, circuit will be

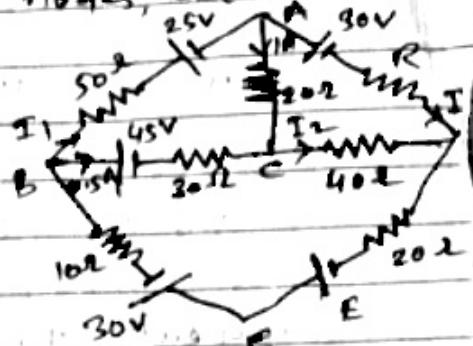

1) At node C, by KCL

$$I_2 = 0.5 + 1, \therefore I_2 = 1.5A$$

Applying KVL to loop ACBA

$$-20(I_1) + (30 \times 0.5) + 45 - (50 \times I_1) - 25 = 0$$

$$\therefore I_1 = 0.3A$$

At node A, by applying KCL we get

$$I_1 = 1 + I_3 \therefore 0.3 = 1 + I_3 \therefore I_3 = -0.7A$$

2) Applying KVL to loop ADCA

$$-30 - I_3 R + 40 I_2 + (20 \times 1) = 0$$

putting values of I_2 & I_3 in above eq.
 we get $R = -71.43\Omega$

3) At node D, by applying KCL

$$\text{current in branch DEB} = I_2 + I_3 = 1.5 - 0.7 \\ = 0.8A$$

Applying KVL to loop DEBCD we get


$$(-20 \times 0.8) + E - 30 - (10 \times 0.8) - 45 - (30 \times 0.5) - (40 \times 1) = 0$$

\therefore After solving this eq. we get

$$E = 174V$$


Star-Delta (Δ - Y) Transformation:

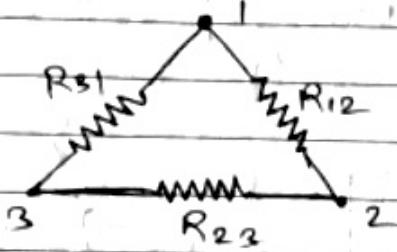- Some n/w s in which the resistances are neither in series nor in parallel and are connected in Δ -or Y -connection.
- n/w cannot be simplified by series/parallel clt rules.
- So first Δ -connection into equivalent Y -conn' and vice-versa is done and then application of series/parallel clt rules is made possible.



Delta Connection

Fig. a

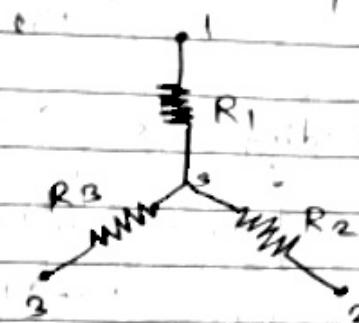

Star connection

fig b

1) Delta (Δ) to Star (Y) Transformation

As per Delta connection n/w in fig a

$$\text{Resistance bet' terminals 1 and 2} = \frac{R_{12}}{(R_{23} + R_{31})}$$

$$= \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad (1)$$

$$R_{12} + R_{23} + R_{31}$$

As per Y (star) connection n/w in fig b

$$\text{Resistance bet' terminals 1 and 2} = R_1 + R_2 \quad (2)$$

Since two n/w s are electrically equivalent,

$$R_1 + R_2 = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad (3)$$

Similarly in Δ n/w

$$\text{Resi. bet' terminals 2 and 3} = \frac{R_{23}}{(R_{12} + R_{31})} = R_{23}(R_{12} + R_{31}) \quad (4)$$

$$R_{23} + R_{12} + R_{31}$$

In Y n/w

$$\text{Resi. bet' 2 & 3} = R_3 + R_2 \quad (5)$$

$$\therefore R_2 + R_3 = \frac{R_{23}(R_{12} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad (6)$$

Similarly referring A and Y m/w
for resistance bet pts 3 and 1 we get

$$R_1 + R_3 = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad \textcircled{7}$$

Subtracting eq $\textcircled{6}$ from eq $\textcircled{7}$

$$R_1 - R_3 = \frac{R_{12}R_{31} - R_{23}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \textcircled{8}$$

Adding eq's $\textcircled{7}$ and $\textcircled{8}$

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \textcircled{9}$$

Similarly obtaining

$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}} \quad \textcircled{10}$$

$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}} \quad \textcircled{11}$$

Star (Y) to Delta (Δ) Transformation.

Multiplying eq's $\textcircled{9}$ and $\textcircled{10}$

$$R_1 R_2 = \frac{R_{12}^2 R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})^2} \quad \textcircled{12}$$

Multiplying eq's $\textcircled{10}$ and $\textcircled{11}$

$$R_2 R_3 = \frac{R_{23}^2 R_{31} R_{12}}{(R_{12} + R_{23} + R_{31})^2} \quad \textcircled{13}$$

Multiplying eq's (9) and (11) we get

$$R_3 R_1 = \frac{R_{31}^2 R_{12} R_{23}}{(R_{12} + R_{23} + R_{31})^2} \quad (14)$$

Adding eq's (12) (13) and (14) we get

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} R_{23} R_{31} (R_{12} + R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})^2}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

or using $R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = R_{12} R_3$$


$$\therefore R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \quad (15)$$

Similarly we can obtain


$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \quad (16)$$

$$\therefore R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} \quad (17)$$

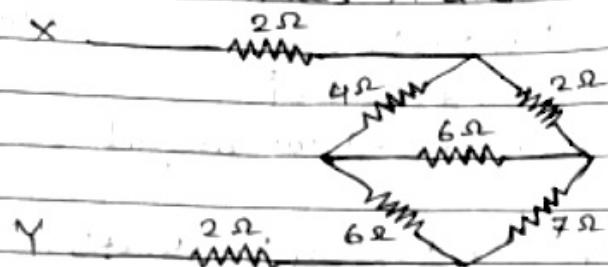
1 Find the equivalent resistance bet' the terminals X and Y in the foll. n/w



Naming different nodes in the given ckt

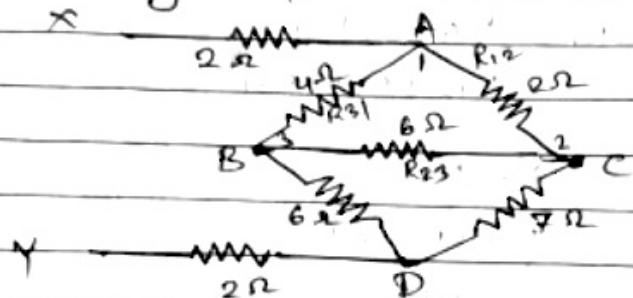

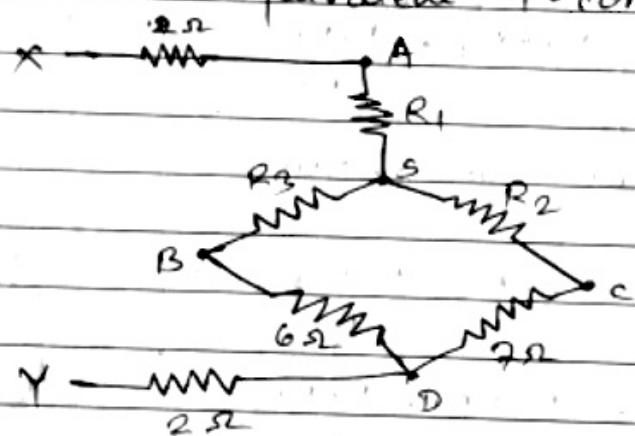ΔABC is Δ connection, so converting this into equivalent Y -connection. $\Delta(ABC) = Y(ABC)$



$$\therefore R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{4 \times 2}{4 + 2 + 6}$$

$$R_1 = 0.67\Omega$$

$$R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{6 \times 2}{4 + 2 + 6}$$

$$R_2 = 1\Omega$$


$$R_3 = \frac{R_{31} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$= \frac{6 \times 4}{4 + 2 + 6}$$


$$R_3 = 2\Omega$$



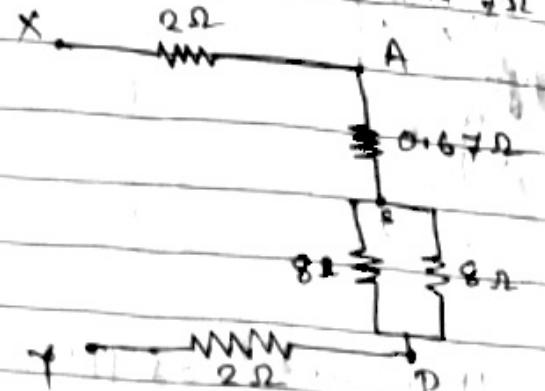
Now resistors 6Ω and 2Ω are in series.
Also resistors 1Ω and 7Ω are in series.



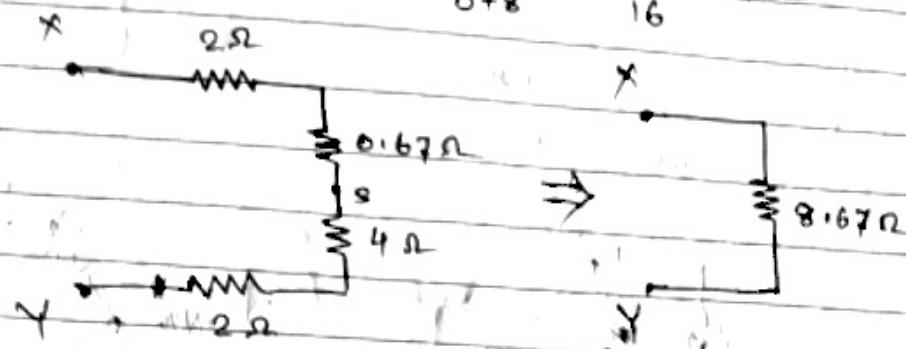Now $8\Omega \parallel 8\Omega \therefore \frac{8 \times 8}{8+8} = \frac{64}{16} = 4\Omega$




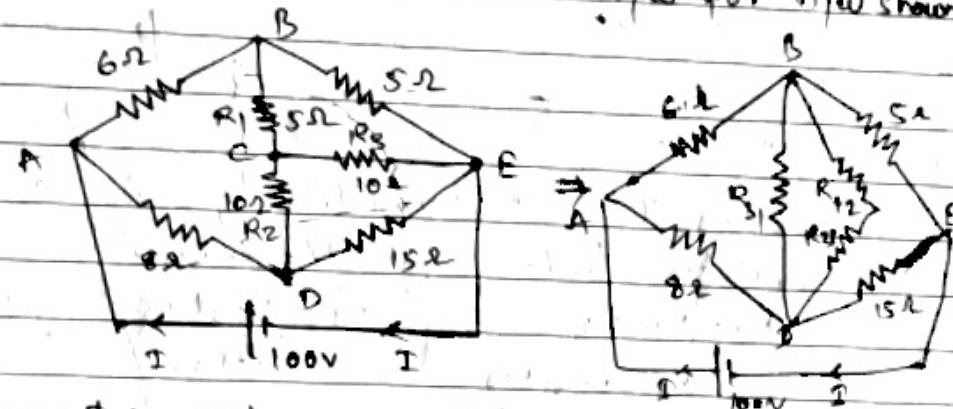Q2 Find the current I in the n/w for n/w shown



Converting star-connection of $5\Omega, 10\Omega, 10\Omega$ into delta-connection, i.e. $\Delta(BED)$ to $\Delta(BED)$

$$\begin{array}{l}
 R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \\
 = 5 + 10 + \frac{(5 \times 10)}{10} \\
 = 20\Omega
 \end{array}
 \quad
 \begin{array}{l}
 R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \\
 = 10 + 10 + \frac{(10 \times 10)}{5} \\
 = 40\Omega
 \end{array}
 \quad
 \begin{array}{l}
 R_{31} = R_3 + R_1 + \frac{R_1 R_3}{R_2} \\
 = 5 + 10 + \frac{(5 \times 10)}{10} \\
 = 20\Omega
 \end{array}$$

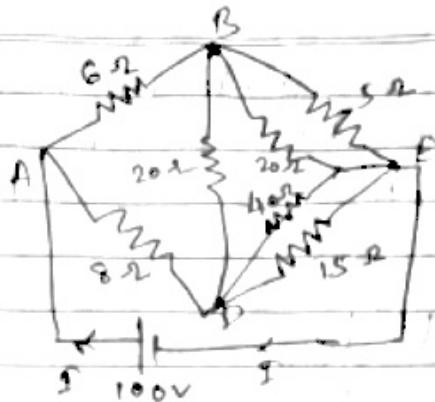

Resistors $20\Omega \parallel 15\Omega$ and $40\Omega \parallel 15\Omega$


$$\frac{20 \times 15}{20+15} = \frac{100}{25}$$

$$= 4\Omega$$

$$\frac{40 \times 15}{40+15} = \frac{600}{55}$$

$$= 10.91\Omega$$

\therefore now will be...

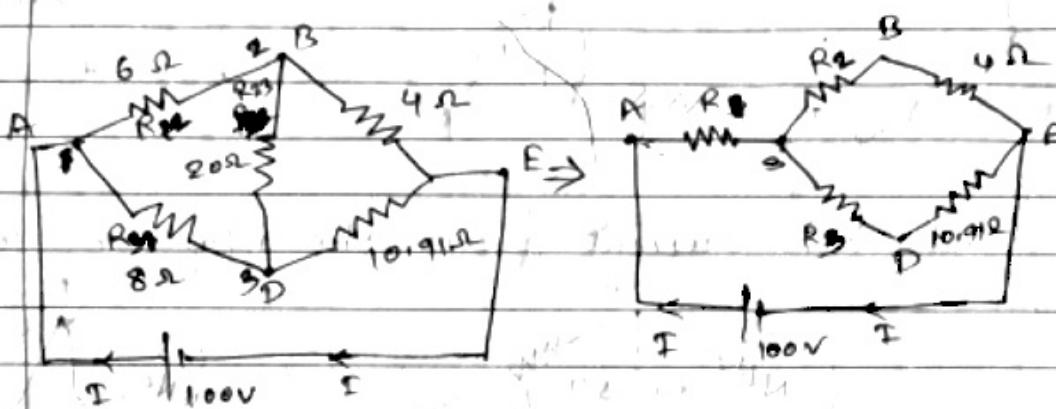

converting Δ -connection of $6\Omega, 20\Omega$ and 8Ω resistors into equil. Y -connection.

$$R_1 = R_{12} R_{31}$$

$$R_{12} = R_{23} R_{13}$$

$$R_3 = R_{31} R_{23}$$

$$R_{12} + R_{23} + R_{31}$$

$$R_{12} + R_{23} + R_{31}$$

$$R_{12} + R_{23} + R_{31}$$

$$= \frac{6 \times 8}{6+20+8}$$


$$= 6+20+8$$

$$= \frac{20 \times 6}{6+20+8} = \frac{8 \times 20}{6+20+8}$$

$$= 1.41\Omega$$




$$= 3.53\Omega$$

$$= 4.71\Omega$$

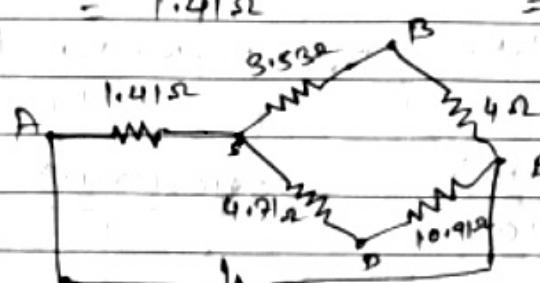

Now $3.53\Omega + 4\Omega$ are in series and 4.71Ω and 10.91Ω are in series. $\therefore 3.53 + 4\Omega = 7.53\Omega$

$$4.71 + 10.91\Omega = 15.62\Omega$$

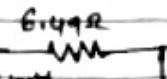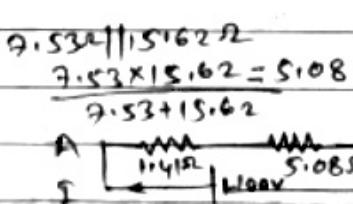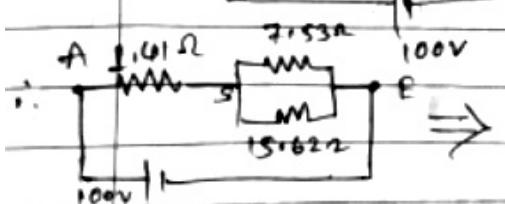

$$I = \frac{100}{6.49\Omega} = 15.41A$$


1.2 Mesh and Nodal Analysis E

Maxwell's Mesh Current Method:

- Kirchhoff's voltage law is applied to each mesh in terms of mesh currents instead of branch currents.


Steps for Maxwell's Mesh current method:

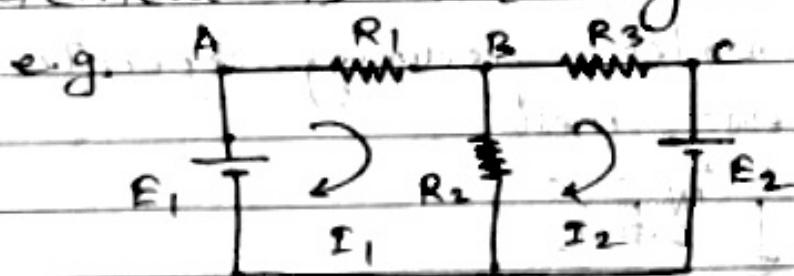- Each mesh is assigned a separate mesh current. For convenience, all mesh currents are assumed to flow in clockwise direction or anticlockwise direction.
- If two mesh currents are flowing through a ckt element, the actual current in the ckt element is the algebraic sum of two.



This ckt consists of two meshes ABD Δ + BCD Δ . I_1 & I_2 mesh currents are assigned respectively. If we assume clockwise direction & move from B to D, then current is $I_1 - I_2$. If we go from D to B in anticlockwise direction, current is $I_2 - I_1$.

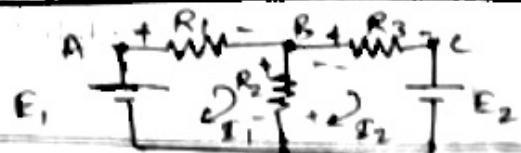- Kirchhoff's voltage law is applied to write eqn for each mesh in terms of unknown mesh currents.



If value of any mesh current comes out to be negative in the solution, it means that true direction of that mesh current is anticlockwise.

Applying KVL to mesh ABDA

$$E_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$I_1 (R_1 + R_2) - I_2 R_2 = E_1 \quad \text{--- (1)}$$


Applying KVL to mesh BCDB

$$-I_2 R_2 - E_2 - (I_2 - I_1) R_1 = 0$$


$$-I_2 R_2 + (R_1 + R_2) I_1 = -E_2 \quad \text{--- (2)}$$

Solving eq's (1) and (2) I_1 & I_2 can be found.

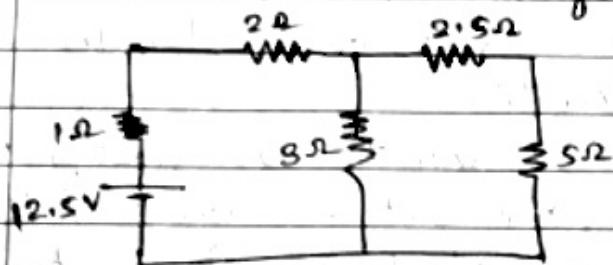- #1 Using mesh current method, find magnitude and direction of the current flowing through 1Ω resistor in the foll. netw



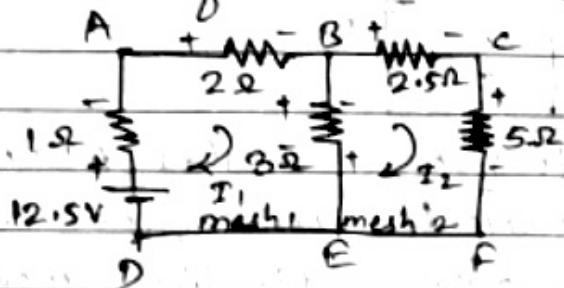Naming the nodes & assuming separate mesh current for each mesh.



Applying KVL to mesh 1

$$12.5 - I_1 - 2I_1 - 3(I_1 - I_2) = 0$$

$$-6I_1 + 3I_2 = -12.5 \quad \text{--- (1)}$$

Applying KVL to mesh 2

$$-3(I_2 - I_1) - 2.5I_2 - 5I_2 = 0$$

$$3I_1 - 10.5I_2 = 0 \quad \text{--- (2)}$$

Solving eq's ① + ②

$$-6I_1 + 3I_2 = -12.5$$

$$3I_1 - 10.5I_2 = 0$$

$$-3I_1 - 6.5I_2 = -12.5$$

$$\therefore -6.5I_2 + 12.5 = 3I_1$$

$$\therefore I_1 = \frac{-6.5I_2 + 12.5}{3}$$


putting this in eq ②

$$3\left(\frac{-6.5I_2 + 12.5}{3}\right) - 10.5I_2 = 0$$


$$I_1 = 2.43A$$

I₂ current flowing the '1Ω' res is 2.43A.

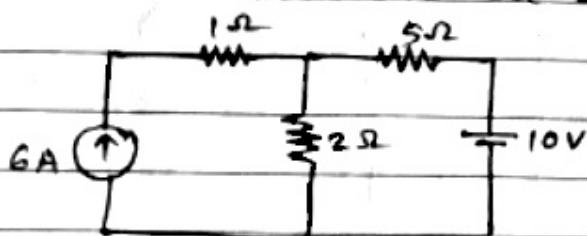
7.2 By mesh analysis method, find current through 2Ω resistor in the ckt shown.



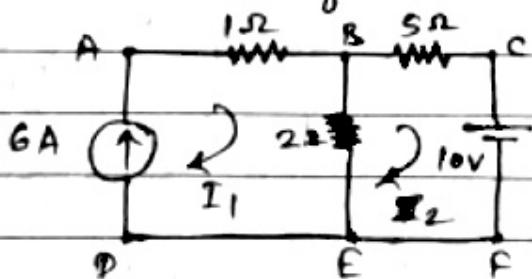Naming the nodes and assigning separate mesh current for each mesh we get



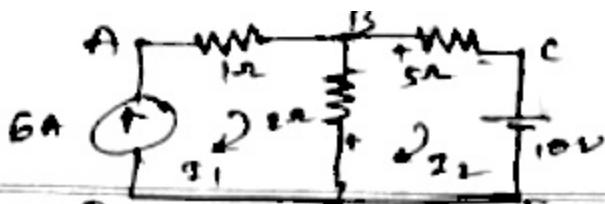If a current source exists in any mesh of a ckt KVL cannot be applied to such mesh.



In the given circuit, current source of 6A is present in mesh ABCDEA, so KVL cannot be applied.

$$\therefore I_1 = 6$$

For mesh BCFFEB KVL can be applied

$$-2(I_2 - I_1) - 5I_2 - 10 = 0$$

$$2I_1 - 7I_2 = 10$$


$$2(6) - 7I_2 = 10$$

$$-7I_2 = -2$$

$$\therefore I_2 = 2/7 = 0.285 \text{ A}$$

Current flowing through resist. = $I_1 - I_2$


$$6 - 0.285 = 5.71 \text{ A}$$

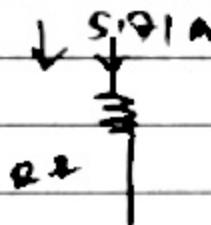

Nodal Analysis Method:

- Based on Kirchhoff's current law (KCL)
- Used to determine voltages of different nodes with respect to reference node.
- After determining node voltage, currents in all branches can be determined.
- This method is useful where no. of loops is large and so mesh analysis become lengthy.
- In this method advantage is a min. no. of eq's need to be written to determine the unknown quantities.

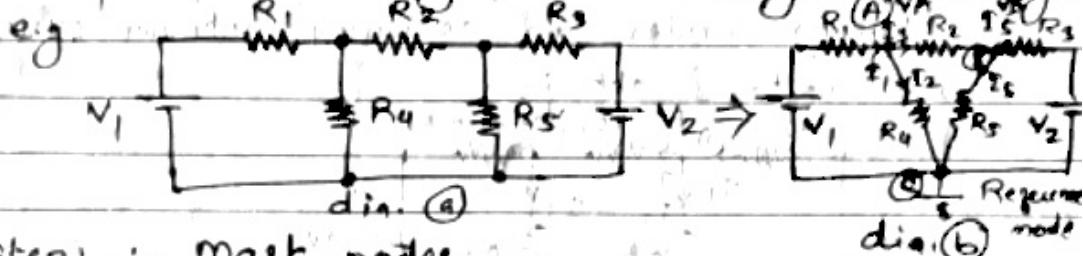Steps for solving problems using Nodal Analysis



Step 1 :- Mark nodes.

In the above circuit dia. (a) has 4 nodes

But Lower two nodes are same, so by joining them, we get only three nodes as shown in dia. (b)

Step 2 :- Select one of nodes as reference node.

For convenience, a node where max. elements are connected or max. branches are meeting is selected.

In above example, node (c) is selected as reference node.

Step 3 :- Assign the unknown potentials of all nodes w.r.t. the reference node.

In above example at node A potential V_A and at node B, potential V_B .


Step 4 :- At each node, excluding reference node, assume unknown currents and mark their direction.

Step 5: Apply KCL at each node and write eq's


In terms of node voltages. By solving eq's, determine the node voltages.

From node voltages, current in any branch can be determined.
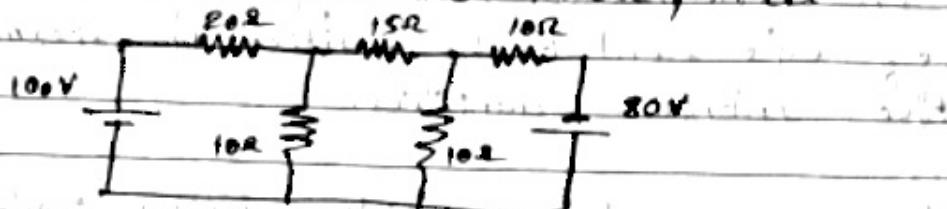
#1 Using node voltage analysis method, find the current through 15Ω resi in the foll. ckt



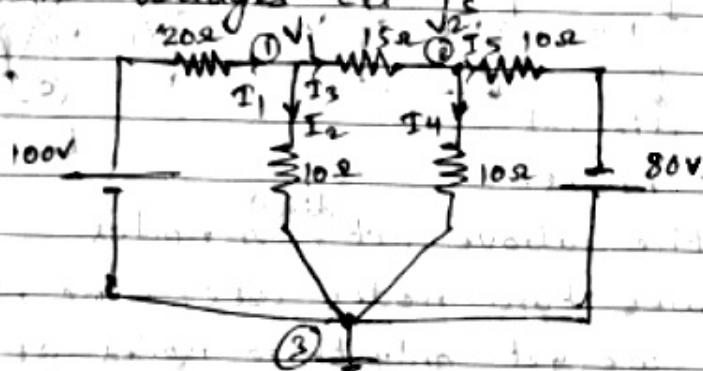Naming nodes and assigning unknown currents and voltages ckt is



Now applying KCL at node 1

$$I_1 = I_2 + I_3$$

$$\text{or } \frac{100 - V_1}{20} = \frac{V_1 - V_2}{10} + \frac{V_1 - V_2}{15}$$

$$\therefore 13V_1 - 4V_2 = 300 \quad \text{--- (1)}$$

Applying KCL at node 2

$$I_3 = I_4 + I_5$$

$$\text{or } \frac{V_1 - V_2}{15} = \frac{V_2 - 0}{10} + \frac{V_2 - (-80)}{10}$$

$$\therefore V_1 - 4V_2 = 120 \quad \text{--- (2)}$$

From eq's (1) and (2) we get


$$V_1 = 15V, V_2 = -26.25V$$

$$\text{Current through } 15\Omega \text{ resi} = I_3 = \frac{V_1 - V_2}{15} = 2.75A$$

2 Find the current thr' 2Ω and 3Ω resistances using nodal analysis in foll. circuit.



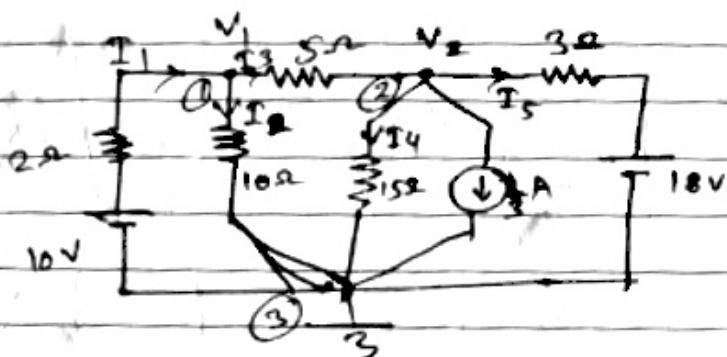Naming the nodes, assigning unknown currents & voltages to the circuit. By joining same nodes circuit will be



Applying KCL at node 1

$$T_1 = T_2 + T_3$$

$$\text{or } \frac{10 - v_1}{2} = \frac{v_1 - 0}{10} + \frac{v_1 - v_2}{5}$$

$$\text{or } 8V_1 - 2V_2 = 50 \quad \text{--- (1)}$$

Applying KCL at node 2

$$T_3 = T_4 + T_5 + \frac{1}{3}$$

$$\text{or } \alpha = \frac{V_1 - V_2}{5} = \frac{V_2 - 0}{15} + \frac{V_2 - 18}{3} + \frac{1}{3}$$

$$3v_1 - 9v_2 = -85 \quad \text{---} (2)$$


Solving eq's ① & ②

$$V_1 = 9.394 \text{ V}, V_2 = 12.576 \text{ V}$$

$$\text{Current through } 2\Omega \text{ resistor} = \frac{10 - V_1}{2} = 0.303A \uparrow, \quad V_{ER} = V_2 - 18 \\ = -1.8V \rightarrow \boxed{3}$$


Superposition Theorem:

- Linear n/w :- If current in the n/w is linearly related to voltage as per Ohm's law.
- Bilateral n/w :- Volg. - current relation is the same for the current flowing in either direction.
- This theorem is applicable for linear and bilateral n/w's.
- If there are no of sources acting simultaneously in any linear bilateral n/w, then each source acts independently of the others i.e. as if other source did not exist.
- * This theorem is stated as, in a linear n/w containing more than one source, the resultant current in any branch is the algebraic sum of the currents that would be produced by each source, acting alone, all other sources of emf being replaced by their respective internal resistances.

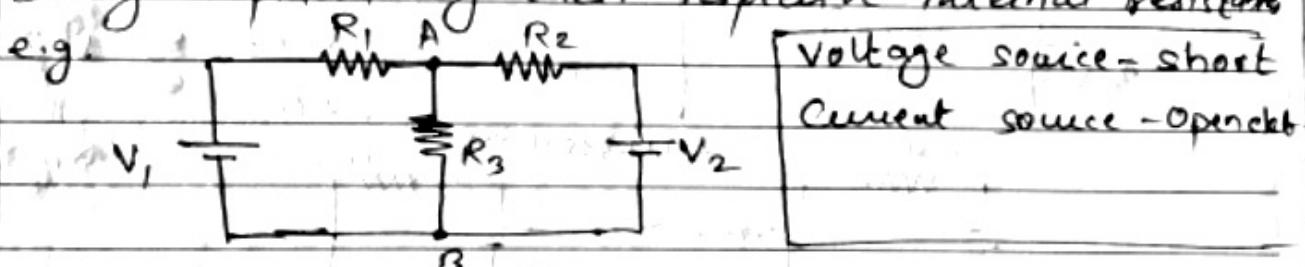


case 1: Consider source V_1 acting independently. Other sources must be replaced by internal resistances. But as internal resi. of V_2 is not given, it is assumed to be zero. So V_2 will be replaced by a short circuit, to obtain the

current thr' AB due to source V_1 alone.

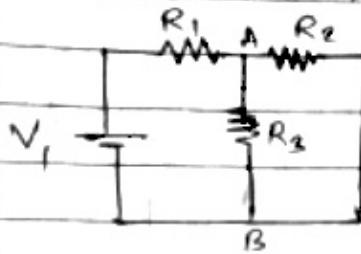

case 1 obt

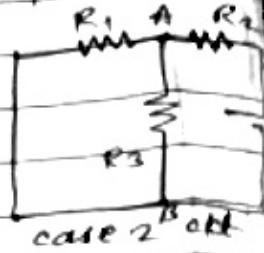


case 2 obt

Case 2 :- Consider source V_2 alone. V_1 will be replaced by a short ckt to obtain current thr' AB. using any method


case 3 :- As per superposition th, the resultant current thr' branch AB is the sum of the currents thr' branch AB produced by each source acting independently.
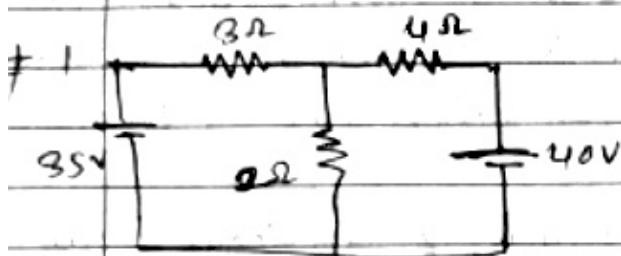
$$\therefore I_{AB} = I_{AB} \text{ due to } V_1 + I_{AB} \text{ due to } V_2$$



In the ckt shown,
find the different
branch currents by
using Superposition th

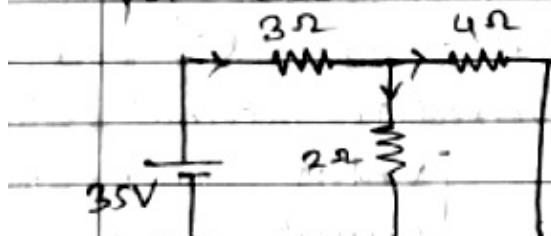
(1) Considering only 35V supply and replacing 40V supply by short ckt. We will get
foll. ckt



In this ckt, resistors

$$2\Omega \parallel 4\Omega$$
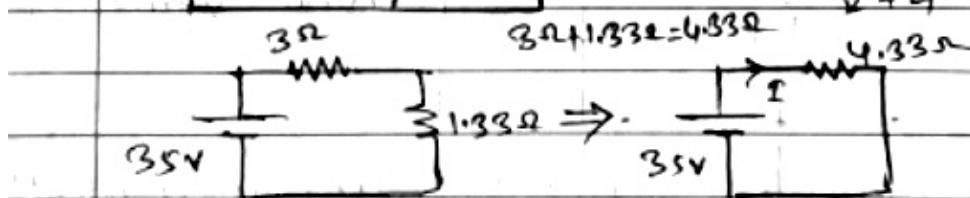
$$\therefore \frac{2 \times 4}{2+4} = \frac{8}{6} = 1.33\Omega$$



$$3\Omega + 1.33\Omega = 4.33\Omega$$

$$4.33\Omega$$


$$\therefore \text{current } I = \frac{35}{4.33} = 8.08A$$

\therefore current in $3\Omega = 8.08A \rightarrow$

$$\text{current in } 4\Omega = 8.08 \times \frac{2}{2+4} = 2.69A \rightarrow$$

$$\text{current in } 2\Omega = I_{3\Omega} - I_{4\Omega} = 8.08 - 2.69 = 5.39A$$

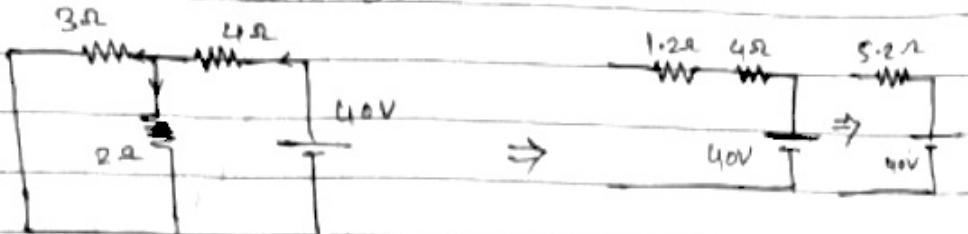Step 2: Considering 40V source acting alone,
Replacing 35V source by short circuit
ckt will be.



$$3\Omega \parallel 2\Omega = \frac{3 \times 2}{3+2} = \frac{6}{5} = 1.2\Omega$$

It will be in series with ~~the res~~.

Using Ohm's law current $I = \frac{V}{R}$

$$I = \frac{40}{5.2} = 7.69A$$

∴ current in 4Ω resist = 7.69A (\leftarrow direction).

By current division rule, current in 3Ω resist

$$I_{3\Omega} = \frac{7.69 \times 2}{3+2} = 3.08A (\leftarrow)$$

$$\text{current in } 2\Omega \text{ resist} = 7.69 - 3.08 = 4.61A (\downarrow)$$


Step 3: Total current thru all required branches is summation of currents due to source 1 & source 2.

$$\begin{aligned} \therefore I_{3\Omega}(\text{Tot.}) &= I_{3\Omega}|_{35V} + I_{3\Omega}|_{40V} \\ &= 3.08(\rightarrow) + (3.08 \times \leftarrow) \\ &= 8.08 - 3.08 \\ &= 5A. \rightarrow \end{aligned}$$


$$\begin{aligned} I_{(2\Omega)}\text{Tot.} &= I_{2\Omega}|_{35V} + I_{2\Omega}|_{40V} \\ &= 4.61(\downarrow) + 4.61(\downarrow) \\ &= 10A (\downarrow) \end{aligned}$$

$$\begin{aligned} I_{(4\Omega)}\text{Tot.} &= I_{4\Omega}|_{35V} + I_{4\Omega}|_{40V} \\ &= 2.69(\rightarrow) + 7.69(\leftarrow) \\ &= 2.69 - 7.69 = -5A \text{ or } 5A(\leftarrow) \end{aligned}$$

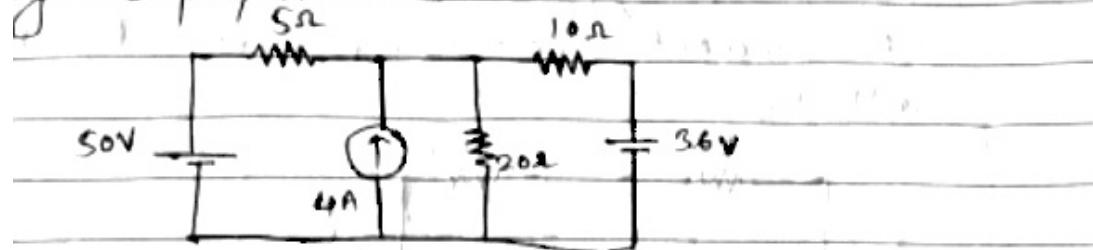Determine the current in '5Ω res' in the given
by superposition th.



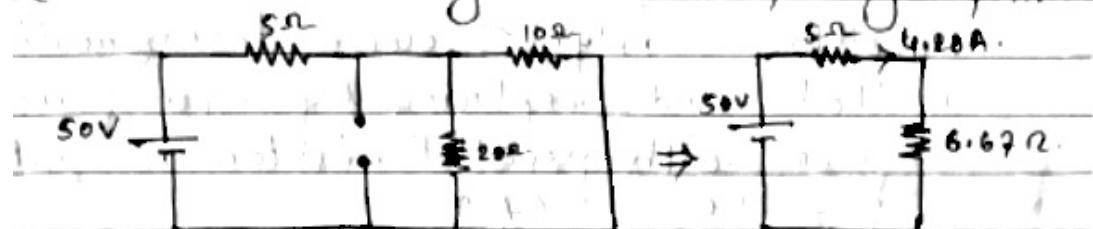Step 1 :- Consider 50V source acting alone,
and replacing 4A source by open circuit
& 36V source by short ckt, we get foll. ckt




In this fig. resistors $20\Omega \parallel 10\Omega$,


$$\therefore \frac{20 \times 10}{20 + 10} = \frac{200}{30} = 6.67\Omega$$

$$\text{Current in '5Ω res'} = I_{5\Omega} = \frac{50}{11.67} = 4.28A \rightarrow$$

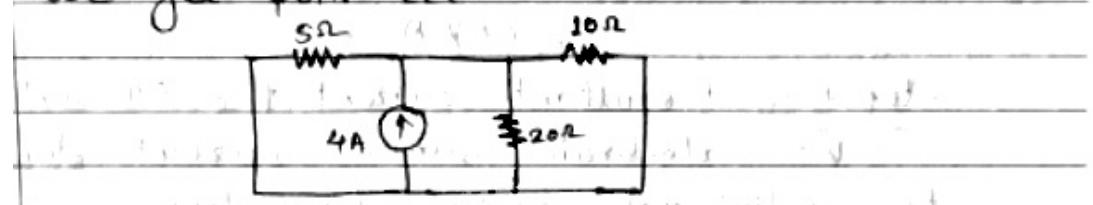Step 2 :- Considering 4A source acting alone,
replaced 50V & 36V volg. sources by short ckt
we get foll. ckt



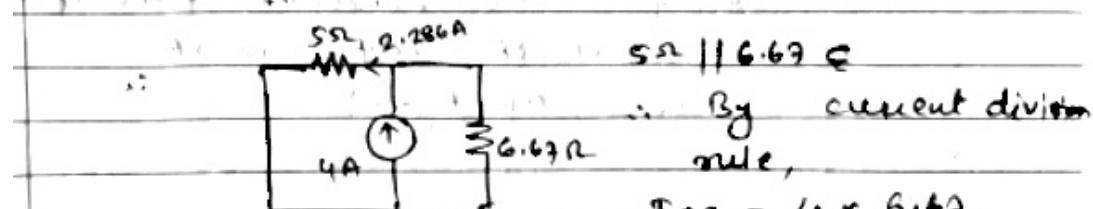
$$\text{In this dia. resistors } 20\Omega \parallel 10\Omega \quad \frac{20 \times 10}{20 + 10} = 6.67\Omega$$



\therefore By current division rule,


$$I_{5\Omega} = 4 \times \frac{6.67}{5+6.67} \\ = 2.286A \leftarrow$$

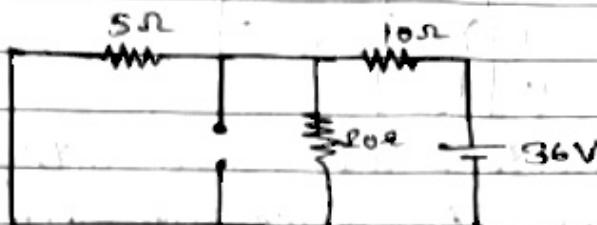Step 3 : Considering ~~36V~~ source acting alone, replacing ~~36V~~ by short ckt and 4A current source by open ckt, ckt will be



For 36V volg. source with 10Ω series resistor, applying source transformation method and replacing by equi current source with parallel resistor. we get
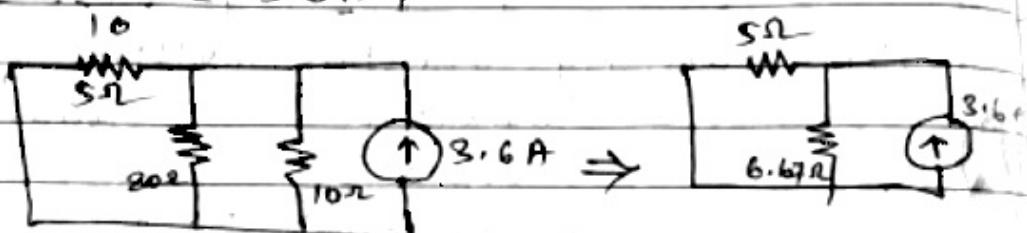
$$I = \frac{36}{10} = 3.6 \text{ A} \uparrow$$



$$20\Omega / 10\Omega = 6.67\Omega$$

$I_{5\Omega}$ using current division rule

$$I_{5\Omega} = \frac{3.6 \times 6.67}{5 + 6.67}$$

$$= 2.057 \text{ A} \leftarrow$$

Step 4 : Resultant current thr' 5Ω will be algebraic sum of currents due to individual sources acting alone.

$$\therefore I_{5\Omega} = 4.28(\rightarrow) + 2.286A(\leftarrow) + 2.057A(\leftarrow)$$


$$= 4.28A - 2.286A - 2.057A$$

$$= 0.063 \text{ A} (\leftarrow)$$

Thevenin's Theorem: - (French Eng M.L. Thevenin - 1883)

- It is used to simplify a complex problem and obtain the ckt. solution quickly.
- It is useful to find the current in a particular branch of a n/w as the rest of that branch is varied by keeping all other resistances and sources constant.

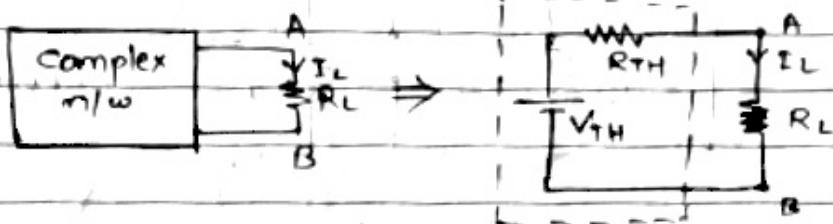
As per this theorem, any two-terminal ^{complex} n/w can be replaced by a single source of emf V_{TH} known as Thevenin Voltage in series with a single resi. R_{TH} known as Thevenin resistance.



Thevenin's Equivalent ckt.

V_{TH} is the voltage that appears across terminals A and B with Load removed. The resi. R_{TH} is the resi. obtained with load removed and looking back into the terminals A and B when all the sources in the ckt are replaced by their internal resistances.

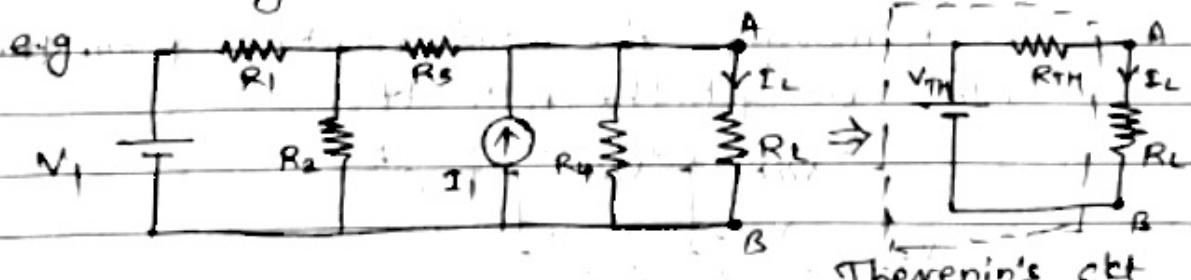
Once Thevenin's equ. ckt is obtained, current through any load R_L connected across AB can be easily obtained.



Thevenin's ckt.


V_{TH} : - Open ckt. Thevenin's Voltage

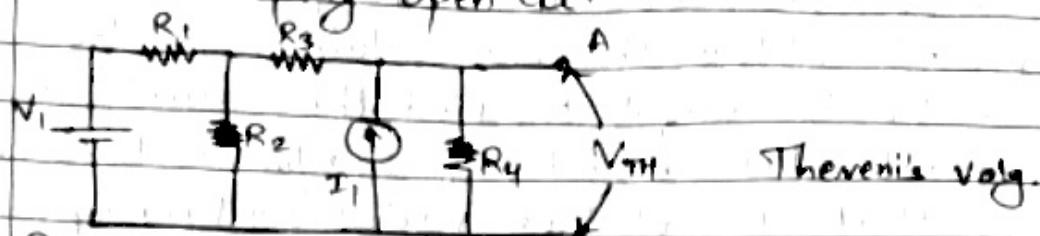- V_{TH} is calculated bet' A & B by removing R_L & keeping open ckt.




For calculating V_{TH} any method can be used.

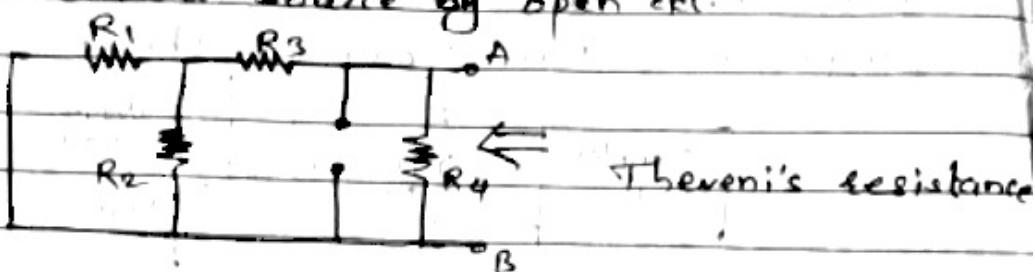- R_{TH} is equivalent resi. obtained as viewed thr' terminals A and B with R_L removed and replacing volg. source with short ckt and current source by open ckt.




$$I_L = \frac{V_{TH}}{R_L + R_{TH}}$$

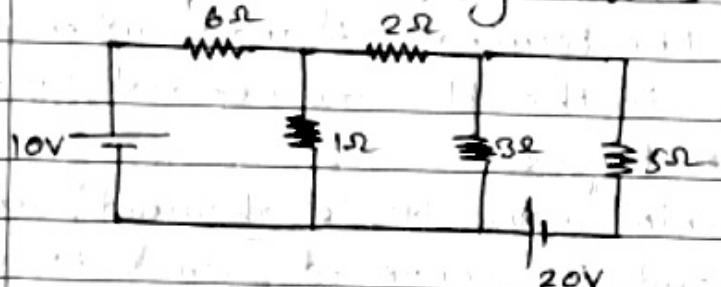- #1 Determine the current thr' 5Ω resistor in the n/w shown, by Thevenin's theorem.



Step 1 :- calculation of V_{TH}

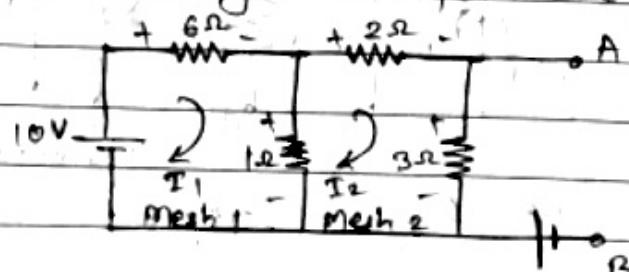Removing the Load resistance from the n/w we get the foll. ckt



Voltage across Load terminals A and B, V_{AB} is Thevenin's voltage. V_{TH} .

As shown in dotted line in dia. any path from A to B is selected. 3Ω resistor is present in the selected path and for V_{TH} calculation current through res. is required.

Using mesh analysis method, T_{22} can be calculated. Applying KVL to mesh 1:

$$10 - 6I_1 - 1(I_1 - I_2) = 0$$

$$\therefore 7I_1 - I_2 = 10 \quad \text{--- (1)}$$

Applying KVL to mesh 2

$$-2I_2 - 3I_2 - (I_2 - I_1) = 0$$

$$I_1 - 6I_2 = 0 \quad \text{--- (2)}$$

Solving (1) and (2)

$$I_2 = 0.244A$$

$$\therefore I_{22} = 0.244A \downarrow$$

$$\text{Thus } V_{TH} = V_{AB}$$


$$= 20 + 3I_2$$

$$= 20 + 3(0.244)$$

$$= 20.732V$$

Step 2 :- Calculation of R_{TH}

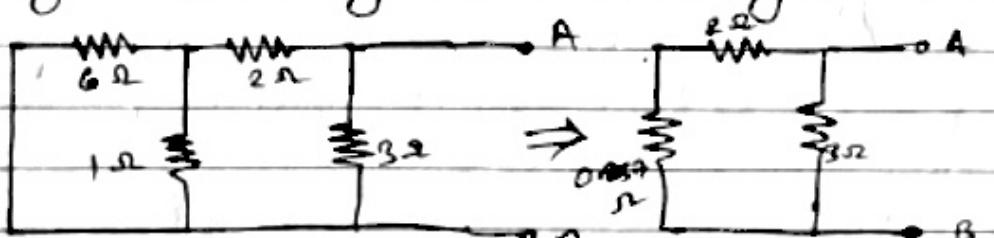Removing the load resi from net and replacing the vol. sources by short ckt we get




Equivalent resi across load terminals A and B is called Thevenin's res. R_{TH} .

$$6\Omega // 1\Omega = \frac{6 \times 1}{6+1} = \frac{6}{7} = 0.857\Omega$$

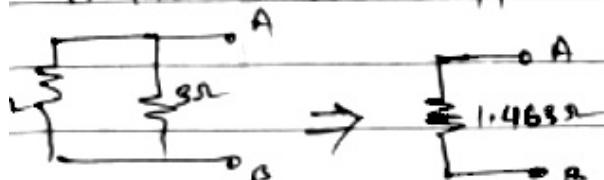
0.857Ω is in series with $2\Omega = 2.857\Omega$

$$\therefore \text{Now } 2.857\Omega // 3\Omega = \frac{2.857 \times 3}{2.857 + 3} = 1.463\Omega$$



$$iii) R_{TH} = R_{AB} = 1.463 \Omega$$

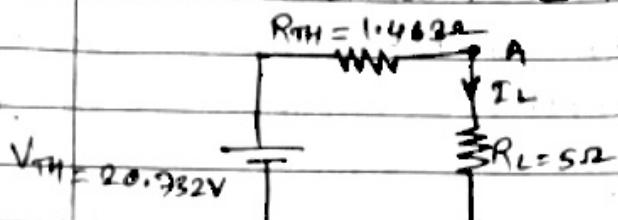Step 3 :- Calculation of Load current
with V_{TH} & R_{TH} , Thevenin's equiv. ckt
can be drawn as :




Using Ohm's law:

$$I_L = \frac{V_{TH}}{R_L + R_{TH}}$$

$$= \frac{20.932}{5 + 1.463}$$

$$I_L = 3.21A$$

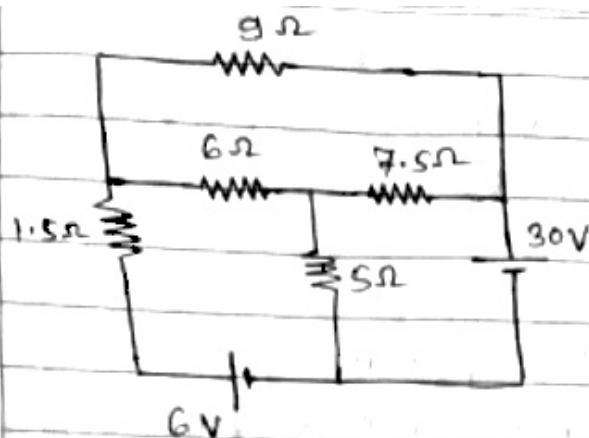

Determine the current thr' 1.5Ω resistor in the network shown in fig. using Thevenin's theorem.

1.5Ω resistor is Load resistor R_L . Its terminals will be named as A & B as load terminals.


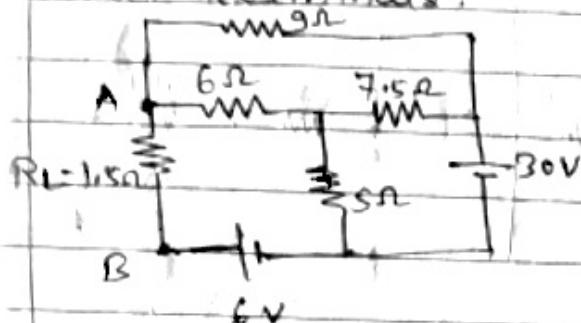


Diagram showing 1.5Ω res' as R_L at load terminals A & B

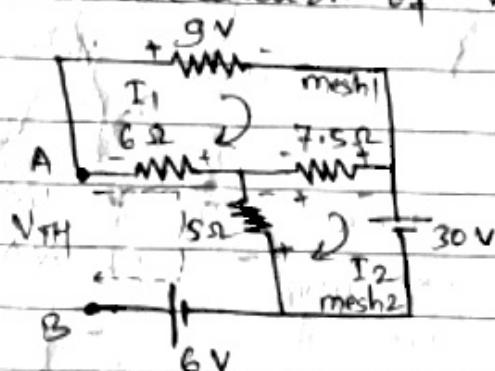Step 1 :- Calculation of V_{TH} (Removing R_L from circuit)



Voltage across A & B will be V_{TH} (Thevenin's volt.)

Using mesh analysis method, $V_{AB} = V_{TH}$ can be calculated.

Applying KVL to mesh 1

$$-9I_1 - 7.5(I_1 - I_2) - 6I_1 = 0$$

$$\therefore -22.5I_1 + 7.5I_2 = 0 \quad \text{--- (1)}$$

Applying KVL to mesh 2

$$-7.5(I_2 - I_1) - 30 - 5I_2 = 0$$

$$\therefore 7.5I_1 - 12.5I_2 = 30 \quad \text{--- (2)}$$

Solving eq's (1) + (2) we get

$I_1 = -1 \text{ Amp}$
$I_2 = -3 \text{ Amp}$

$$\therefore V_{AB} = V_{TH}$$

$$= -6 - 5I_2 - 6I_1$$


$$= -6 (-5x-3) - 6(-1)$$

$$V_{TH} = 15V$$

Step 2 :- Calculation of R_{TH}


Remove R_L & replace voltage sources by short circuit.

Now, ckt will be

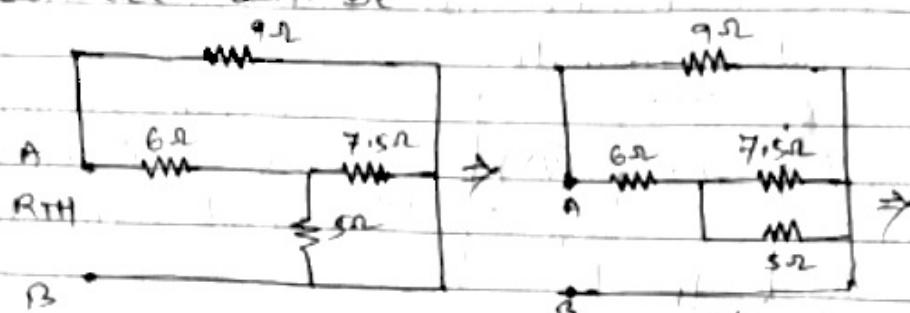

$$7.5\Omega // 5\Omega$$
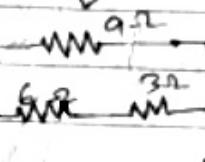
$$\frac{7.5 \times 5}{7.5 + 5} = 3\Omega$$




$$6 + 3\Omega = 9\Omega$$

$$R_{TH} = \frac{9\Omega // 9\Omega}{9+9} = \frac{9+9}{18} = 4.5\Omega$$

$$9\Omega // 9\Omega$$


$$\frac{9+9}{18} = 4.5\Omega$$

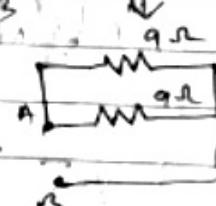

Step 3 :- Calculation of load current

Thevenin's equivalent ckt will be now

$$R_{TH} = 4.5\Omega$$

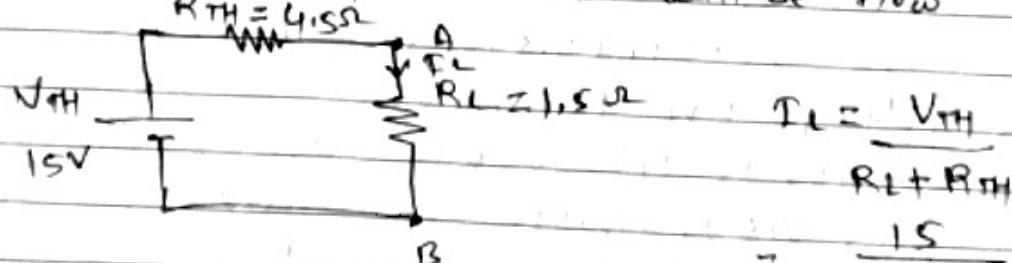


$$I_L = \frac{V_{TH}}{R_L + R_{TH}}$$

$$= \frac{15}{1.5 + 4.5} = 2.5A$$

$$= 2.5A \downarrow$$

\therefore Current flowing through 1.5Ω is $2.5A \downarrow$

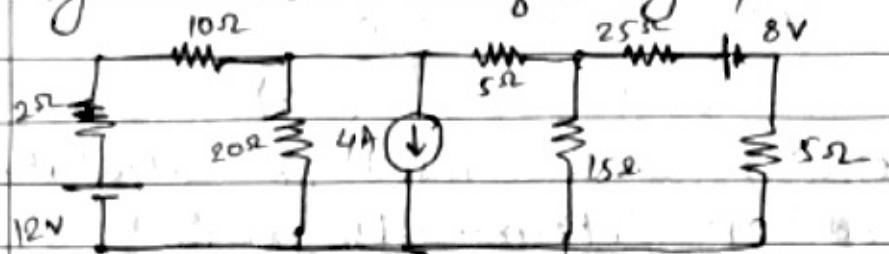
#2 Using Thevenin's theorem, obtain the power drawn by 20Ω res. in the following net.




Power across 20Ω res. is $P_{20\Omega} = I_{20\Omega}^2 \times 20$.

so, we can assume current the 20Ω res. as load current and 20Ω res. as load resistor.

Its terminals can be named as A & B.

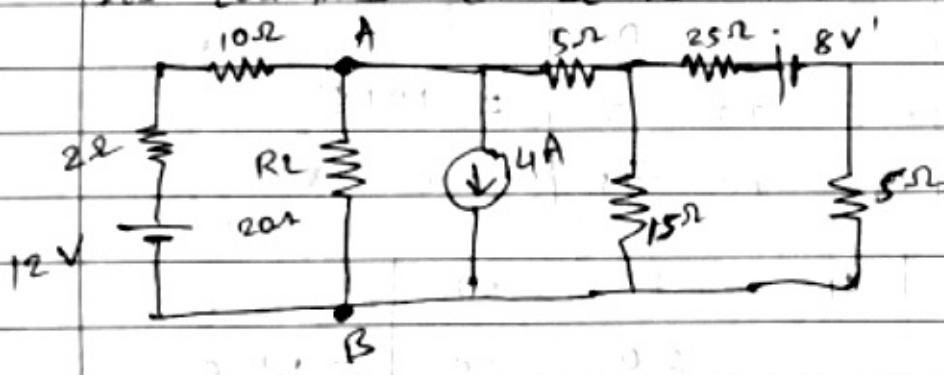

Step I : Calculation of V_{TH}

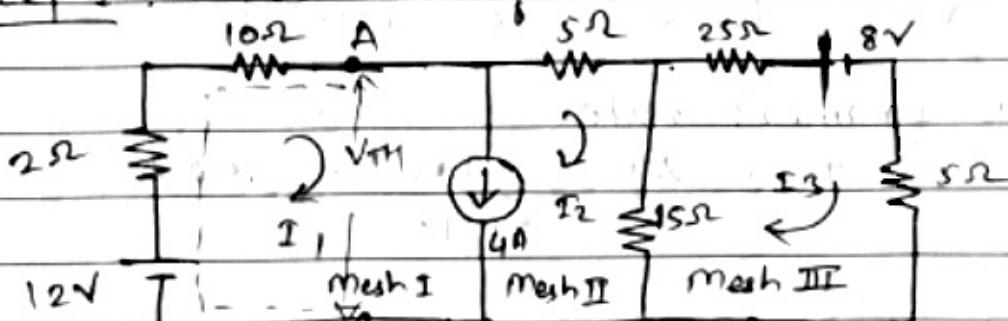

$\text{load } 20\Omega \text{ from A \& B}$

Removing or open circuiting at terminals A & B we get above circuit.

Volg. bet A & B is V_{TH} .

Mesh I and Mesh II are as shown in fig.

$$\therefore I_1 - I_2 = 4 \quad \text{--- (1)}$$

Now by applying KVL to the supermesh we get

$$12 - 10I_1 - 5I_2 - 15(I_2 - I_3) - 2I_1 = 0$$

$$\text{or } -12I_1 - 20I_2 + 15I_3 = -12 \quad \text{--- (2)}$$

Now by applying KVL to mesh III

$$-8 - 25I_3 - 5I_3 - 15(I_3 - I_2) = 0$$

$$\text{or } 15I_2 - 45I_3 = 8 \quad \text{--- (3)}$$

Eqs (1), (2) & (3) can be used to calculate I_1 by method of determinants as:

$$\begin{vmatrix} 1 & -1 & 0 \\ -12 & -20 & 15 \\ 0 & 15 & -45 \end{vmatrix} \begin{vmatrix} I_1 \\ I_2 \\ I_3 \end{vmatrix} = \begin{vmatrix} 4 \\ -12 \\ 8 \end{vmatrix}$$

$$\text{so } \Delta = \begin{vmatrix} 1 & -1 & 0 \\ -12 & -20 & 15 \\ 0 & 15 & -45 \end{vmatrix} = 1215$$

$$A_1 = \begin{vmatrix} 4 & -1 & 0 \\ -20 & 15 & \\ 8 & 15 & -45 \end{vmatrix} = 3120$$

By Cramer's rule

$$I_1 = \frac{A_1}{\Delta} = \frac{3120}{1215} = 2.57 \text{ A}$$

$$V_{TH} = V_{AB}$$


$$= 12 - 2I_1 - 10I_1$$

$$= 12 - 2(2.57) - 10(2.57)$$


$$V_{TH} = -18.84 \text{ V}$$

Step 2 :- Calculation of R_{TH}

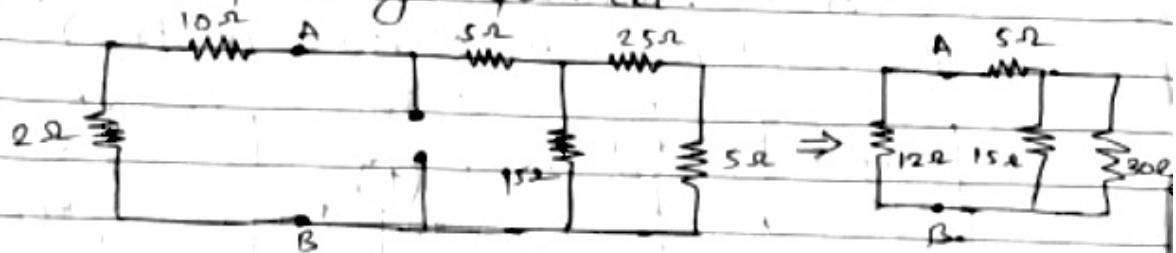Removing R_L from A+B and replacing volg source by short ckt and current source by open ckt, we get foll. ckt:



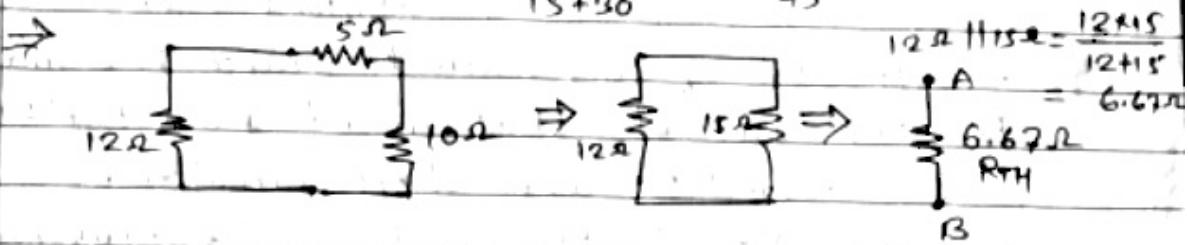
$$15\Omega \parallel 30\Omega = \frac{15 \times 30}{15+30} = \frac{450}{45} = 10\Omega$$



$$\therefore R_{TH} = 6.67\Omega$$

Step 3 :- Calculation of load current:

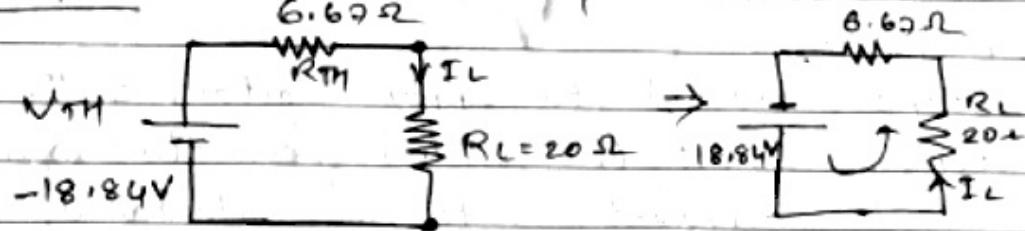

Using Ohm's Law

$$I_L = \frac{V_{TH}}{R_{TH} + R_L} = \frac{18.84}{6.67 + 20} = 0.706 \text{ A} (\uparrow)$$

\therefore Power drawn by 20Ω Load res' will be


$$P_{20\Omega} = I_{20\Omega}^2 \times 20$$

$$= (0.706)^2 \times 20$$

$P_{20\Omega} = 9.97 \text{ Wattle}$

Norton's Theorem:-

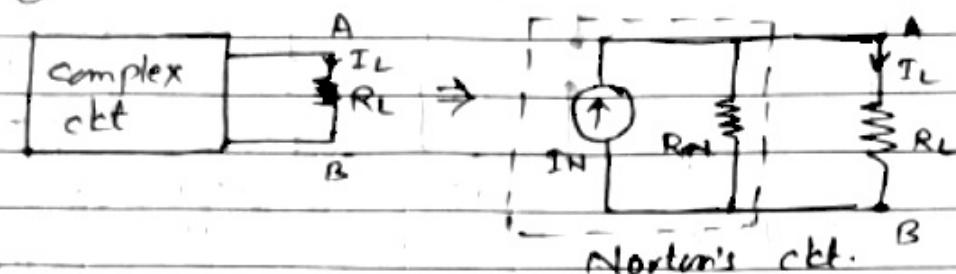- Any two-terminal n/w can be replaced by a single current source of magnitude I_N (Norton's current) in parallel with a single resistance R_N (Norton's resistance)



- Q/P I_N of the current source is equal to the current that would flow the AB when A and B are short circuited.
- Resi. R_N is the resi. of the n/w measured bet A and B with the load removed and replacing the source with their internal resistances.

Steps involved to apply Norton's thm.

Step 1: Short the branch resi. thi' which current is to be calculated.


Step 2: Obtain the current thi' the short circuited branch using any method.
This current is Norton's current I_N .

Step 3: Calculate R_N as viewed thi' the two terminals of the branch from which current is to be calculated by removing that branch resi. & replacing all sources by their internal resistances.

Step 4: Draw Norton's equiv. ckt


Step 5: Reconnect the branch resi. R_L & calculate $I_L = I_N \frac{R_N}{R_L + R_N}$
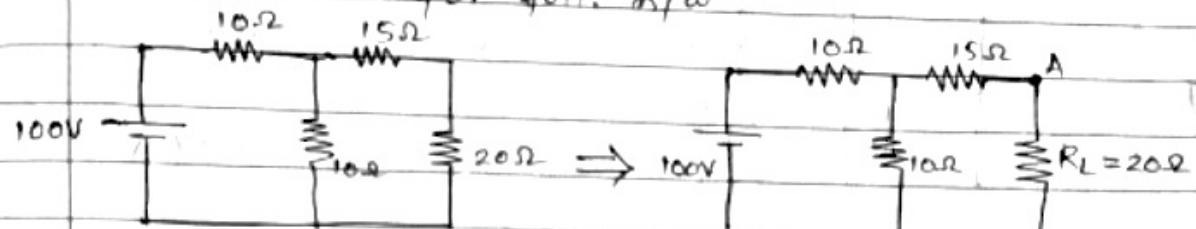
#1. Using Norton's theorem method, find the current in 20Ω res for foll. n/w



Step 1 : Calculation of I_N

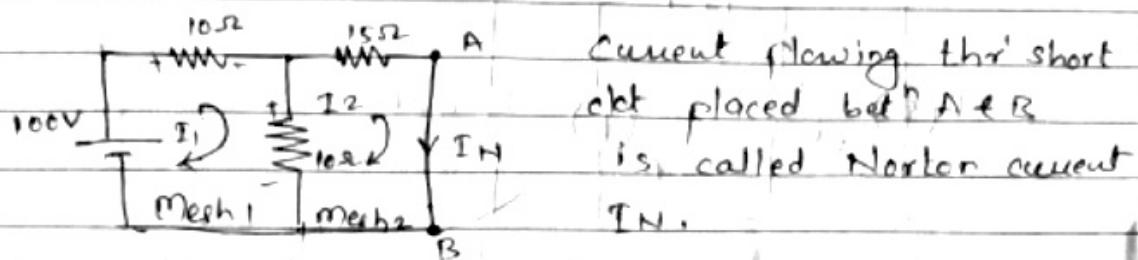Removing R_L & replacing by short ckt, n/w will be



By mesh analysis

Applying KVL to mesh 1

$$100 - 10I_1 - 10(I_1 - I_2) = 0$$

$$\text{or } -20I_1 + 10I_2 = -100 \quad \textcircled{1}$$

Applying KVL to mesh 2

$$-10(I_2 - I_1) - 15I_2 = 0$$

$$\text{or } 10I_1 - 25I_2 = 0 \quad \textcircled{2}$$

Solving eq's $\textcircled{1}$ and $\textcircled{2}$


$$I_2 = 2.5A.$$

$$\therefore I_N = 2.5A \downarrow$$

Step 2 : Calculation of R_N


Removing R_L from n/w & keeping open dt.

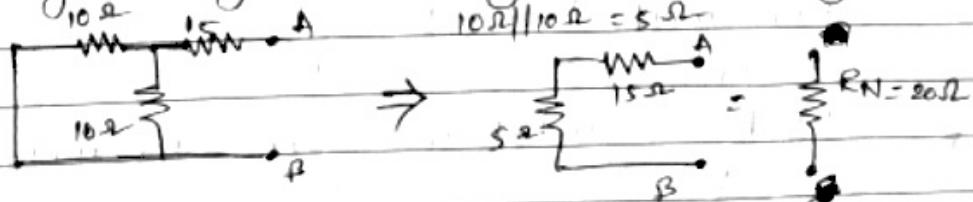Replacing voltage source by short ckt, we get n/w:



Step 3:- Calculation of load current

Norton's equivalent circuit is

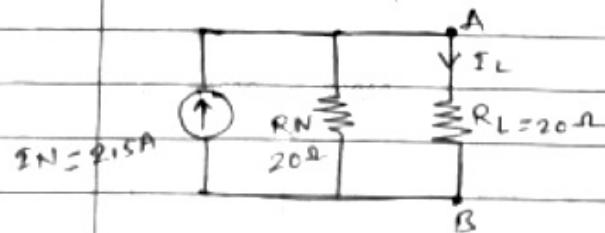


By current division rule


$$I_L = I_{20\Omega} = \frac{2.5 \times 2}{2+2}$$

$$= 1.25 \text{ A} \downarrow$$

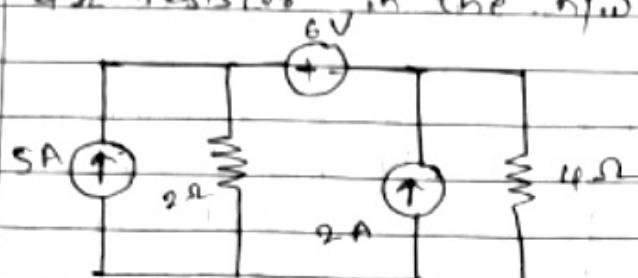2 By Norton's theorem, find the current in 4Ω resistor in the network shown.




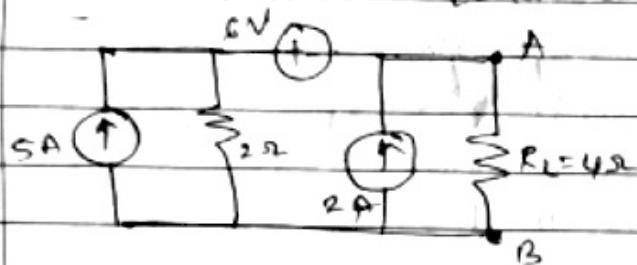4Ω resistor is load resi" R_L , It's terminals A & B will be load terminals.



Step 1 Calculation of I_N

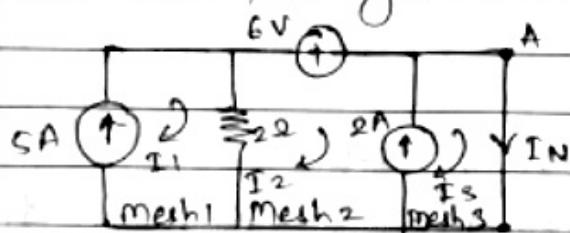Remove load resistance & short circut the load terminals, we get



I_N can be calculated by mesh analysis method:
For mesh 1

$$I_1 = 5A \quad \text{--- (1)}$$

Mesh 2 and Mesh 3 are supermesh.

$$I_3 - I_2 = 2 \quad \text{--- (2)}$$

By applying KVL to the supermesh we get

$$-6 - 2(I_2 - I_1) = 0 \quad \text{--- (3)}$$

$$0 + -2I_1 - 2I_2 = 6 = -I_1 - I_2 = 3 \quad \text{--- (3)}$$


Solving eq's ①, ② & ③ we get

$$I_3 = 4A$$


$$\therefore I_{TH} = 4A \downarrow$$

Step 2 Calculation of R_H

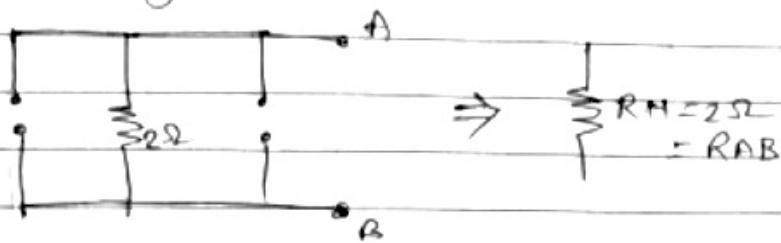Removing load resi from A + B & replacing volt. source by short ckt and current sources by open ccts we get foll. nw



Step 3 Calculation of load current

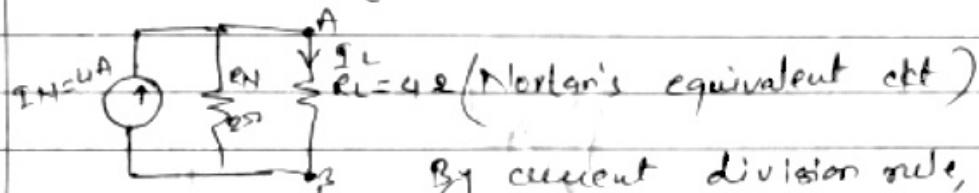

By current division rule,

$$I_L = I_{4A} = 4 \times \frac{2}{2+4}$$


$$= 1.33A \downarrow$$

Maximum Power Transfer Theorem

Transfer of max. power from a source to load is required.

Theorem:

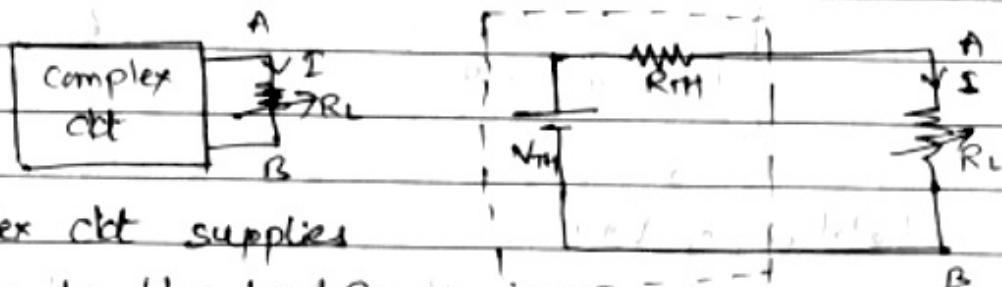In dc cts, max. power is transferred from a source to a load when the load resistance is made equal to the equivalent res. of the n/w as viewed from the load terminals, with load removed and replacing all sources with their internal resistances.



Complex ckt supplies power to the load R_L
ckt enclosed in box

Thevenin's circuit

can be replaced by Thevenin's eq^t ckt consisting of single source of emf V_{TH} (Thevenin voltage) in series with a single res. R_{TH} , ~~the res. measured bet' terminals A and B~~ with R_L removed and replacing the sources with their internal resistances.

As per Max. Power Transfer theorem, max. power will be transferred from the ckt to the load when R_L is made equal to R_{TH} ($R_L = R_{TH}$)

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} \text{ watts}$$


$$P = \frac{V_{TH}^2}{R_L + R_{TH}} R_L$$

$$(R_L + R_{TH})^2$$

when $R_L = R_{TH}$ $P = P_{max}$

$$\therefore P_{max} = \frac{V_{TH}^2 R_{TH}}{(R_L + R_{TH})^2} = \frac{V_{TH}^2}{4R_{TH}} W$$

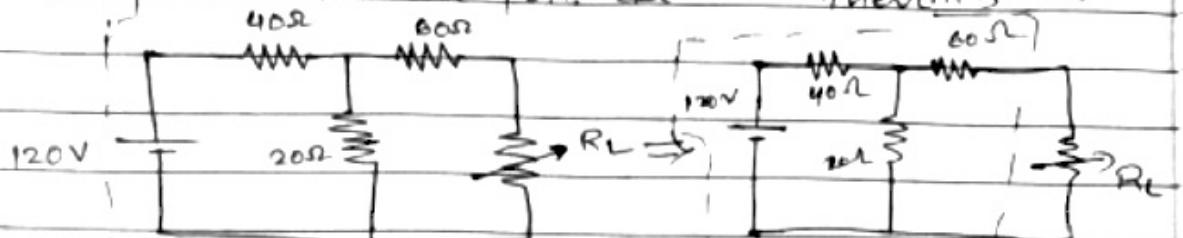
1 Calculate the value of R_L so that it will absorb the max. power and find out the max. power in the foll. ckt. Thevenin's ckt.



Step 1 Calculation of R_{TH}

Removing load resi. from
nw & replacing volg. source
by short ckt.

So nw becomes:

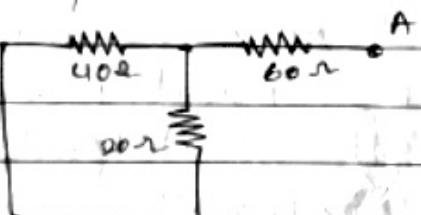

$$40/120 = \frac{40 \times 20}{40+20} = \frac{800}{60} = 13.33\Omega$$

$$= 13.33\Omega$$

13.33Ω in series with


$$60\Omega = 13.33 + 60$$

$$= 73.33\Omega$$

$$\boxed{R_{TH} = 73.33\Omega}$$

Step 2 : Calculation of V_{TH}

Removing R_L from the nw, we will get

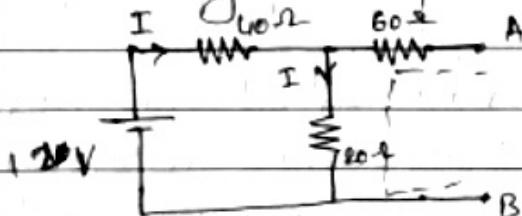

Volg. across terminals A + B will be Thevenin's volg. V_{TH} . To calculate V_{AB} , the selected path from A to B is marked by dotted line as shown in the dia. As this path contains 20Ω resi, current thro' this res. is required.

Using Ohm's law, circuit current

$$I = \frac{120}{40+20} = 2A$$

$$\therefore V_{TH} = V_{AB} = (20 \times 2) + (60 \times 0) = 40V$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$


$$V_{TH} = 40V$$

$$R_{TH} = 7.833\Omega$$

$$= \frac{(40)^2}{4(7.833)}$$

$$P_{max} = 5.45W$$

2

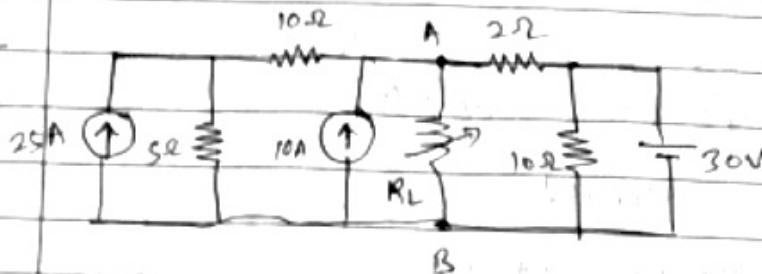


Determine the max. power delivered to R_L .


Step 1 :- Calculation of V_{TH}

- Removing R_L & making open circuit at load terminals A & B.

- Resultant circuit is :

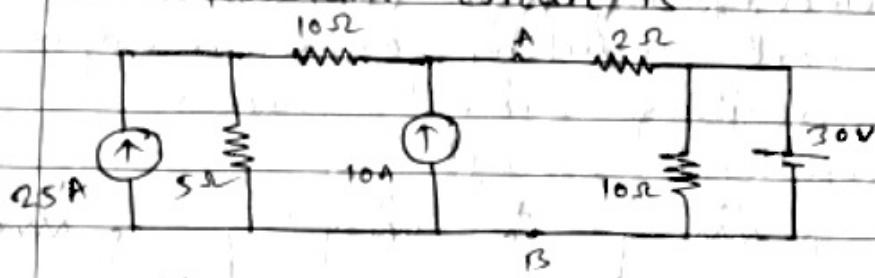

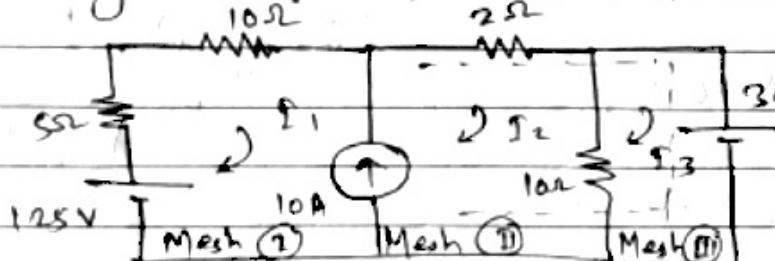Converting 25A, 5Ω current source into equiv. voltage source, resultant ckt is



Selected path from A to B is marked by

from above dia. mesh (I) + mesh (II) dotted line for V_{TH} calcul. are forming Supermesh.

$$\therefore I_2 - I_1 = 10 \quad \text{--- (1)}$$

Applying KVL to supermesh we get i's as
 $+125 - 5I_1 - 10I_1 - 2I_2 - 10(I_2 - I_3) = 0$

Simplifying and rearranging eqⁿ.

$$-15I_1 - 12I_2 + 10I_3 = -125 \quad \text{--- (2)}$$

Applying KVL to mesh (1)

$$-10(I_3 - I_2) - 30 = 0$$

$$-10I_3 + 10I_2 = 30$$

$$\therefore I_2 - I_3 = 3 \quad \text{--- (3)}$$

Solving eqⁿ's (1), (2) and (3)

$$I_2 = 14.41 \text{ A}$$

$$V_{AB} = V_{TH} = 30 + I_2(2\Omega)$$


$$= 30 + 14.41(2)$$

$$\boxed{V_{TH} = 58.82 \text{ V}}$$


Step 2 :- Calculation of R_{TH}

- Removing R_L from load terminal A & B
- Short circuiting voltage source & open circuiting current sources.

Resultant circuit is

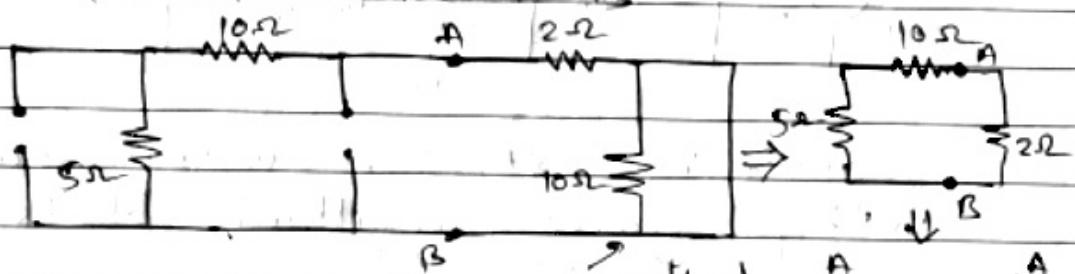

$$\boxed{R_{TH} = 1.76 \Omega}$$

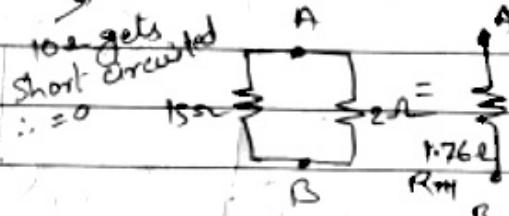

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

$$= \frac{(58.82)^2}{4 \times (1.76)}$$

$$\boxed{P_{max} = 491.45 \text{ W}}$$