

Test -2: Solution

Max. Marks: 40




Class: FY B.Tech

Branch: MECH/IT/COMP

Name of the Course: Elements of Electrical and Electronics Engineering

Duration: 1hr.30 min

Semester: I

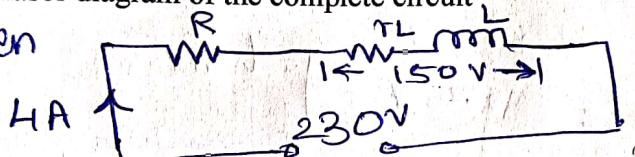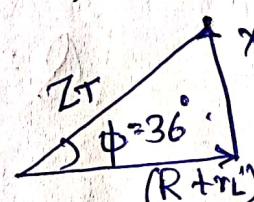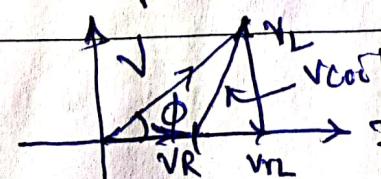Q. No.		Mark Distri
Q. 1	<p>When a resistor and a choke coil in series are connected across a 230V, 50Hz AC supply. The current of magnitude 4A and lagging behind supply voltage by 36° flows. If the voltage across the coil is 150V, find</p> <ol style="list-style-type: none"> Value of resistor Draw impedance triangle of the complete circuit Resistance of choke coil Inductance of choke coil Draw the phasor diagram of the complete circuit <p><u>Soln:</u> Given</p>  <p>$\phi = 36^\circ$</p> <p>\rightarrow Total impedance</p> $ Z_T = \frac{230}{4} = 57.3 \Omega$ $Z_T^2 = (R + r_L)^2 + X_L^2 \Rightarrow (57.3)^2 = (R + r_L)^2 + X_L^2 \quad \text{eqn. ①}$ $\rightarrow Z_{coil} = \frac{150}{4} = 37.5 \Omega$ $Z_{coil}^2 = r_L^2 + X_L^2 \Rightarrow (37.5)^2 = r_L^2 + X_L^2 \quad \text{eqn. ②}$ <p>\rightarrow Impedance triangle</p>  $(R + r_L) = Z_T \cos \phi = 57.3 \cos 36^\circ = 46.36 \Omega$ $\rightarrow (R + r_L)^2 = (57.3)^2 - (46.36)^2$ $\rightarrow r_L = \sqrt{(57.3)^2 - (46.36)^2} = 33.67 \Omega$ $\therefore L = \frac{33.67}{2\pi \times 50} = 0.107 H \quad \text{eqn. ③}$ $\rightarrow \text{From eqn. ① } r_L^2 = (37.5)^2 - (33.67)^2 = 16.51 \Omega$ $\rightarrow R + r_L = 46.36 \Omega$ $\therefore R = 29.85 \Omega$ <p><u>phasor diagram</u></p> 	10

Q. 2 Solve Any two of the following.

- (a) Two impedances $(12+j16)\Omega$ and $(10-j20)\Omega$ are connected in parallel across 230 V, 50Hz supply. Find 1. Power factor 2. Active Power
3. Reactive Power 4. Apparent Power

10

5

Soln:

$$Z_1 = 12 + j16, \quad Y_1 = \frac{1}{Z_1} = \frac{1}{12 + j16} = 0.03 - j0.04$$

$$Z_2 = 10 - j20, \quad Y_2 = \frac{1}{Z_2} = 0.02 + j0.04$$

$$Y = Y_1 + Y_2 = 0.05 - j0$$

$$Z = \frac{1}{Y} = 20 \angle 0^\circ, \quad \therefore \phi = 0^\circ$$

$$\rightarrow \therefore \text{power factor} = \cos \phi = \cos 0^\circ = 1$$

$$I = \frac{230V}{20\Omega} = 11.5A$$

$$\rightarrow \text{Active power } P = VI \cos \phi = 230 \times 11.5 \times 1$$

$$P = 2645W$$

$$\rightarrow \text{Reactive power } Q = VI \sin \phi = 230 \times 11.5 \times 0$$

$$Q = 0 \text{ VAR}$$


$$\rightarrow \text{Apparent power } S = VI = 2645W$$

$$= 230 \times 11.5$$

$$= 2645 \text{ VA}$$

(b) A coil having resistance of $47\ \Omega$ and an inductance of 0.5H is connected in series with a $10\mu\text{F}$ capacitor to a variable frequency. An alternating voltage of 230V is applied to the circuit. At what value of the frequency will the current in the circuit be maximum? Find value of maximum current. Also find voltage across inductor and quality factor.

5

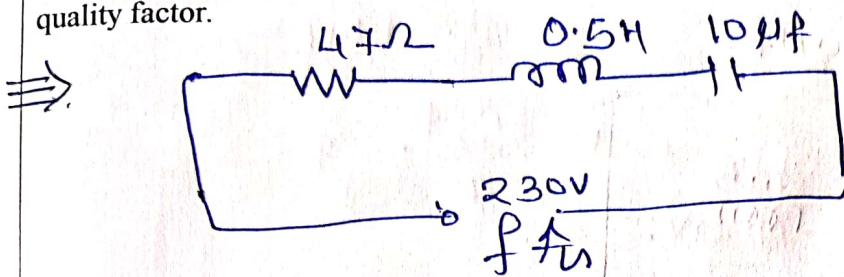

Series Resonant circuit : frequency (f_r)

$$f_r = \frac{1}{2\pi \sqrt{0.5 \times 10 \times 10^{-6}}} \quad \text{--- (1)}$$

→ Current will be maximum at freqn.
 $f_r = 71.17\text{ Hz}$

$$\rightarrow I_{\max} = \frac{230}{47} = 4.89\text{ A} \quad \text{--- (2)}$$

$$\rightarrow V_L = I_{\max} \times X_L = I_{\max} (2\pi f_r L)$$

$$= 4.89 \times (2\pi \times 71.17 \times 0.5)$$


$$\boxed{V_L = 1093.34} \quad \text{--- (3)}$$

$$\rightarrow Q = \frac{\omega_r L}{R} = \frac{2\pi \times 71.17 \times 0.5}{47} \quad \text{--- (4)}$$

$$\boxed{Q = 4.75} \quad \text{--- (5)}$$

(c) An inductive coil of resistance 33Ω and inductance of $0.5H$ is connected in parallel with $100\mu F$ capacitor to a variable frequency, $100V$ supply. Find the frequency at which total current drawn by the circuit is in phase with supply voltage. Also find the value of this current. Find the current flowing through coil and capacitor.

(5)

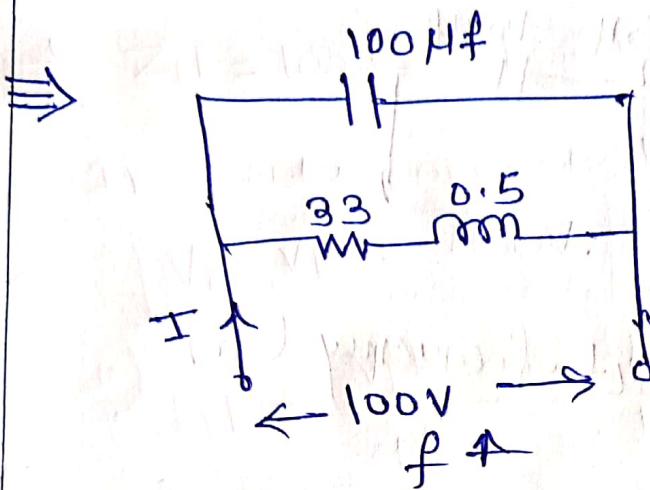

\Rightarrow At resonant freq I will be in phase with applied voltage

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{0.5 \times 100 \times 10^{-6}} - \frac{(33)^2}{(0.5)^2}}$$

$$f_r = \frac{1}{2\pi} \sqrt{20000 - 4356} =$$

$$\boxed{f_r = 19.9 \text{ Hz}}$$

$$\Rightarrow I = \frac{100}{Z_D} \quad \therefore Z_D = \frac{L}{CR} = \frac{0.5}{100 \times 10^6 \times 33} = 15.5$$

$$I = \frac{100}{15.5} = 0.66 \text{ A}$$

$$\Rightarrow I_C = \frac{V}{X_C} = \frac{100}{X_C}$$

$$X_C = \frac{1}{2\pi f r_c} = \frac{1}{2\pi \times 19.9 \times 100 \times 10^6} = 79.97 \Omega$$


$$\therefore \boxed{I_C = 1.25 \text{ A}}$$

Q. 3

Solve any two of the following


(a) Deduce the relation between phase and line quantities (voltage, current) and power in 3 phase star connected system.

5

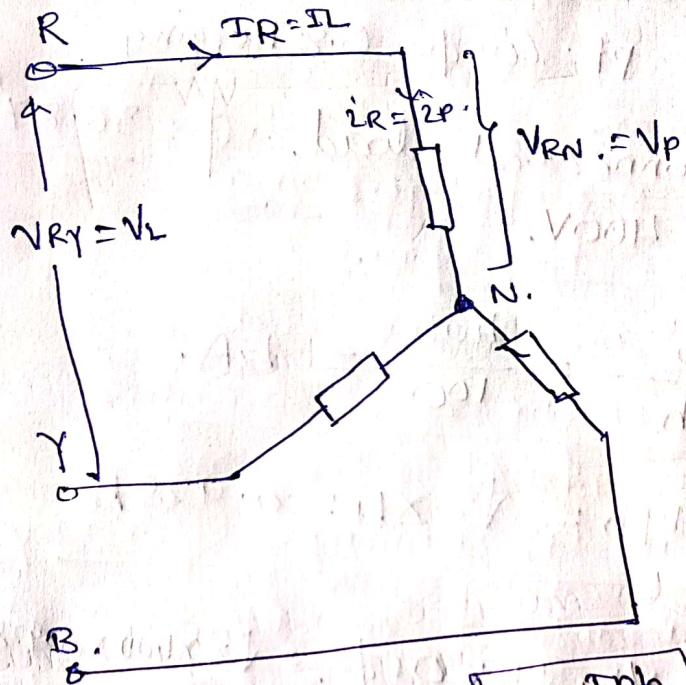

$$\Rightarrow \text{for star connection } \bar{I}_L = \bar{I}_{\text{ph}}$$

$$\text{& } \bar{V}_{RY} = \bar{V}_{RN} \neq \bar{V}_{YN}$$

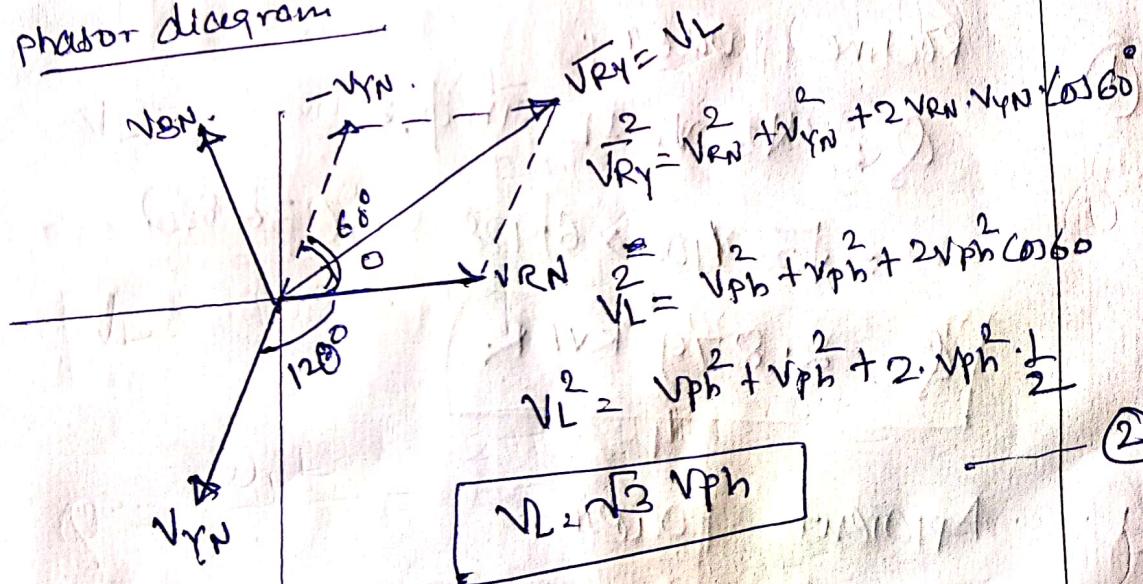Phasor diagram

$$\text{Power} = V_L \cdot I_L \cos \phi$$

$$= \sqrt{3} V_L I \cos \phi$$

(b) A balanced load of phase impedance 100Ω and power factor $0.8(\text{lag})$ is connected in delta to a 400 V , 3-phase supply.

Calculate 1. Phase and line current 2. Phase and line voltage

3. Active Power 4. Reactive Power 5. Apparent Power

(5)

$$\Rightarrow Z_{\text{ph}} = 100 \Omega \quad \text{pf} = \cos \phi = 0.8 \text{ lagging}$$

In delta connected load. $\therefore \phi = 36.87^\circ$

$$\boxed{V_L = V_{\text{ph}} = 400 \text{ V.}}$$

$$\textcircled{1} \quad I_{\text{ph}} = \frac{V_{\text{ph}}}{Z_{\text{ph}}} = \frac{400}{100} = 4 \text{ A.}$$

$$\textcircled{2} \quad I_L = \sqrt{3} I_{\text{ph}} = \sqrt{3} \times 4 = 6.928 \text{ A}$$

$$\textcircled{3} \quad \text{Active power} \\ P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 6.928 \times 0.8$$

$$\textcircled{4} \quad \boxed{P = 3.839 \text{ kW.}}$$

$\textcircled{5}$ Reactive power

$$Q = \sqrt{3} V_L I_L \sin \phi \approx$$

$$= \sqrt{3} \times 400 \times 6.928 \sin(36.87^\circ)$$

$$\boxed{Q = 2.879 \text{ kVAR.}}$$


$\textcircled{6}$ Apparent power

$$S = \sqrt{3} V_L I_L = \sqrt{3} \times 400 \times 6.928$$

$$\boxed{S = 4.799 \text{ kVA}}$$

(c) Draw neat circuit diagram showing connection of two watt meter method used to measure power in three phase delta connected inductive load. With neat phasor diagram prove that two watt meters measures total power in this 3 phase load.

(5)

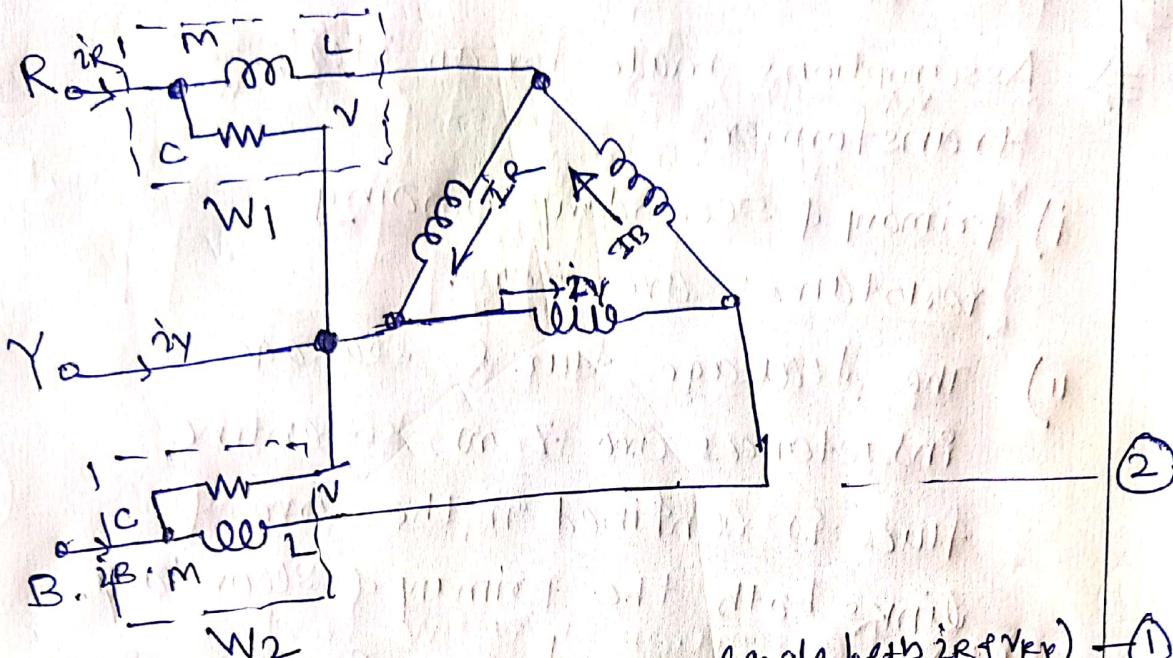

$$W_1 (\text{reading}) = V_R Y_R \times \cos(\text{angle between } i_R \text{ & } V_R) \quad (1)$$

$$W_2 (\text{reading}) = V_B Y_B \times \cos(\text{angle between } i_B \text{ & } V_B) \quad (2)$$

$$W_2 (\text{reading}) = V_B Y_B \times \cos(\text{angle between } i_B \text{ & } V_B) \quad (2)$$

In Delta Connected load

$$\bar{i}_R = \bar{i}_R - \bar{i}_B \quad (3)$$

$$\bar{i}_B = \bar{i}_B + \bar{i}_Y \quad (4)$$

$$W_1 = I_L V_L \cos(30 + \phi) \quad (5)$$

$$W_2 = I_L V_L \cos(30 - \phi) \quad (6)$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi. \quad (7)$$

(3)

Q.4

Solve any two of the following

- (a) What are assumptions made for an ideal transformer? Draw phasor diagram of an ideal transformer with no load.


(5)

\Rightarrow Assumptions made for an ideal transformer.

- i) primary & secondary winding resistances are zero.
- ii) the leakage flux & leakage inductances are zero, so entire flux is confined in the core & links both the primary & secondary.
- iii) the reluctance of core is zero so negligible mmf is required to establish flux.
- iv) the iron & core losses are zero so efficiency is 100% and regulation is 0%.

(H)

phasor diagram of ideal transformer on no load, with steps indicated in ① to ⑤.

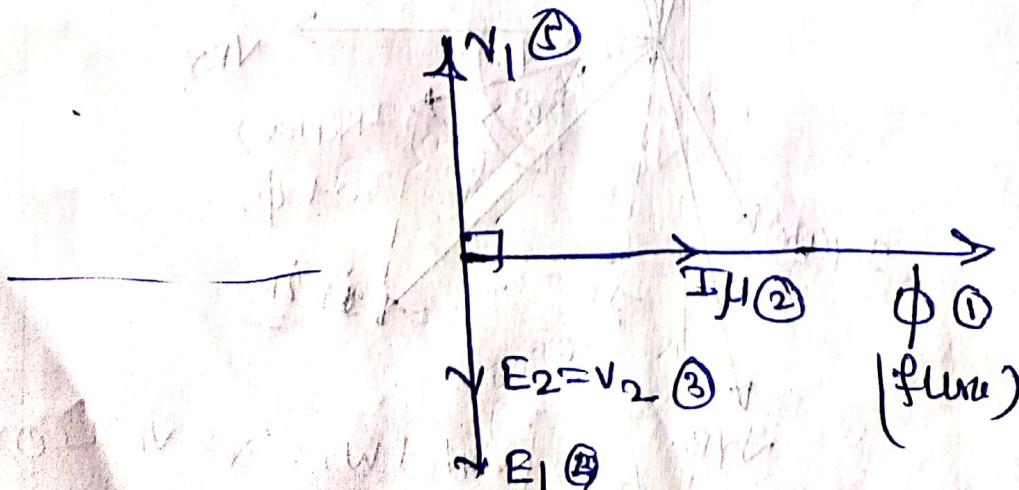① to ⑤

(b) Derive the condition for maximum efficiency of a transformer.

$$\% \text{ efficiency} = \frac{\text{Output power (watts)}}{\text{Input power (watts)}}$$

$$= \frac{\text{Output power}}{\text{Output power} + \text{losses.}}$$

$$\% \eta = \frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + W_1 + I_2^2 R_{02}}$$

Where W_1 & R_{02} represents iron loss & equivalent resistance referred to the secondary side, respectively.

$$\frac{d\eta}{dI_2} = 0.$$

$$\frac{d}{dI_2} \left[\frac{V_2 I_2 \cos \phi_2}{V_2 I_2 \cos \phi_2 + W_1 + I_2^2 R_{02}} \right] = 0$$


Solving

$$I_2^2 R_{02} = W_1$$

so Variable copper

loss is equal to constant iron loss & the condition for maximum efficiency.

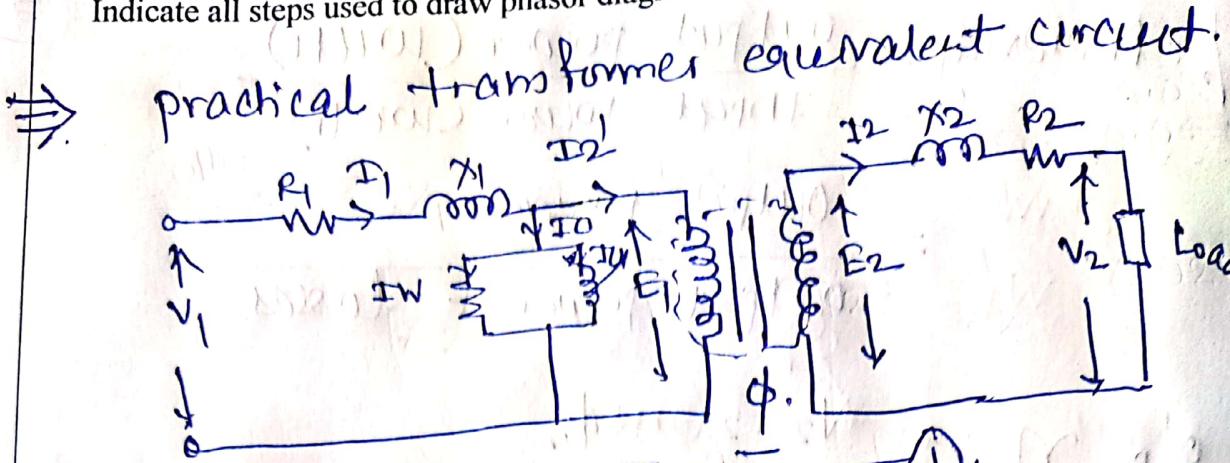(c) Draw phasor diagram of a practical transformer on inductive load.
Indicate all steps used to draw phasor diagram.



$$E_2 = I_2 R_2 + I_2 X_2 + V_2 \quad \text{--- (1)}$$

$$I_2' = -k I_2, \quad I_1 = I_2 + I_0$$

$$I_0 = I_w + I_u \quad \text{and} \quad V_1 = I_1 R_1 + I_1 X_1 + E_1$$

phasor diagram on inductive load,

