



**K. J. Somaiya College of Engineering, Mumbai-77**  
**(Autonomous College Affiliated to University of Mumbai)**  
**Semester: July 18 – November 18**

**Max. Marks: 40**

**Class: FY**


**Branch: ALL**

**Course Name: Elements of Electrical and Electronics Engineering**

**Duration: 1hr. 30 min.**


**Semester: I**

**Test 1**

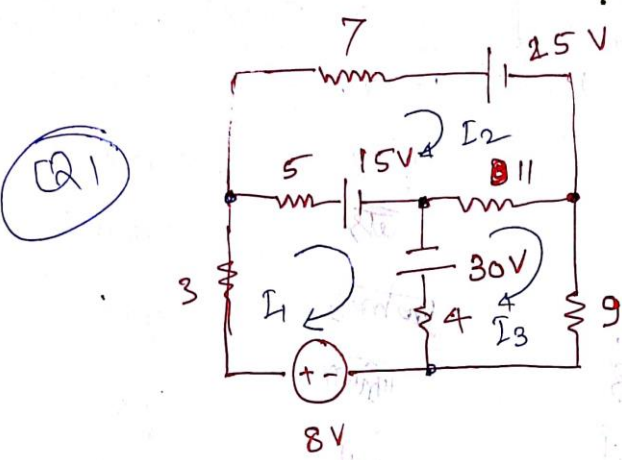Q. No	Questions	Marks
Q.1	<p>Use mesh analysis to calculate current flowing through <math>7\ \Omega</math> resistance in the following electrical network.</p>  <p style="text-align: center;">using loop ana. find current thru. <math>7\ \Omega</math> resis. (10)</p> <p><u>In Loop ①</u></p> $-3I_1 - 5(I_1 - I_2) - 15 + 30 - 4(I_1 - I_3) + 8 = 0$ $\therefore -12I_1 + 5I_2 + I_3 = -23 \quad \text{--- ①}$ <p><u>In Loop ②</u></p> $-7I_2 - 25 - 11(I_2 - I_3) + 15 - 5(I_2 - I_1) = 0$ $\therefore 5I_1 - 23I_2 + 11I_3 = 10 \quad \text{--- ②}$ <p><u>In Loop ③</u></p> $-30 - 11(I_3 - I_2) - 9I_3 - 4(I_3 - I_1) = 0$ $\therefore 4I_1 + 11I_2 - 24I_3 = 30 \quad \text{--- ③}$ <p>From above 3 eqs we get</p> $I_1 = 1.03\text{ A}$ $I_2 = -0.932\text{ A}$ $I_3 = 1.51\text{ A}$ <p style="text-align: center;"><math>I_{7\Omega} = I_2 = 0.932\text{ A} \leftarrow</math></p>	10

OR

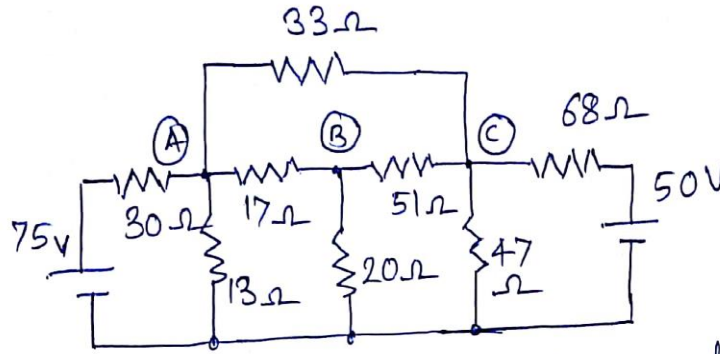Using nodal analysis, calculate power absorbed in  $17\ \Omega$  resistance in the following electrical circuit



When node Ⓐ is considered, we get

$$\frac{V_A - 75}{30} + \frac{V_A}{13} + \frac{V_A - V_B}{17} + \frac{V_A - V_C}{33} = 0$$

$$\therefore V_A \left( \frac{1}{30} + \frac{1}{13} + \frac{1}{17} + \frac{1}{33} \right) - \frac{V_B}{17} - \frac{V_C}{33} = \frac{75}{30} \quad \text{--- (1)}$$

When node Ⓑ is considered, we get

$$\frac{V_B - V_A}{17} + \frac{V_B}{20} + \frac{V_B - V_C}{51} = 0$$

$$\therefore -\frac{V_A}{17} + V_B \left( \frac{1}{17} + \frac{1}{20} + \frac{1}{51} \right) - \frac{V_C}{51} = 0 \quad \text{--- (2)}$$

When node Ⓒ is considered, we get

$$\frac{V_C - V_B}{51} + \frac{V_C}{47} + \frac{V_C - 50}{68} + \frac{V_C - V_A}{33} = 0$$

$$\therefore -\frac{V_A}{33} - \frac{V_B}{51} + V_C \left( \frac{1}{51} + \frac{1}{47} + \frac{1}{68} + \frac{1}{33} \right) = \frac{50}{68} \quad \text{--- (3)}$$

From above three eqs. we get


$$V_A = 18.52\text{V}, V_B = 11.18\text{V}, V_C = 17.64\text{V}$$

$$P_{17\Omega} = \frac{(V_A - V_B)^2}{17} = \frac{(18.52 - 11.18)^2}{17} = \underline{3.17\text{W}}$$

Q.2

Calculate current flowing through  $4\ \Omega$  resistance in the following network by using Norton's theorem.

10

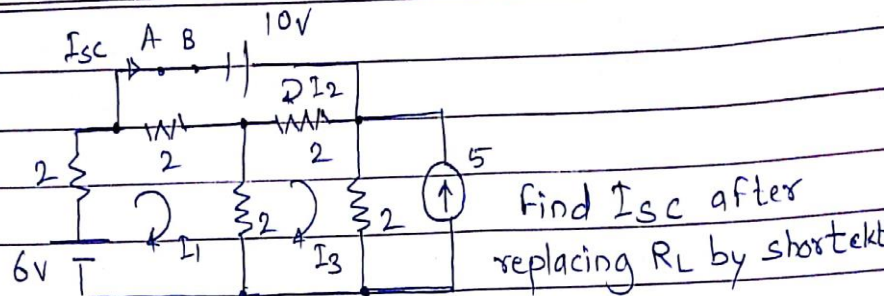

When Loop ① is considered, we get

$$-2I_1 - 2(I_1 - I_2) - 2(I_1 - I_3) + 6 = 0$$

$$\therefore -6I_1 + 2I_2 + 2I_3 = -6 \quad \text{--- ①}$$

When Loop ② is considered, we get

$$-2(I_2 - I_1) + 10 - 2(I_2 - I_3) = 0$$

$$\therefore 2I_1 - 4I_2 + 2I_3 = -10 \quad \text{--- ②}$$

When Loop ③ is considered, we get

$$-2(I_3 - I_2) - 2(I_3 + 5) - 2(I_3 - I_1) = 0$$



$$\therefore 2I_1 + 2I_2 - 6I_3 = 10 \quad \text{--- ③}$$

after solving above eq. ①, ② & ③ we get


$$I_1 = 2.50\text{ A}, I_2 = 4.00\text{ A}, I_3 = 0.5\text{ A}$$

$$I_{sc} = I_2 = 4\text{ A (}\rightarrow\text{)} = I_N$$

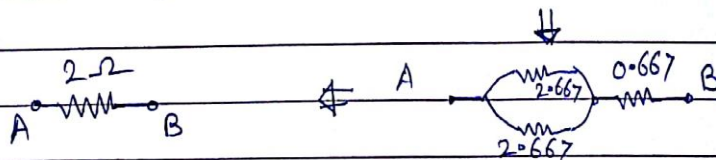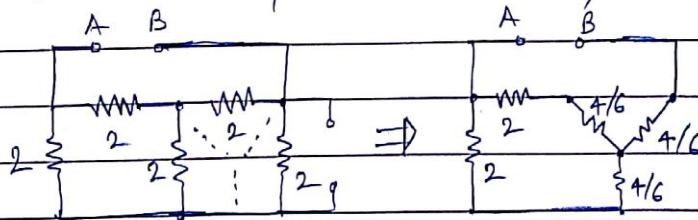To find  $R_N$  replace all sources by its eqv. resistances.



$$\therefore R_N = 2\ \Omega$$

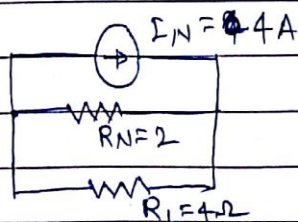


$$I_L = \frac{R_N}{R_N + R_L} I_N = 1.33\text{ A (+)}$$



OR

Calculate current flowing through  $10\ \Omega$  resistance in the following network by using Thevenin's theorem.

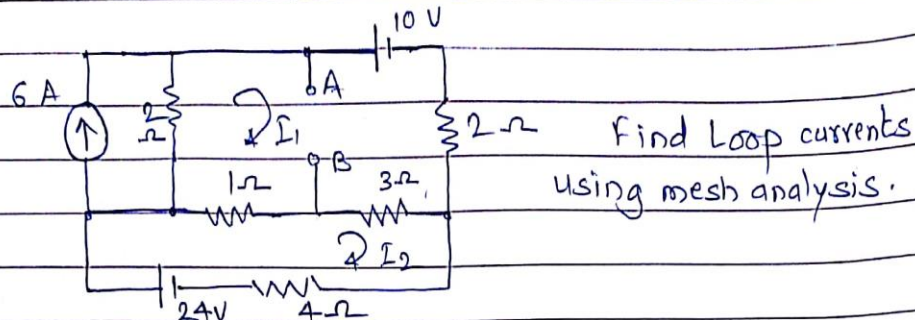Find open circuit voltage by removing load resistance from ckt.



Find Loop currents using mesh analysis.

When Loop ① is considered, we get.

$$-2(I_1 - 6) - 10 - 2I_1 - 4(I_1 - I_2) = 0$$

$$\therefore -8I_1 + 4I_2 = -2 \quad \text{--- (1)}$$

When Loop ② is considered, we get

$$-4(I_2 - I_1) - 4I_2 + 24 = 0$$

$$\therefore 4I_1 - 8I_2 = -24 \quad \text{--- (2)}$$

After solving eq. ① & ② we get,

$$I_1 = 2.333\text{A}, I_2 = 4.1667\text{A}$$



considering left side of Loop ①





$$\therefore V_{AB} - 2(6 - I_1) - 1(I_2 - I_1) = 0$$

$$\therefore V_{AB} = 2(6 - 2.333) - 1(4.1667 - 2.333) = 0$$

$$\therefore V_{AB} = 9.168\text{V} = V_{TH}$$

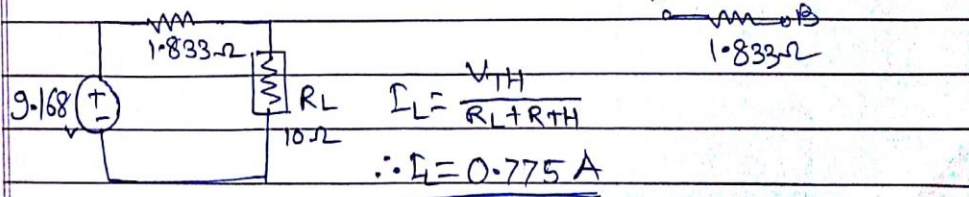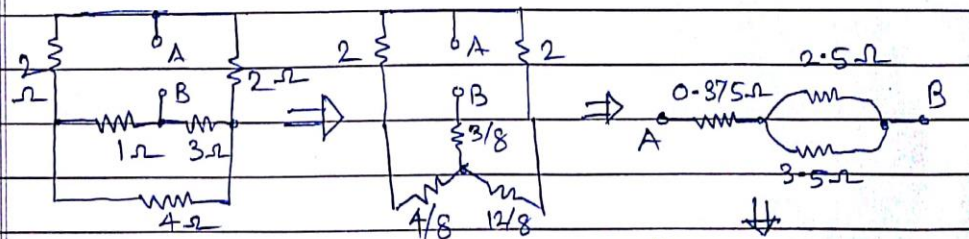to find  $R_{TH}$  replace all sources by its eqv. resistances.



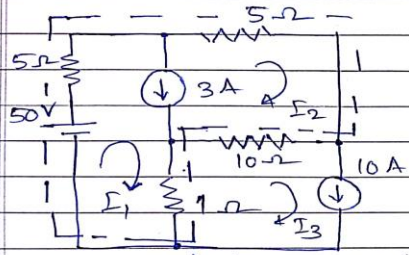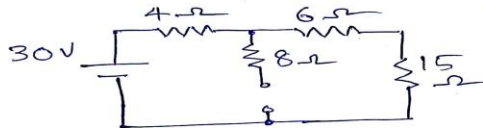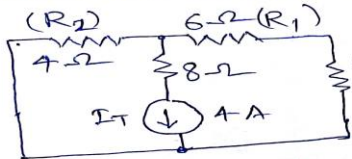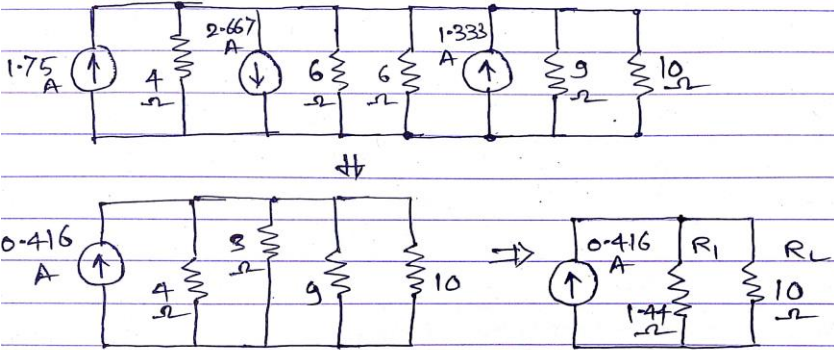Q.3	<p>Calculate power consumed by <math>10\ \Omega</math> resistance in the following electrical circuit using super-mesh analysis.</p>  <p>In the given n/w we know that Loop ③ has constant current source <math>\therefore I_3 = 10\text{ A}</math>          Loop ① &amp; ② form a super Loop &amp;  <math>I_1 - I_2 = 3\text{ A}</math> - ① given.</p> <p>considering superloop formed by Loop ① &amp; Loop ②          we get : <math>50 - 5I_1 - 5I_2 - 10(I_2 - I_3) - 1(I_1 - I_3) = 0</math>  <math>\therefore 50 - 5I_1 - 5I_2 - 10(I_2 - 10) - 1(I_1 - 10) = 0</math>  <math>\therefore -6I_1 - 15I_2 = -160</math> - ②  <math>\therefore I_1 = 9.762\text{ A}, I_2 = 6.762\text{ A}</math>  <math>I_{10\Omega} = I_2 - I_3 = 6.762 - 10 = -3.238\text{ A}</math> (↑)  <math>\therefore P_{10\Omega} = I_{10\Omega}^2 \times R = 3.238^2 \times 10 = 104.85\text{ W}</math></p>	10
Q 4 A	<p>With the help of superposition theorem calculate current flowing through <math>15\ \Omega</math> resistance in the following electrical circuit.</p> <p>When <math>30\text{ V}</math> source is present in the ckt.</p>  <p><math>I_1' = \frac{30}{4+6+15} = 1.2\text{ A}</math> (↓)</p> <p>When <math>4\text{ A}</math> source is present in the ckt.</p>  <p><math>I_1'' = I_T \times \frac{R_2}{R_2 + R_1 + R_L}</math>  <math>= 4 \times \frac{4}{4+6+15}</math>  <math>= 0.64\text{ A}</math> (↑)</p> <p><math>I_1 = I_1'' + I_1'</math>  <math>= 1.2\text{ A} (\downarrow) + 0.64\text{ A} (\uparrow) = 0.56\text{ A} (\downarrow)</math></p>	5
Q 4 B	<p>What will be current flowing through <math>10\ \Omega</math> resistance in the following electrical circuit? Use source transformation technique.</p>  <p><math>I_{10\Omega} = I_T \times \frac{R_1}{R_1 + R_L} = 0.416 \times \frac{1.44}{10 + 1.44} = 0.052\text{ A}</math></p>	5