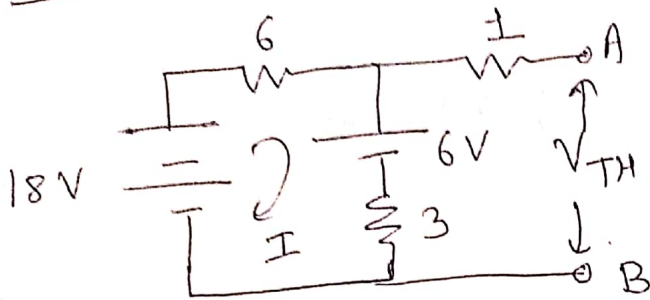


Q.2 A.




$$6I + 6 + 3I - 18 = 0$$


$$9I - 12 = 0$$

$$I = \frac{12}{9} = \frac{4}{3} \text{ A}$$

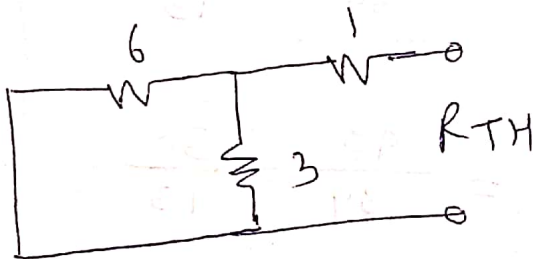
$$V_{TH} = 6 + 3I = 6 + 3 \cdot \frac{4}{3} = 10 \text{ V} \quad \text{--- (2) marks}$$


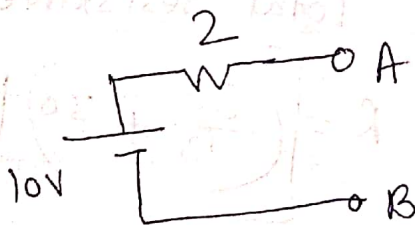
$$R_{TH} = (6 \parallel 3) + 1 = \frac{18}{9} + 1 = 2 \Omega \quad \text{--- (1) mark}$$





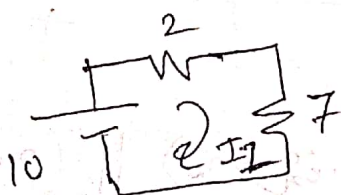Thevenin's equivalent circuit --- (1) mark



$$I_7 = \frac{10}{2+7} = \frac{10}{9} \text{ A} \quad \text{--- (1) mark}$$

Q.2 B)

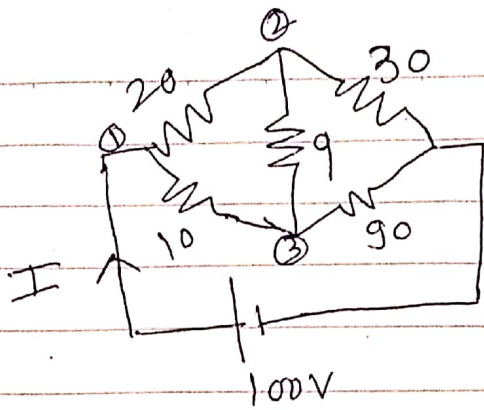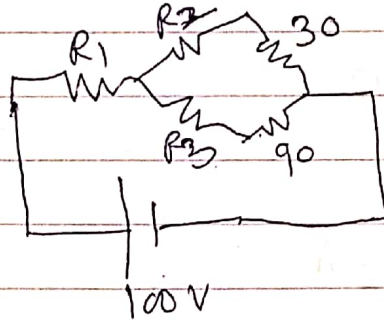Find I - Δ to Y conversion by pts. ①, ② & ③


$$R_1 = \frac{20 \times 10}{20 + 10 + 9}$$

$$R_1 = \frac{200}{39}$$

$$R_2 = \frac{20 \times 9}{39} = \frac{180}{39} = \frac{60}{13}$$

$$R_3 = \frac{10 \times 9}{39} = \frac{90}{39} = \frac{30}{13}$$

(2) marks

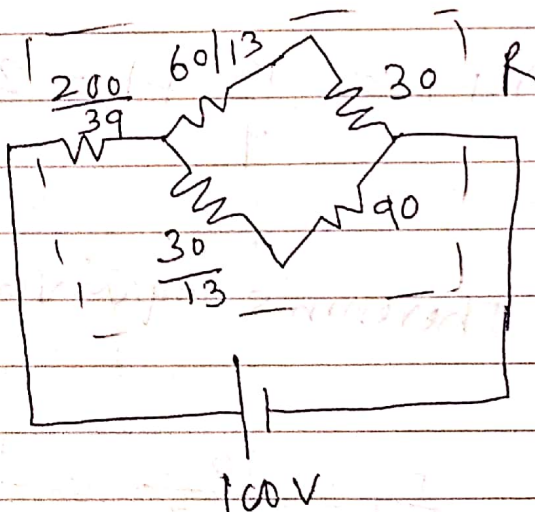Total resistance R

$$R = \left[\left(\frac{60}{13} + 30 \right) \parallel \left(\frac{30}{13} + 90 \right) \right] + \frac{200}{39}$$


$$R = \left[(4.62 + 30) \parallel (2.31 + 90) \right] + \frac{200}{39}$$

Teacher's Signature.....

$$R = (34.62 \parallel 92.31) + 5.13$$


$$R = 25.17 + 5.13 = 30.31 \text{ — (2) marks}$$
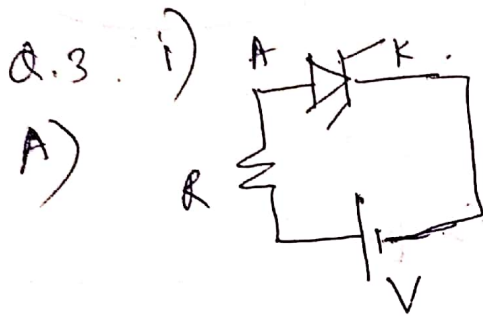
$$I = \frac{100}{30.31} = 3.299 \text{ A. — (1) mark.}$$




i) Forward biased.

— (2) marks.

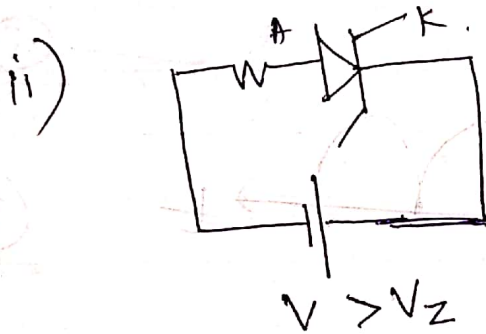


ii) Reverse biased.

— (2) marks.

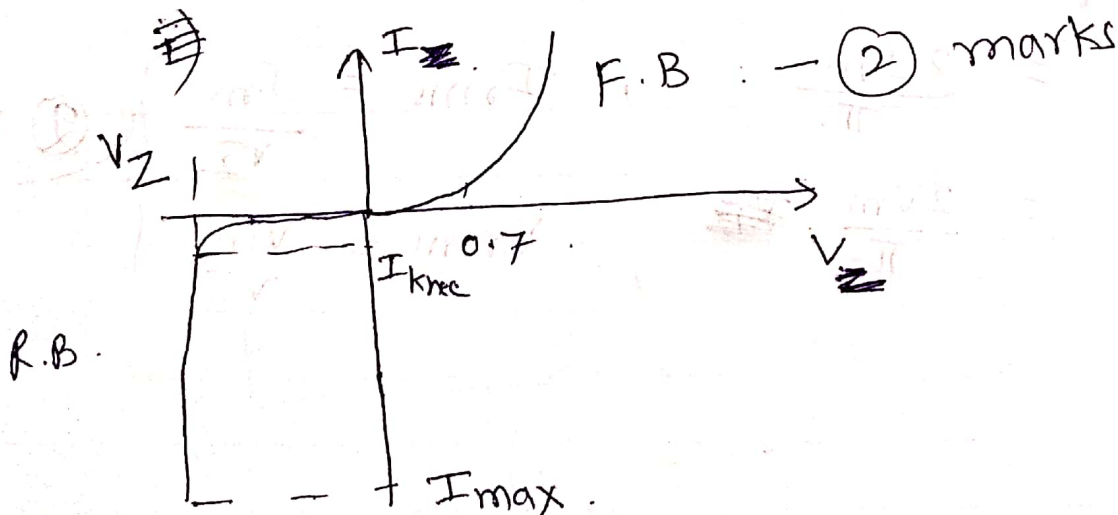


Q.3 B)

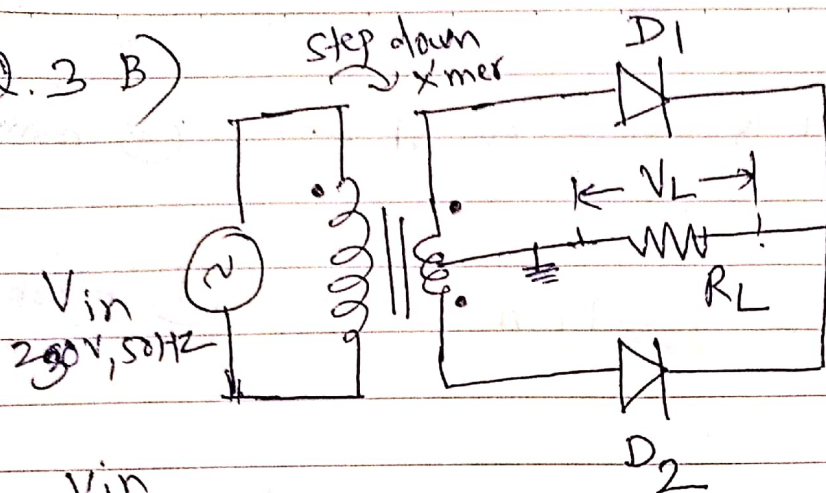

1 1/2 marks

1 1/2 marks

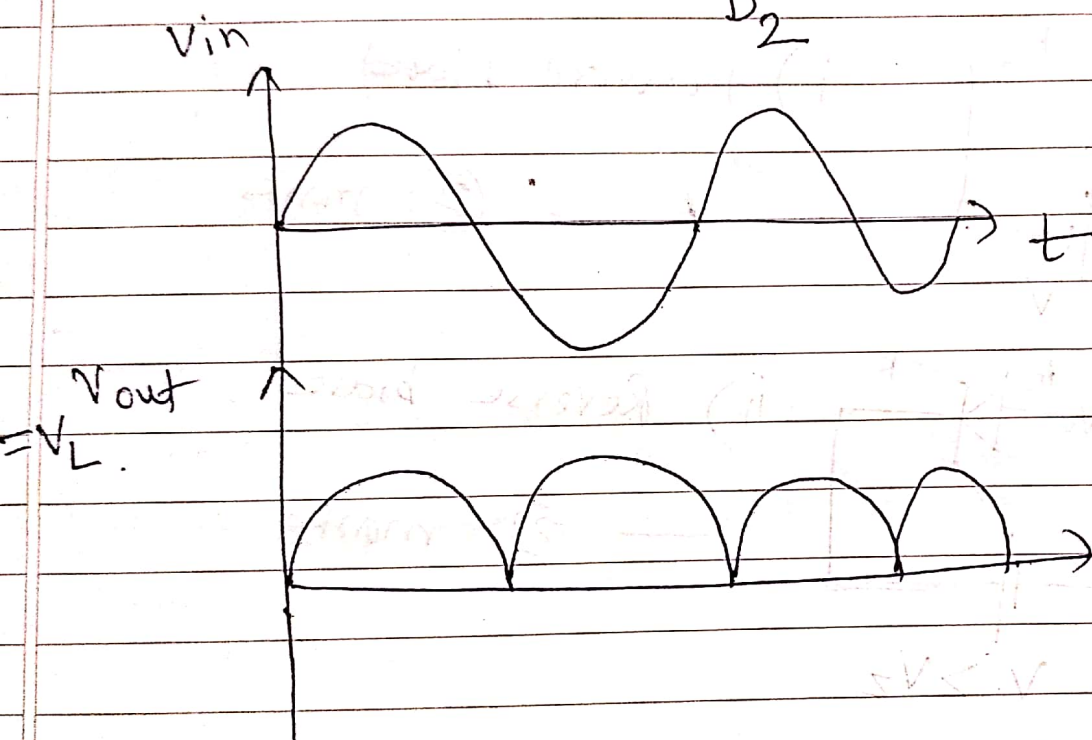① mark
②

1/2 mark

$$I_{dc} = \frac{2I_m}{\pi}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

② mark


$$V_{dc} = \frac{2V_m}{\pi}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

OR

Q.3.

CB — construction dia —

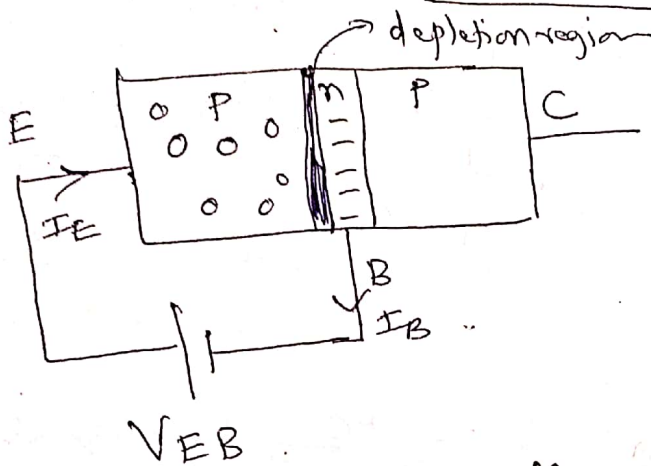

(2) marks


— Forward biased E-B jⁿ

— Width of depletion region reduces resulting in heavy flow of majority carrier current from p to n.

(2) marks

p — holes are majority carriers.

n — electrons are majority carriers.

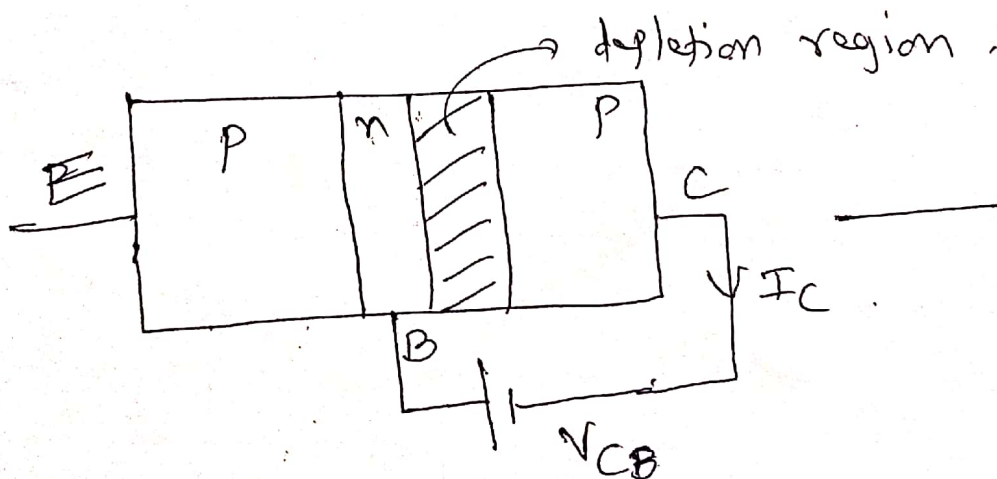

(2) marks


— Reverse biased B-C jⁿ.

— Width of depletion region increases

(2) marks

OR

OR.
CB - configuration dia.

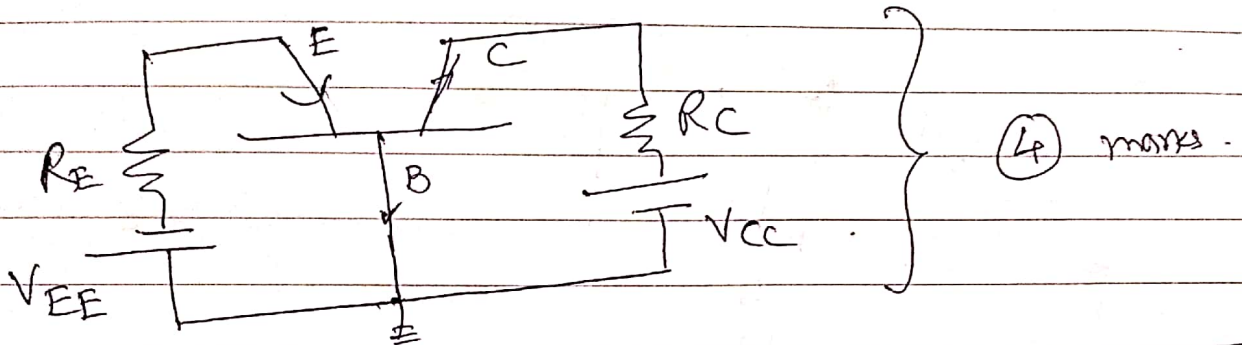

current gain, $\alpha = \frac{I_C}{I_E}$ — (1) mark