

D.C. Circuits

Classification of electrical energy sources:

i) Voltage Source:

- i) Independent: a) Ideal
b) Practical
- ii) Dependent

ii) Current Source

- i) Independent: a) Ideal
b) Practical
- ii) Dependent

Independent Voltage Source


i) Ideal Voltage Source

Symbol:



→ Case I:


With $R_L = \infty$ (open circuit)

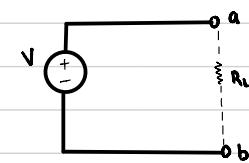

- Complete voltage 'V' is available across terminals 'a' & 'b'


→ Case II

With load resistance = R_L

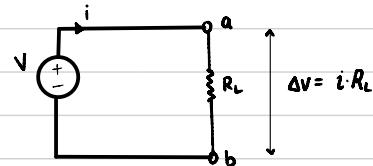


2) Practical Voltage Source

Symbol:

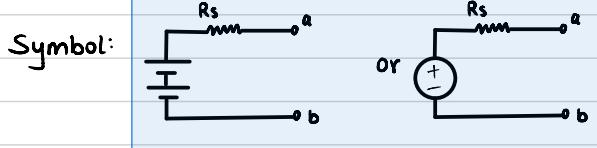


→ Case I:

With $R_L = \infty$ (open circuit)

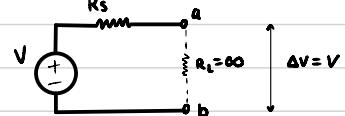

→ Case II


With load resistance = R_L

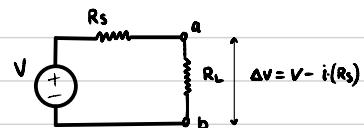

Independent Current Source


1) Ideal Current Source

Symbol:

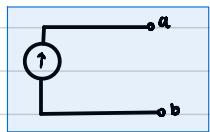


Case I:

With $R_L = \infty$ (open circuit)

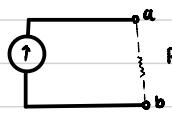


• Shunt resistance is ∞ .

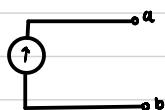


→ Case II

With load resistance = R_L

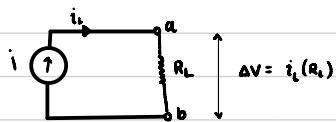

2) Practical Current Source


Symbol:

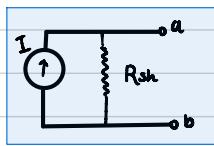

* R_{sh} : Internal shunt resistance


Case I:

→ With $R_L = \infty$ (open circuit)

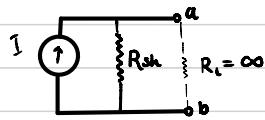

→ Case II

With load resistance = R_L

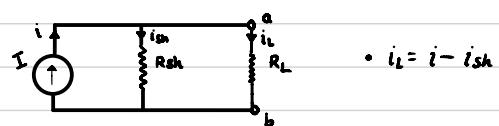


• $i_L = i - i_{sh}$

Dependent Voltage Source

- Voltage or current of source depends on some other voltage or current
- 4 types — Having 2 input & 2 output terminals
- i) 'V' controlled 'V' source (VCSV)
- ii) 'V' controlled 'C' source (VCVS)
- iii) 'C' controlled 'V' source (CCVS)
- iv) 'C' controlled 'C' source (CCCS)


VCVS

Symbol:

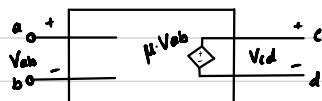

$$V_{cd} = \mu \cdot V_{ab}$$


VCCS

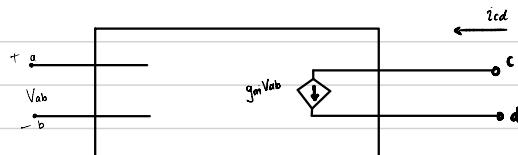

g_m = transconductance / mutual conduction

$$i_{cd} = g_m \cdot V_{ab}$$

CCVS

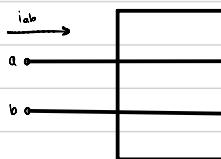


$$V_{cd} = r \cdot i_{ab}$$

r : mutual resistance / transresistance

Unit: V/Amp or ohm.


CCCS

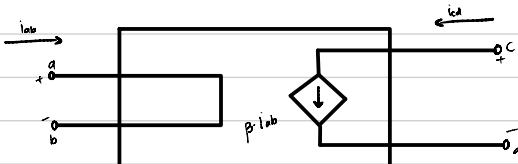

where β = current gain

Transformation of Sources

Case - I

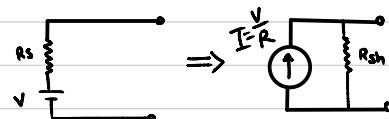

Example: i)



ii)




Case - II





Example: i)




ii)

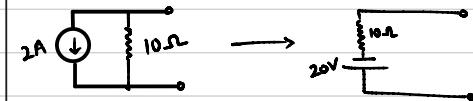


Case - III

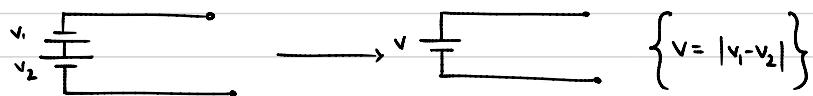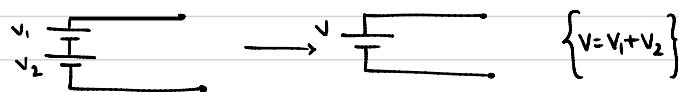


Case - IV

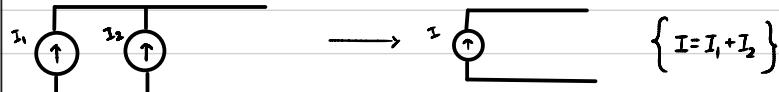


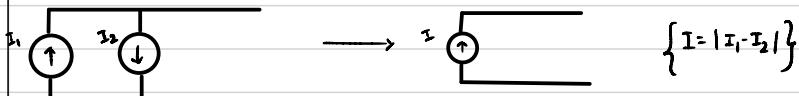

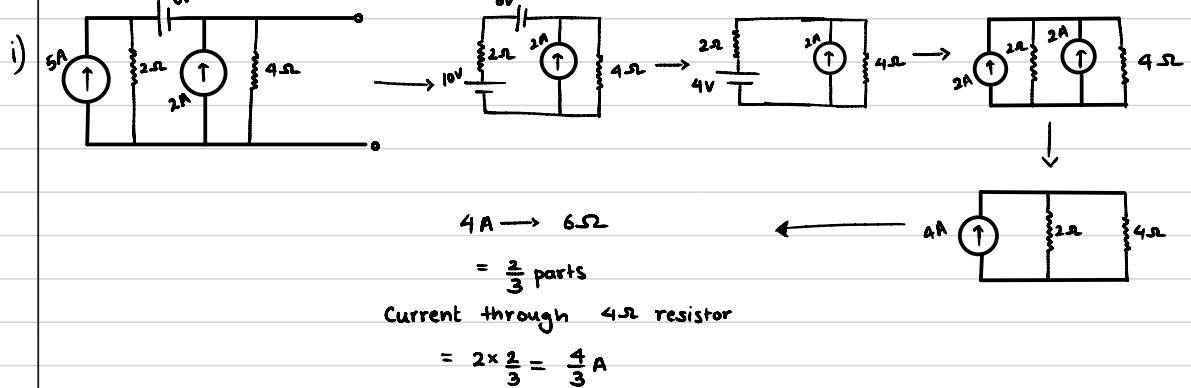Q. Find value of current in following circuits.




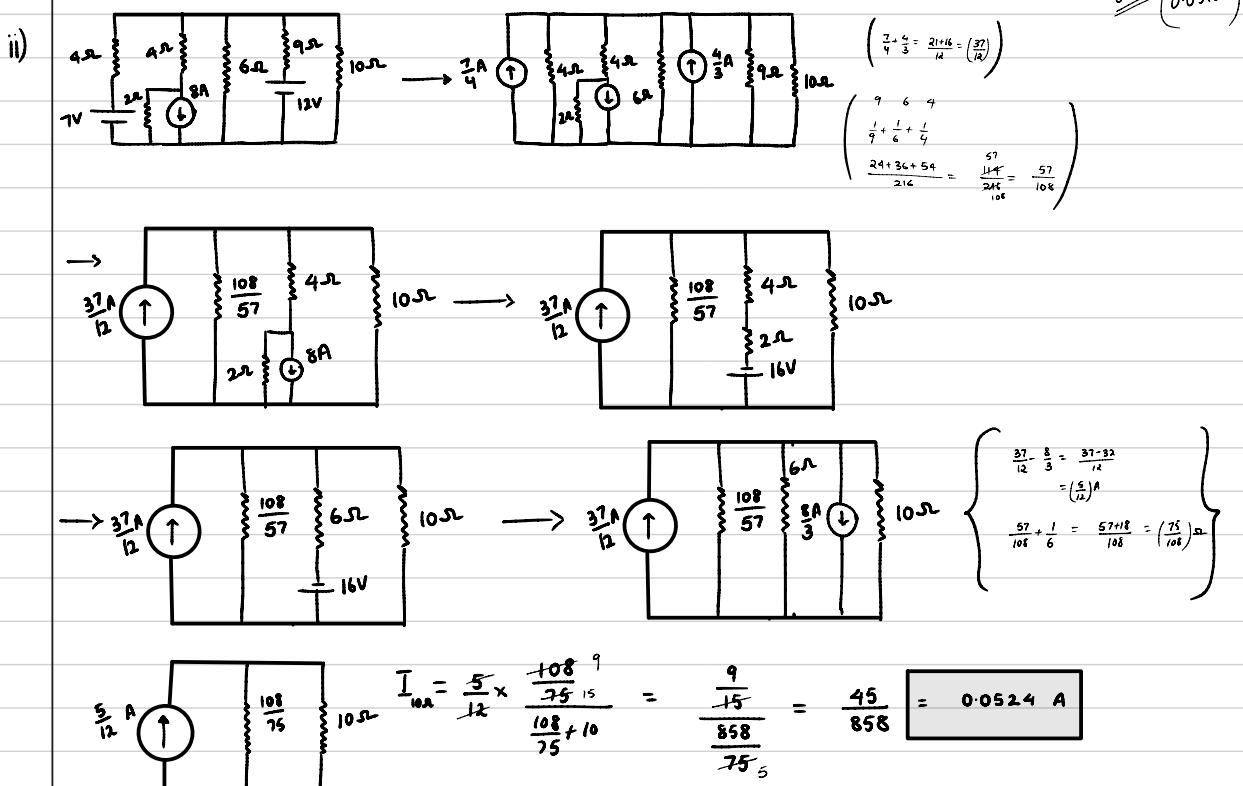Ans: Current through 4Ω resistor
is $1.334 A$



Voltage Divider Circuit

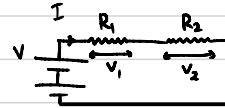- $V_1 = I(R_1) = \frac{V}{R_1} \cdot R_1$



$$V = V_1 + V_2$$

- $V_2 = I(R_2) = \frac{V}{R_1} \cdot R_2$

Current Divider Circuit

- $i_1 = \frac{V}{R_1}$


- $i_2 = \frac{V}{R_2}$

- $i_3 = \frac{V}{R_3}$


$$\left. \begin{array}{l} i_1 \\ i_2 \\ i_3 \end{array} \right\} = \frac{V}{R_1 + R_2 + R_3}$$

$$i_T = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$i_T = \frac{V}{R_T}$$

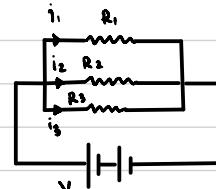

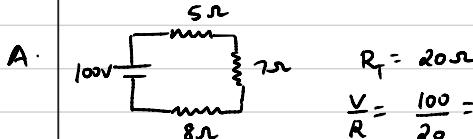Q. Determine the current through & voltages across 5Ω , 7Ω , 8Ω connected in series across $100V$ supply.



$$R_T = 20\Omega$$


$$\frac{V}{R} = \frac{100}{20} = 5A$$

$$V_1 = 5(5), V_2 = 5(7), V_3 = 5(8)$$

$$= 25V$$

$$= 35V$$

$$= 40V$$

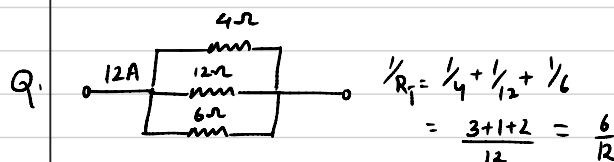

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{12} + \frac{1}{6}$$

$$= \frac{3+1+2}{12} = \frac{6}{12}$$

$$V = IR \\ = 12(2)$$

$$= 24V$$


$$(R_T = 2\Omega)$$

$$i_1 = \frac{24}{4} = 6A$$

$$i_2 = \frac{24}{12} = 2A$$

$$i_3 = \frac{24}{6} = 4A$$

Q.

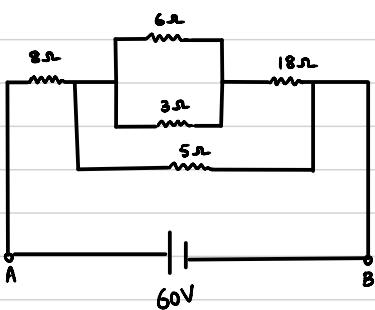

$$\frac{1}{6} + \frac{1}{3} = \frac{3+6}{18} = \frac{1}{2} \Rightarrow 2\Omega + 18\Omega = 20\Omega$$

$$\frac{1}{20} + \frac{1}{5} = \frac{5}{20} \Rightarrow \frac{1}{4} = 4\Omega$$


$$4 + 8 = (12\Omega) - R_T$$

$$V = IR$$

$$I = \frac{60}{12} = (5A)$$

Current through
8Ω resistor = 5A

Ans: 3.435Ω

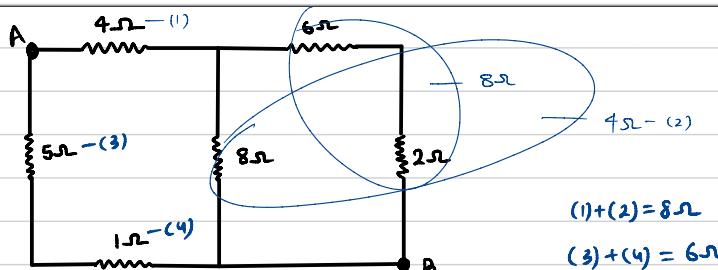

$$(1) + (2) = 8\Omega$$


$$(3) + (4) = 6\Omega$$

$$\frac{1}{R} = \frac{1}{8} + \frac{1}{6}$$

$$\rightarrow \frac{1}{R} = \frac{6+8}{48} \rightarrow \frac{1}{R} = \frac{14}{48} = \frac{7}{24}$$

$$\therefore R = \frac{24}{7} = 3.43\Omega$$

Terminology

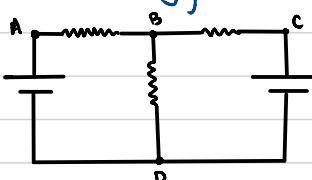

1]

Node: Junction where two or more elements are connected.
(in above example: A, B, C, D)

2)

Branches: Any element/s connected between two nodes.
(in above example: AB, BD, BC)

- ~~1~~ 3) Loop: Any closed path in a circuit.
(In example: ABDA, BCDB, ABCDA)


- ~~1~~ 4) Mesh:

Kirchoff's Law

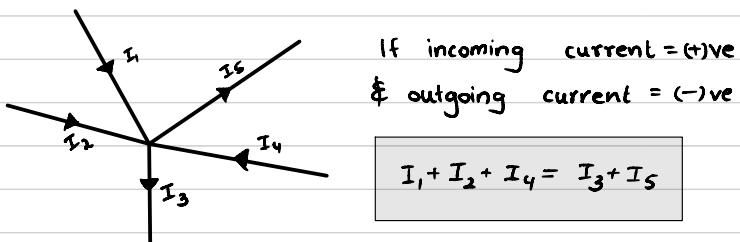- 1) Kirchoff's current law (KCL)
- 2) Kirchoff's voltage law (KVL)

Kirchoff's Current Law

Algebraic sum of current meeting at a junction/node in an electric circuit is zero.




Kirchoff's Voltage Law

In any closed circuit / mesh, algebraic sum of electromotive forces & voltage drop equals zero.

Sign Conventions

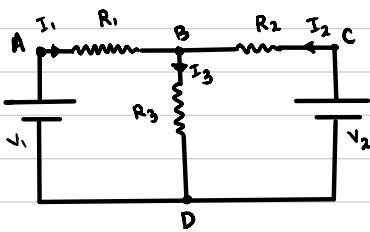- 1) Rise in potential — (+)ve
- 2) Fall in potential — (-)ve
- 3) ΔV along the flow of current across a resistor — (-)ve
- 4) ΔV opposite the flow of current across a resistor — (+)ve



Using KVL in ABDA


$$V_1 - i_1 R_1 - i_3 R_3 = 0$$

Using KVL in ABCDA

$$V_1 - i_1 R_1 + i_2 R_2 - V_2 = 0$$

Using KVL in BCDB

$$V_2 - i_2 R_2 - i_3 R_3 = 0$$

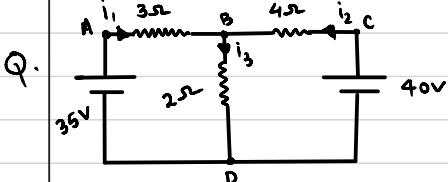

$$36 - i_1(3) - i_3(2) = 0$$

$$3i_1 + 2i_3 = 36 \quad \text{--- (1)}$$

$$40 - i_2(4) - i_3(2) = 0$$

$$4i_2 + 2i_3 = 40$$


$$36 - i_1(3) + i_2(4) - 40 = 0$$

$$4i_2 - 3i_1 = 5 \quad \text{--- (2)}$$

$$\begin{aligned} i_3 &= (i_1 + i_2) \\ 2i_2 + i_1 + i_2 &= 20 \\ i_1 + 3i_2 &= 20 \end{aligned}$$

$$5i_1 + 2i_2 = 35$$
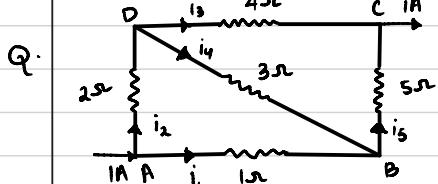
$$\begin{aligned} i_1 &= 5A \\ i_2 &= 5A \\ i_3 &= 10A \end{aligned}$$



$$i_1 + i_2 = 1A$$

$$i_3 + i_5 = 1A$$

$$i_3 + i_4 = i_2$$

$$i_1 + i_4 = i_5$$

$$-i_2(2) - i_4(3) + i_1(1) = 0$$

$$i_1 = 2i_2 + 3i_4 \rightarrow i_4 = \frac{i_1 - 2i_2}{3} \rightarrow 1 - i_2 = 2i_2 + 3(i_2 - i_3)$$

$$1 = 6i_2 - 3i_3 \quad \text{--- (1)}$$

$$-i_3(4) + i_5(5) + i_4(3) = 0$$

$$4i_3 = 3i_4 + 5i_5 \quad \leftarrow \quad 4i_3 = 6 - 8i_2 + 5i_4$$

$$4i_3 = 3(i_1 - 2i_2) + 5i_5$$

$$4i_3 = 6 - 8i_2 + 5i_4$$

$$9i_3 = 6 - 3i_2$$

$$3i_2 + 9i_3 = 6$$

$$4i_3 = i_1 - 2i_2 + 5i_5$$

$$i_2 + 3i_3 = 2 \quad \text{--- (1)}$$

$$4i_3 = 1 - 3i_2 + 5i_5$$

$$+ \frac{6i_2 - 3i_3 = 1}{7i_2 = 3} \rightarrow i_2 = \frac{3}{7}A \quad \text{hence } i_3 = \frac{11}{21}A$$

$$i_3 + i_4 = i_2$$


$$i_4 = \frac{3 - 11}{7 - 21} = \frac{-8}{14} = -\frac{4}{7}A$$

$$i_1 = 1 - i_2 \Rightarrow i_5 = i_1 + i_4$$


$$\therefore i_1 = \frac{4}{7}A \quad = \frac{4}{7} - \frac{4}{7} = \frac{10}{21}A$$

<u>Ans:</u>	$i_1 = \frac{4}{7}A = 0.571A$	$i_3 = \frac{11}{21}A = 0.523A$	$i_5 = \frac{10}{21}A = 0.476A$
	$i_2 = \frac{3}{7}A = 0.428A$	$i_4 = -\frac{4}{7}A = -0.571A$	

Star - Delta Transformation

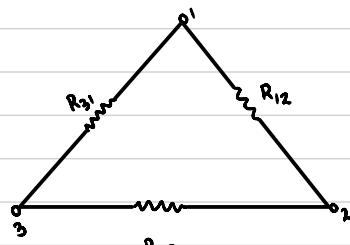

— Delta connection (Fig 1.1)

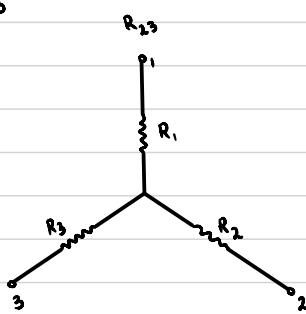

— Star Connection (Fig 1.2)

(I) Delta (Δ) to Star (Y) transformation

In Fig 1.1, $R_{12} \parallel (R_{23} + R_{31})$

$$R_{eq} = \frac{(R_{12})(R_{23} + R_{31})}{R_{12} + (R_{23} + R_{31})}$$

In Fig 1.2, R_{eq} between ① & ② is in series

$$\therefore R_{eq} = R_1 + R_2$$

Since both networks are electrically equivalent

$$\Rightarrow \frac{(R_{12})(R_{23} + R_{31})}{R_{12} + (R_{23} + R_{31})} = R_1 + R_2 \quad \text{--- (between ① & ②)} \quad \text{--- i}$$

$$\frac{(R_{23})(R_{12} + R_{31})}{R_{23} + (R_{12} + R_{31})} = R_2 + R_3 \quad \text{--- (between ② & ③)} \quad \text{--- ii}$$

$$\frac{(R_{31})(R_{12} + R_{23})}{R_{31} + (R_{12} + R_{23})} = R_3 + R_1 \quad \text{--- (between ③ & ①)} \quad \text{--- iii}$$

iii - i

$$R_1 - R_3 = \frac{(R_{12})(R_{31}) - (R_{23})(R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- iv}$$

iii + iv

$$R_1 = \frac{(R_{12})(R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{--- v}$$

$$R_3 = \frac{(R_{31})(R_{23})}{R_{12} + R_{23} + R_{31}} \quad \text{--- vii}$$

$$R_2 = \frac{(R_{23})(R_{12})}{R_{12} + R_{23} + R_{31}} \quad \text{--- vi}$$

Star (γ) to Delta (Δ) transformation

(v) \times (vi)

$$R_1 R_2 = \frac{(R_{12})^2 (R_{23})(R_{31})}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- viii}$$

Similarly,

$$R_2 R_3 = \frac{(R_{12})(R_{23})^2 (R_{31})}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- ix} \quad \text{and} \quad R_3 R_1 = \frac{(R_{12})(R_{23})(R_{31})^2}{(R_{12} + R_{23} + R_{31})^2} \quad \text{--- x}$$

viii + ix + x

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} R_{23} R_{31} (R_{12} + R_{23} + R_{31})}{(R_{12} + R_{23} + R_{31})^2}$$

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_{12} \cdot R_{23} \cdot R_{31}}{(R_{12} + R_{23} + R_{31})} \quad \text{--- xi}$$


Using vii in xi

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = R_{12} \cdot R_3$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$
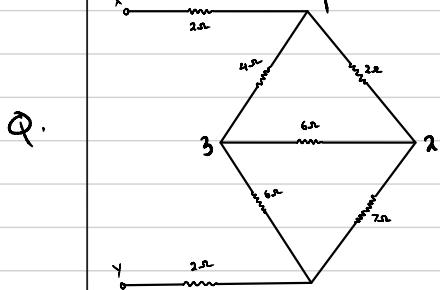
$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2}$$




Find eq. resistance

Ans:


$$R_1 = \frac{4 \times 2}{12} = \frac{8}{12} = \frac{2}{3}$$

$$R_2 = \frac{6 \times 2}{12} = \frac{12}{12} =$$
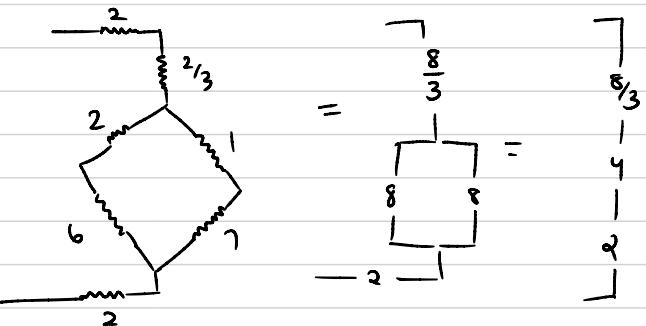
$$R_3 = \frac{4 \times 6}{12} = \frac{24}{12} = 2$$


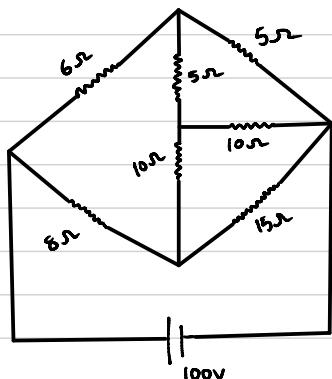
$$= 6 + \frac{8}{3} = \frac{18+8}{3} = \frac{26}{3} \Omega = 8.667 \Omega$$



Find current

$$R_1 = 5\Omega \quad R_2 = 10\Omega \quad R_3 = 10\Omega$$

$$R_{12} = \frac{R_1 + R_2 + \frac{R_1 R_2}{R_3}}{R_3}$$

11




$$R_{23} = \frac{10 + 10 + 10 \times 10}{-5}$$

$$R_{23} = 40 \Omega$$

$$R_{3j} = \frac{10 + 5 + 10 \times 5}{P}$$


$$R_{31} = 20\Omega$$

$$R_{12} = 20 \Omega$$

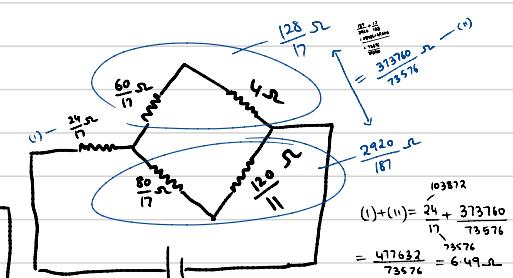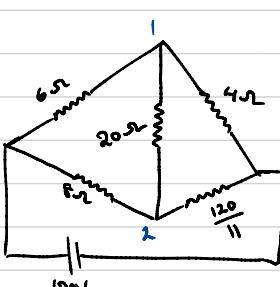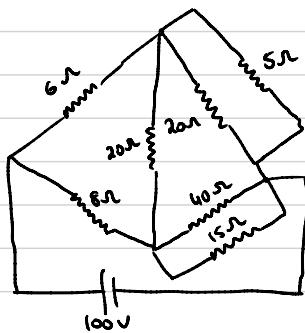

$$V = iR \rightarrow i = \frac{100}{6.49} = 15.40 \text{ A}$$

Mesh Analysis Method

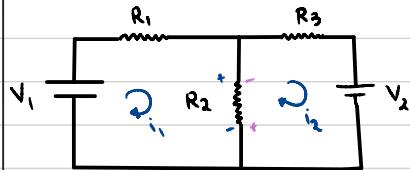


Using Kirchoff's Voltage Law:

$$V_2 + i_2 R_3 + (i_2 - i_1) R_2 = 0$$

$$V_2 = i_1 R_2 - i_2 R_2 - i_2 R_3$$

$$V_2 = i_1 R_2 - i_2 (R_2 + R_3)$$

Q.

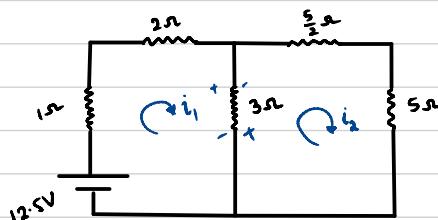

$$12.5 - i_1(1) - i_1(2) - (i_1 - i_2)(3) = 0$$

$$\rightarrow 12.5 - 6i_1 + 3i_2$$

$$\rightarrow (2i_1 - i_2) = \frac{12.5}{3} \rightarrow 2i_1 - i_2 = 4.166$$

$$2.5(i_2) - 5(i_2) - (i_2 - i_1)(3) = 0$$

$$= 3i_1 - 5.5i_2 = 0$$

$$i_1 = \frac{5.5i_2}{3} \quad (2)$$

$$2\left(\frac{5.5i_2}{3}\right) - i_2 = 4.166$$

$$\rightarrow 11i_2 - 3i_2 = 4.166 \times 3$$


$$\rightarrow 8i_2 = 12.498$$

$$i_2 = 1.56 \text{ A}$$

$$i_1 = \frac{5.5 \times 1.56}{3}$$

$$i_1 = 2.86 \text{ A}$$

Q. Find current through 2Ω resistor.

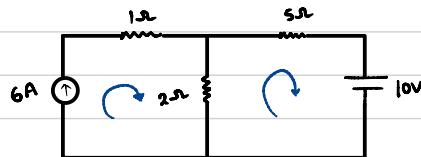

$$-5i_2 - 10 - (i_2 - i_1)(2) = 0$$

$$\rightarrow i_1 = 6 \quad (1)$$

$$-5i_2 - 10 - 2i_2 + 2(6) = 0$$

$$-7i_2 + 2 = 0$$

$$\rightarrow i_2 = \frac{2}{7} \text{ A}$$

Ans: In mesh 1 KVL is not applicable.




$$i_1 = 6 \text{ A}$$

\therefore Current through 2Ω


$$= \frac{2}{7} - 6 = \frac{2 - 42}{7} = \frac{-40}{7} = 5.71 \text{ A}$$

Nodal Analysis

- Based on KCL.

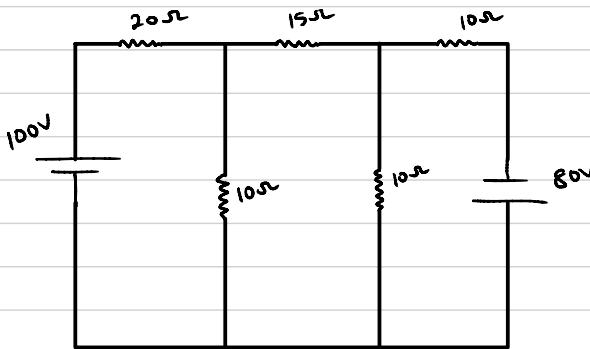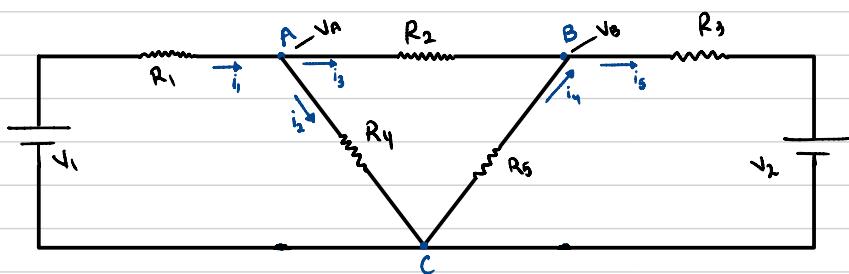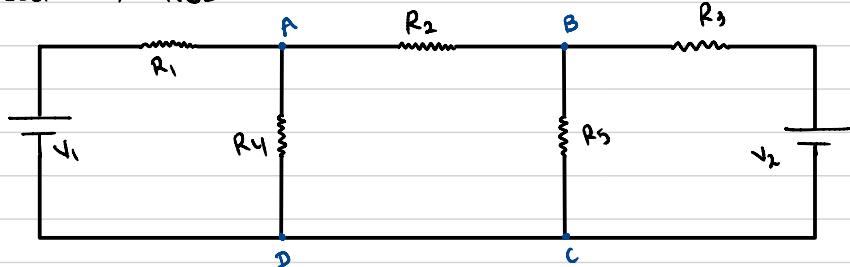

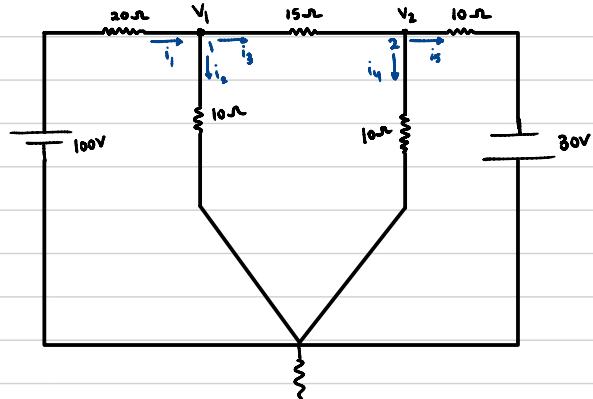Using nodal analysis
find current through
15Ω resistor.



Applying KCL at node ①

$$I_1 = I_2 + I_3$$

$$\frac{100-V_1}{20} = \frac{V_1-0}{10} + \frac{V_1-V_2}{15}$$

$$\frac{100-V_1}{20} = \frac{15V_1 + 10V_1 - 10V_2}{150}$$

$$= 1500 - 15V_1 = 30V_1 + 20V_1 - 20V_2$$

$$\Rightarrow 1500 = 65V_1 - 20V_2$$

$$\Rightarrow 300 = 13V_1 - 4V_2 \quad \text{--- (1)}$$

Applying KCL at node 2

$$I_3 = I_4 + I_5$$

$$\frac{V_1-V_2}{15} = \frac{V_2-0}{10} + \frac{V_2-(-80)}{10}$$

$$\frac{V_1-V_2}{15} = \frac{2V_2 + 80}{10} \Rightarrow 10V_1 - 10V_2 = 30V_2 + 1200$$

$$10V_1 - 40V_2 = 1200$$

$$V_1 - 4V_2 = 120 \quad \text{--- (2)}$$

$$(1) - (2) \quad 300 = 13V_1 - 4V_2$$

$$-120 = -V_1 + 4V_2$$

$$12V_1 = 180$$

$$V_1 = \frac{180}{12} = \frac{30}{2} \rightarrow V_1 = 15V$$


$$15 - 4V_2 = 120$$

$$4V_2 = 15 - 120$$

$$\therefore I_3 = \frac{15 + 26.25}{15}$$

$$= 2.75A$$

$$V_2 = -26.25V$$

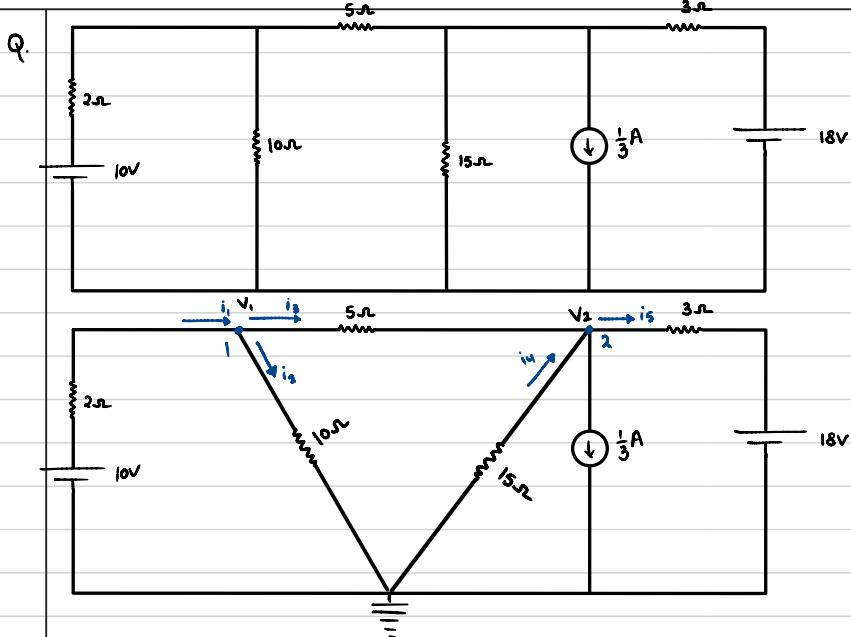

At node ①

$$\frac{10 - V_1}{2} = \frac{V_1 - 0}{10} + \frac{V_1 - V_2}{5}$$

$$\Rightarrow \frac{10 - V_1}{2} = \frac{V_1 + 2V_1 - 2V_2}{10}$$

$$\Rightarrow 50 - 5V_1 = 3V_1 - 2V_2$$

$$8V_1 - 2V_2 = 50$$

$$\Rightarrow 4V_1 - V_2 = 25 \quad (1)$$

At node ②

$$\frac{V_1 - V_2}{5} = \frac{V_2 - 0}{15} + \frac{V_2 - 18}{3} + \frac{1}{3}$$

$$\frac{V_1 - V_2}{5} = \frac{V_2 + 5V_2 - 90 + 5}{15} \rightarrow 3V_1 - 3V_2 = 6V_2 - 85$$

$$\Rightarrow 9V_2 - 3V_1 = 85 \quad (2)$$

$$4V_1 - V_2 = 25 \times 9$$

$$3V_1 - 9V_2 = -85$$

$$\rightarrow 36V_1 - 9V_2 = 225$$

$$- 3V_1 + 9V_2 = + 85$$



$$33V_1 = 310$$

$$V_1 = \frac{310}{33} \quad (1)$$

$$i_2 = \frac{\frac{5}{10} - \frac{310}{33}}{2} = \frac{165 - 155}{33} = \frac{10}{33} = 0.303A$$


Superposition Theorem

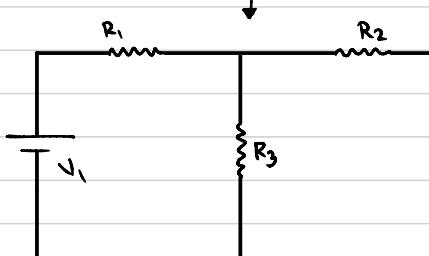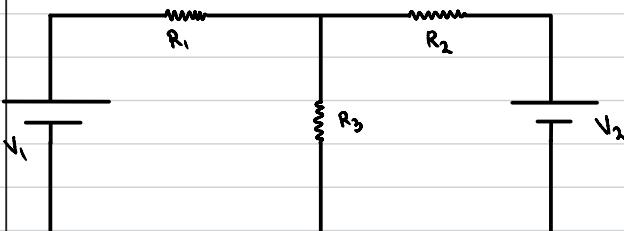- Applicable for linear & bilateral networks.
- Ideal type sources will be replaced by:
voltage — short circuited wire
current — open circuit
- Non-ideal sources are replaced by their internal resistance.



Replacing V_2 with a short wire.

Calculate i through R_3 due to V_1

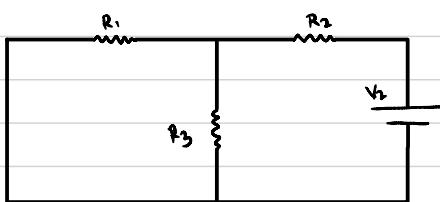


Replacing V_1 with a short wire.

Calculate i through R_3 due to V_2 .

$$I_{3\text{ total}} = I_{R3|V_1} + I_{R3|V_2}$$

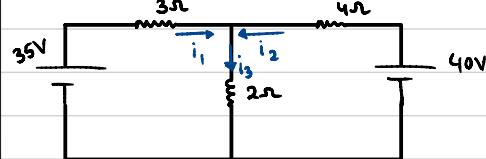Q. Find current through each branch using superposition theorem.



Replacing 35V with short wire:

$$\text{Req} = \frac{3}{2+3} = \frac{3}{5} \Omega \quad \leftarrow \frac{100}{13} \times \frac{3}{2+3} = \frac{100}{13} \times \frac{3}{5}$$

$$V = IR \rightarrow i = \frac{V}{R} = \frac{40}{\frac{26}{5}} = \frac{100}{13} \text{ A} \quad = \frac{60}{13} \text{ through } 2\Omega$$

$$= \frac{40}{13} \text{ through } 3\Omega$$

Replacing 40V with short wire:

$$\text{Req} = \frac{13}{3+2} = \frac{13}{5} \Omega \quad \leftarrow \text{Total current through } R_3 \Rightarrow \frac{100+105}{13} = \frac{205}{13} \text{ A}$$

$$V = IR \quad \leftarrow \frac{1}{2} + \frac{1}{4} = \frac{3}{4} \rightarrow \frac{4}{3} \Omega \quad \therefore i = \frac{V}{R} = \frac{35}{13/3} = \frac{105}{13} \text{ A}$$


$$\frac{4}{3} + 3 = \frac{13}{3} \quad \leftarrow \frac{105}{13} \times \frac{2}{2+4} = \frac{70}{13} \text{ A through } 2\Omega$$

$$= \frac{105}{13} \times \frac{1}{3} = \frac{35}{13} \text{ through } 4\Omega$$

Hence: $i_1 = \frac{65}{13} = 5 \text{ A}$	$i_2 = \frac{65}{13} = 5 \text{ A}$
--	-------------------------------------

$i_3 = \frac{130}{13} = 10 \text{ A}$

Q.

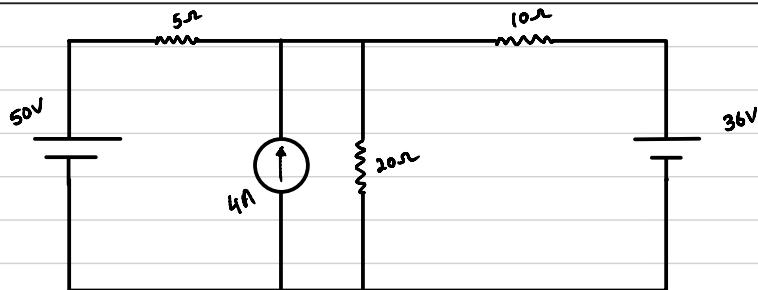


Determine current in 5Ω resistor using superposition theorem.

Ans:

Considering 50V source
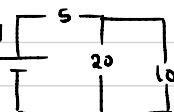
$$\frac{1}{20} + \frac{1}{10} = \frac{3}{20} \rightarrow \frac{20}{3} + 5 = \frac{20+15}{3}$$




$$R_{eq} = \frac{35}{3} \Omega \quad \Rightarrow V = IR \rightarrow i = \frac{V}{R} = \frac{50}{\frac{35}{3}} = \frac{30}{7} A \text{ through } 5\Omega \text{ (→)}$$

$$\frac{30}{7} \times \frac{20}{35} = \frac{20}{7} A \text{ through } 10\Omega \text{ (→)}$$

$$\frac{30}{7} \times \frac{10}{30} = \frac{10}{7} A \text{ through } 20\Omega \text{ (↓)}$$

Considering 36V source

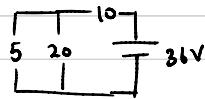


$$\frac{1}{5} + \frac{1}{20} = \frac{5}{20} = \frac{1}{4} = 4\Omega + 10 \Rightarrow R_{eq} = 14\Omega$$

$$V = iR \rightarrow i = \frac{V}{R} \rightarrow i = \frac{36}{14} = \frac{18}{7} A \text{ through } 10\Omega \text{ (←)}$$

$$\frac{18}{7} \times \frac{20}{25} = \frac{72}{35} A \text{ through } 5\Omega \text{ (←)}$$

$$\frac{18}{7} \times \frac{8}{25} = \frac{18}{35} A \text{ through } 20\Omega \text{ (↑)}$$

Considering 4A current source

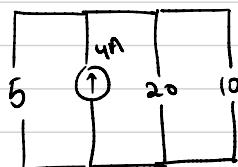

$$\frac{1}{20} + \frac{1}{10} = \frac{3}{20} \Rightarrow \frac{20}{3} \Omega$$



$$4 \times \frac{5}{35} = \frac{4 \times 3}{7} = \frac{12}{7} A \text{ through } \frac{20}{3}\Omega \text{ (→)}$$

$$4 \times \frac{20}{35} = \frac{16}{7} A \text{ through } 5\Omega \text{ (←)}$$


$$\text{Through } 5\Omega \text{ resistor: } \frac{30}{7} - \frac{72}{35} - \frac{16}{7} = \frac{150 - 72 - 80}{35} = \frac{2}{35} A$$

$$= 0.057 A$$

Thevenin's Theorem

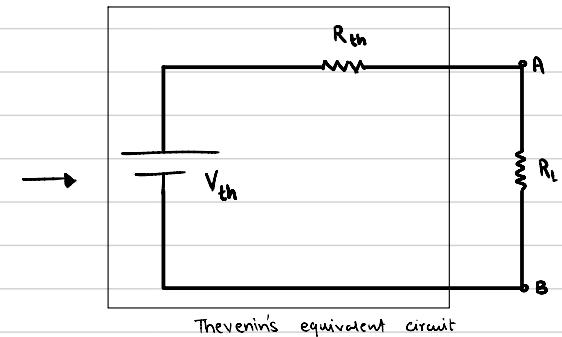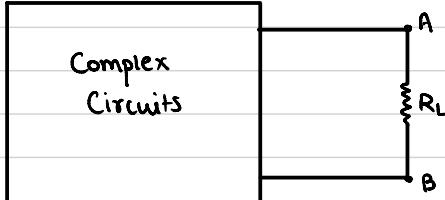

Thevenin's equivalent circuit

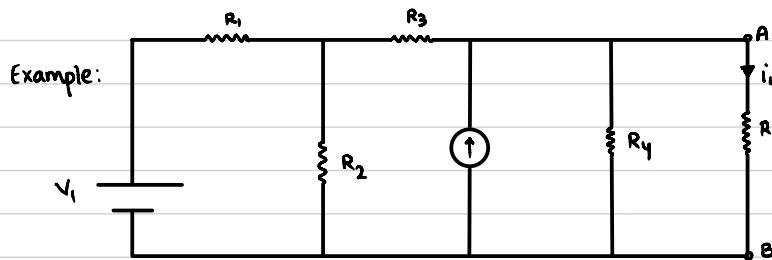

Calculation of V_{th}


- Remove R_L & open the circuit at A & B.
- Calculate V_{th} using any method.

Calculation of R_{th}


- Remove R_L & open the circuit at A & B.
- Replace Voltage Source by equivalent resistance or short wire.
- Replace current source by equivalent resistance or open circuit.

$$i_{load} = \frac{V_{th}}{R_{th} + R_L}$$

Q.

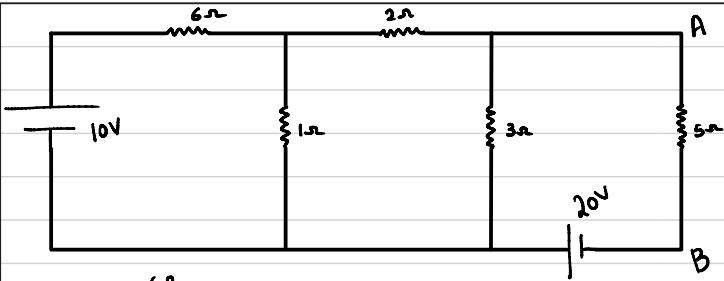

Ans:

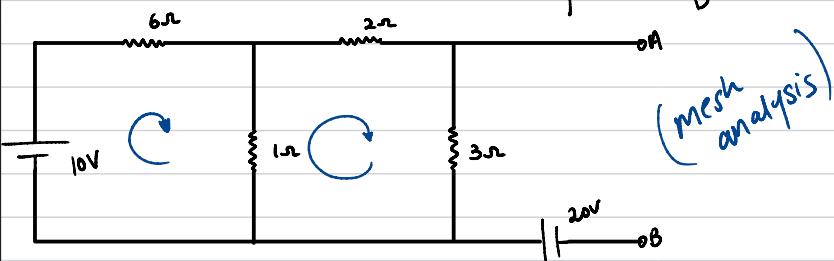

Applying KVL

$$(10 - 6(i_1) - (1(i_1) - i_2)) = 0$$

$$7i_1 - i_2 = 10 \quad \text{--- (1)}$$

$$-2(i_2) - 3(i_2) - (i_2 - i_1) = 0$$

$$i_1 - 6i_2 = 0 \quad \text{--- (2)}$$

$$\therefore i_1 = 6i_2 \quad \text{Putting in (1)}$$

$$42i_2 - i_2 = 10$$

$$i_2 = \frac{10}{41} = 0.244 \text{ A}$$


$$i_1 = \frac{6 \times 10}{41} = 1.46 \text{ A}$$

$$\Delta V_{AB} = V_{th}$$


$$\begin{aligned} V_{th} &= 20 + 3(I_{3\Omega}) \\ &= 20 + 3(0.24) \end{aligned}$$

$$= 20.732$$


$$R_{th} = \begin{array}{c} 2 \\ | \quad | \\ 6 \quad 1 \quad 3 \\ | \quad | \quad | \\ 2 \quad 3 \quad 1 \end{array} \rightarrow \begin{array}{l} \frac{1}{6} + \frac{1}{2} = \frac{7}{6} \rightarrow \frac{6}{7} \Omega \\ \frac{6}{7} + 3 = \frac{6+21}{7} = \frac{27}{7} \Omega \end{array} \left. \begin{array}{l} \frac{7}{20} + \frac{1}{3} = \frac{21+20}{60} \\ = \frac{41}{60} \end{array} \right\} = 6.463 \Omega \quad \boxed{= 1.463 \Omega}$$

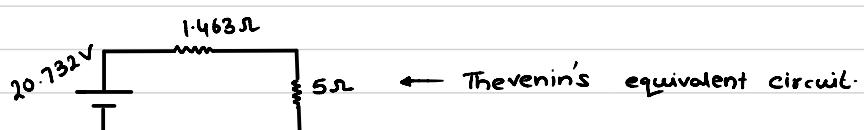
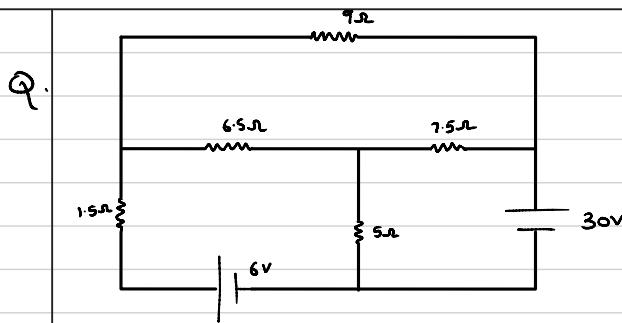
$$i = \frac{v}{R} \rightarrow \frac{20.732}{6.463} = 3.207 \text{ A}$$



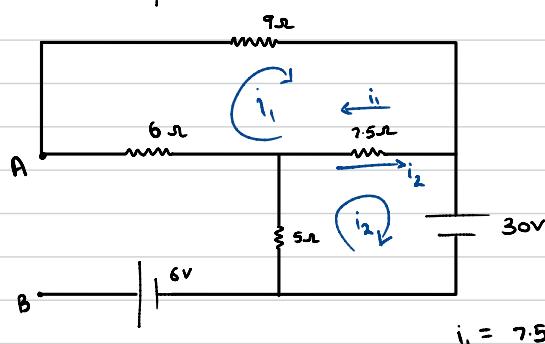- Calculate V_{th}
- Calculate R_{th}
- Draw Thevenin's circuit.



Applying KVL

$$6(i_1) + 7.5(i_1 - i_2) + 9i_1 = 0 \\ 22.5i_1 = 7.5i_2 \quad \text{--- (i)}$$

$$-30 - 5i_2 - 7.5(i_2 - i_1) = 0 \\ 7.5i_1 - 12.5i_2 = 30$$

$$i_1 = \frac{7.5i_2}{22.5} \rightarrow 7.5\left(\frac{7.5i_2}{22.5}\right) - 12.5i_2 = 30$$

$$i_1 = -1A$$

$$i_2 = -3A$$

$$V_A + 6i_1 + 5i_2 + 6 = V_B$$

$$56.25i_2 - 281.25i_1 = 675$$

$$-225i_2 = 675$$

$$i_2 = -\frac{27}{9} = -3A$$


$$i_1 = \frac{-7.5 \times -3}{22.5} = -1A$$

$$V_A - V_B = -6i_1 - 5i_2 - 6$$

$$V_{th} = -6(-1) - 5(-3) - 6 \\ = 6 + 15 - 6$$

$$V_{th} = 15V$$

Check Soln.

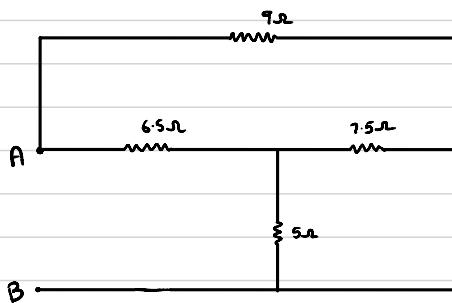


$$\frac{1}{5} + \frac{1}{7.5} = \frac{1+2.5}{37.5} = \frac{3.5}{37.5} = \frac{1}{10.5} = 0.0909\Omega$$

$$\left[\frac{9}{6.5 - 3} \right] \Rightarrow \left[\frac{9}{3.5} \right]$$

$$\Rightarrow \frac{1}{9} + \frac{1}{9.5} = \frac{1+1}{85.5} = \frac{2}{85.5} = \frac{1}{42.75} = 0.0232\Omega$$

Hence, thevenin's circuit:

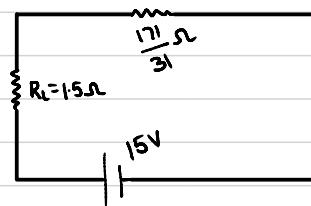


$$4.622 + 1.5$$

$$= 6.122$$

$$V = IR$$


$$i = \frac{15}{6.122} = 2.45A$$

Q.

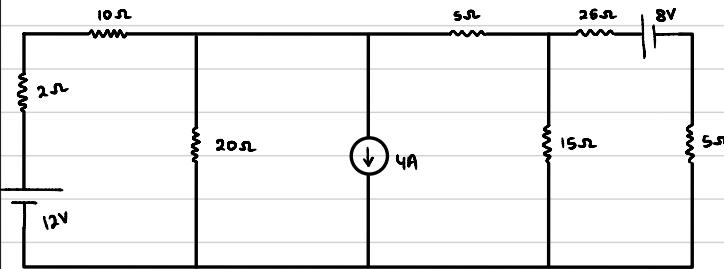

Calculate current through 20Ω resistor using Thevenin's theorem.

Ans.

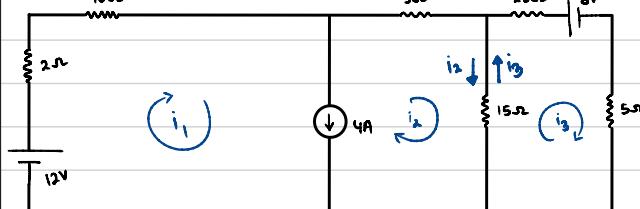

$$i_1 - i_2 = 4A \quad \text{--- (1)}$$

Now applying KVL to supermesh:

$$12 - 2i_1 - 10i_2 - 5i_2 - 15(i_2 - i_3) = 0$$

$$\rightarrow 12 - 12i_1 - 20i_2 + 15i_3 = 0$$

$$\rightarrow 12i_1 + 20i_2 - 15i_3 = 12 \quad \text{--- (2)}$$

Applying KVL in mesh-3:

$$-25i_3 - 8 - 5i_3 - 15(i_3 - i_2) = 0$$

$$15i_2 - 45i_3 = 8 \quad \text{--- (3)}$$

$$\begin{bmatrix} 1 & -1 & 0 \\ 12 & 20 & -15 \\ 0 & 15 & -45 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 12 \\ 8 \end{bmatrix}, \Delta = 1(20x-45 - 15x-15) + 1(12x-45) \\ = -900 + 225 - 540 \\ = -675 - 540$$

$$\Delta = -1215$$


$$\Delta_1 = \begin{bmatrix} 4 & -1 & 0 \\ 12 & 20 & -15 \\ 8 & 15 & -45 \end{bmatrix} = 4(20x-45 - 15x-15) + 1(12x-45 - 8x-15) \\ = 4(-900 + 225) + (-540 + 120) \\ = -4(675) - 420 \\ = -2700 - 420$$

$$\Delta_1 = -3120$$


Using Cramer's rule:

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{-3120}{-1215} = 2.568 A$$
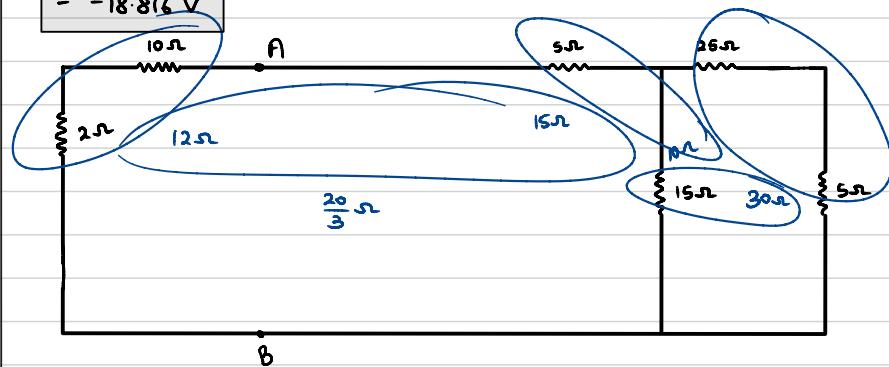
$$\begin{aligned}
 V_{th} &= V_{AB} \\
 &= 12 - 2i_1 - 10i_1 \\
 &= 12 - 12(2.568) \\
 &= 12 - 30.816 \\
 &= -18.816 \text{ V}
 \end{aligned}$$



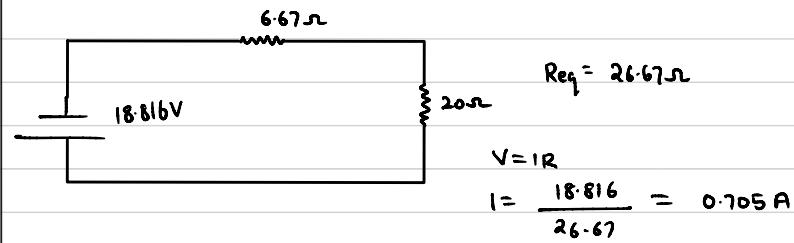
$$R_{th} = \frac{20}{3} \Omega = 6.66 \Omega$$



$$\begin{aligned}
 \therefore \text{Power} &= i^2 R \\
 &= (0.705)^2 (20) \\
 &= 0.497 \times 20 \\
 &= 9.94 \text{ W}
 \end{aligned}$$

Norton's Theorem

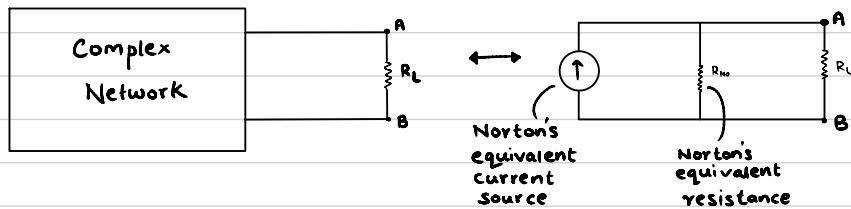


Calculation of Norton's eq. current:

- Short the branch resistance through which current is to be calculated.
- Obtain the Norton's equivalent current from resultant circuit using any method.

Calculation of Norton's Resistance

- Remove R_L
- Replace voltage source by internal resistance / short-circuit if ideal.
Replace current source by internal resistance / open-circuit if ideal.
- Draw Norton's equivalent circuit along with R_L at load terminal.
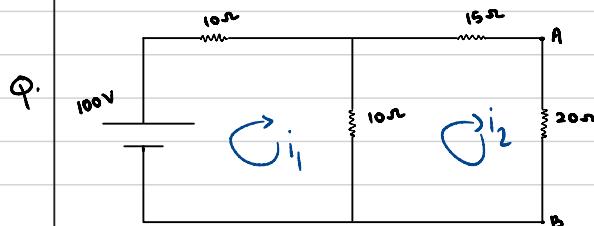
$$\text{Calculate } I_L = I_N \cdot \frac{R_N}{R_L + R_N}$$



Find current through 20 ohm resistor.

Ans:

$$\frac{1}{10} + \frac{1}{15} = \frac{10+15}{100} = \frac{25}{100} \Rightarrow 5\Omega$$

$$R_{eq} = 5 + 15 = 20\Omega$$

$$V = 100V$$

$$100 - 10i_1 - 10(i_1 - i_2) = 0 \quad -15i_2 - 10i_2 + 10i_1 = 0$$

$$-20i_1 + 10i_2 = -100 \quad 10i_1 = 25i_2$$


$$2i_1 - i_2 = 10 \quad 2i_1 = 5i_2$$

$$2i_1 - \frac{2}{5}i_1 = 10 \quad i_2 = \frac{2}{5}i_1$$


$$8i_1 = 50 \quad \frac{\frac{2}{5} \times \frac{50}{8}}{4} \rightarrow 2.5A$$

$$i = 2.5 \times \frac{20}{40} = 1.25A$$

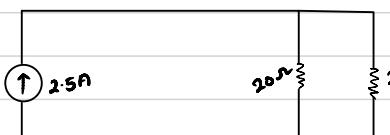Current flowing through 20 ohm resistor = 1.25A




Q.

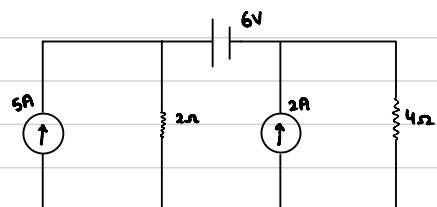

Find current through 4Ω resistor.

Ans:

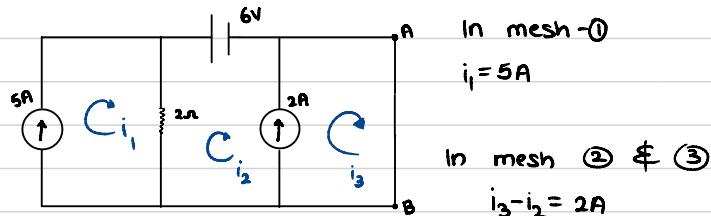

In mesh -①

$$i_1 = 5A$$

In mesh ② & ③

$$i_3 - i_2 = 2A$$

By applying KVL to mesh 2 & 3:

$$-6 - 2(i_2 - i_1) = 0$$

$$-6 - 2i_2 + 2i_1 = 0$$


$$i_1 - i_2 = 3$$

$$5 - 3 = i_2$$


$$i_2 = 2A$$

$$i_3 = 2 + 2$$

$$i_3 = 4A$$

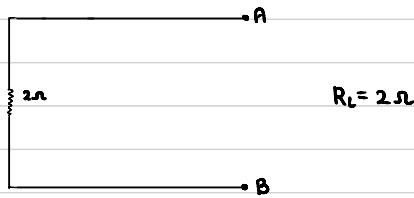

$$R_L = 2\Omega$$

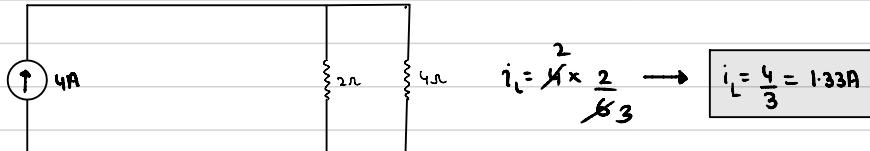


$$i_L = \frac{2}{4+2} \times 2 \rightarrow i_L = \frac{4}{6} = 1.33A$$

Hence current flowing through 4Ω resistor = 1.33A


Max Power Transfer Theorem

$R_{eq} = R_L$ for max. power transfer.

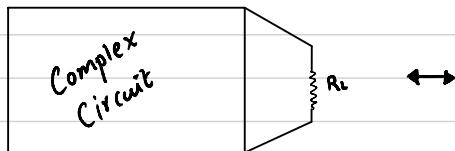


For P_{max} : $R_L = R_{eq} = R_{th}$
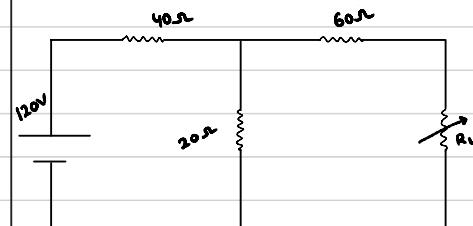
$$P_{max} = \frac{(V_{th})^2}{4(R_{th})} W$$



Find R_L for maximum power transfer.

Ans:

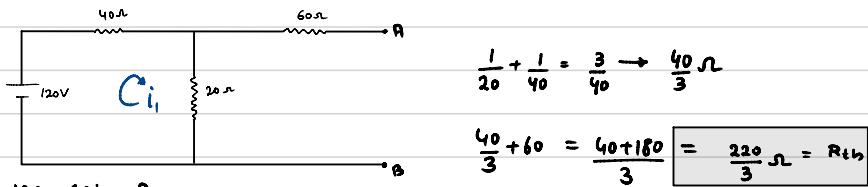

$$\frac{1}{20} + \frac{1}{40} = \frac{3}{40} \rightarrow \frac{40}{3}\Omega$$

$$\frac{40}{3} + 60 = \frac{40+180}{3} = \frac{220}{3}\Omega = R_{th}$$

$$120 - 60i_1 = 0$$


$$i_1 = 2A$$

$$\therefore V = iR \rightarrow V = 2(20) \\ = 40V$$

$$\underline{V = 40V}$$



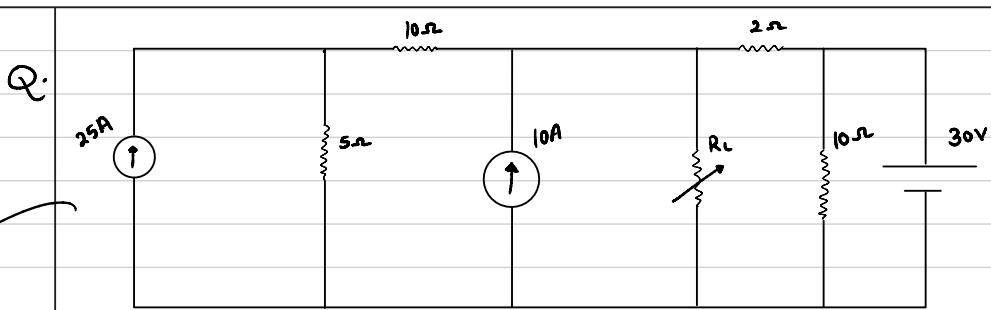
$$\text{Hence Power} = \frac{V^2}{4R} = \frac{\frac{40 \times 40}{4}}{\frac{1}{3} \times \frac{220}{3}} = \frac{120}{22} = 5.45W$$



Determine max. power that can be delivered.


Ans:

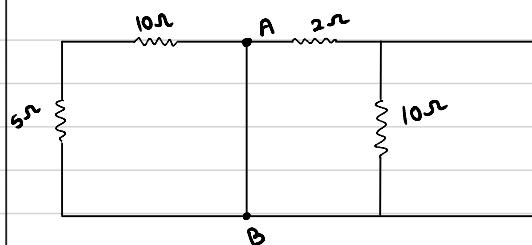

$$10+5=15\Omega$$

$$\frac{1}{15} + \frac{1}{2} = \frac{2+15}{30} \rightarrow \frac{30}{17} \Omega = 1.764 \Omega$$

Converting 25A || 5Ω current source into voltage source:

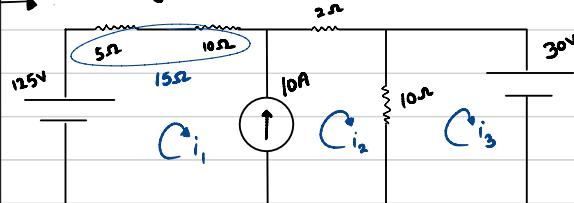

$$i_2 - i_1 = 10 \rightarrow i_2 - 10 = i_1$$

$$125 - 15i_1 - 2i_2 - 10(i_2 - i_3) = 0$$

$$125 - 15i_1 - 12i_2 + 10i_3 = 0$$

$$15i_1 + 12i_2 - 10i_3 = 125 \quad (1)$$

$$15(i_2 - 10) + 12i_2 - 10(i_2 - 3) = 125$$

$$15i_2 - 150 + 12i_2 - 10i_2 + 30 = 125$$

$$17i_2 = 245$$

$$i_2 = 14.41A$$

$$\therefore V = iR = 14.41(2) \\ = 28.82V + 30V$$

$$V_{th} = 58.82V$$

$$-30 - 10(i_3 - i_2) = 0$$

$$-30 - 10i_3 + 10i_2 = 0$$

$$10i_2 - 10i_3 = 30$$

$$i_2 - i_3 = 3 \quad (2)$$

$$i_2 - 3 = i_3$$

$$P = \frac{V^2}{4R} = \frac{(58.82)^2}{4 \times 1.764} = \frac{3459.79}{7.056}$$

$$P = 490.33W$$