

Solution TT1\_EEE

KVL in mesh ①

$$12 - 2I_1 - 10(I_1 - I_2) - I_1 + I_3 = 0$$

$$12 - 2I_1 - 10I_1 + 10I_2 - I_1 + I_3 = 0$$

$$\boxed{-13I_1 + 10I_2 + I_3 = -12} \quad \textcircled{1}$$

KVL to mesh 2

$$-10 - 2I_2 - 3(I_2 - I_3) - 10(I_2 - I_1) = 0$$

$$-10 - 2I_2 - 3I_2 + 3I_3 - 10I_2 + 10I_1 = 0$$

$$\boxed{10I_1 - 15I_2 + 3I_3 = 10} \quad \textcircled{2}$$

KVL to mesh 3

$$-3(I_3 - I_2) - 4I_3 + 24 - I_3 + I_1 = 0$$

$$-3I_3 + 3I_2 - 4I_3 + 24 - I_3 + I_1 = 0$$

$$I_1 + 3I_2 + 2I_3$$


$$\boxed{I_1 + 3I_2 - 8I_3 = -24} \quad \textcircled{3}$$

On solving ①, ② & ③ we get

$$I_3 = 4.1A$$

$$I_{4\Omega} = 4.1A (\leftarrow)$$

Q-16

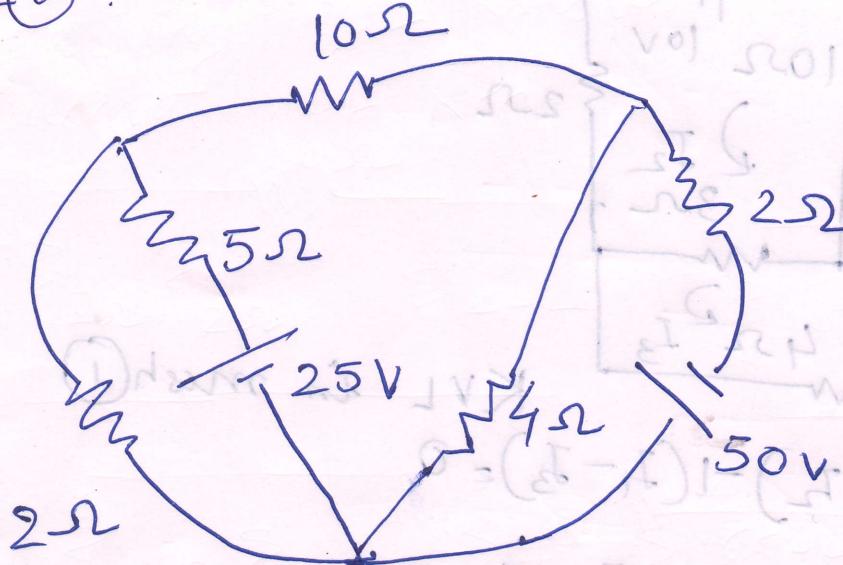

\* node Voltage at node 1

$$\frac{v_1 - 0}{2} + \frac{v_1 - v_2}{10} + \frac{v_1 - 25}{5} = 0 \Rightarrow 5v_1 + v_1 - v_2 + 2v_1 - 50 = 0.$$

$$8v_1 - v_2 = 50$$

node Voltage at node 2

$$\frac{v_2 + 50}{2} + \frac{v_2 - 0}{4} + \frac{v_2 - v_1}{10} = 0$$

$$10v_2 + 500 + 5v_2 + 2v_2 - 2v_1 = 0$$

$$-2v_1 + 17v_2 + 500 = 0$$

$$2v_1 - 17v_2 - 500 = 0$$

$$2v_1 - 17v_2 = -500$$

$$v_2 = -29.104V$$

$$v_1 = 2.612V$$



Current in  $10\Omega$  Resistor is

$$I = \frac{v_A - v_B}{10} = \frac{2.612 - (-29.104)}{10} = 3.1716A$$


$$\text{power dissipated} = I^2 R = (3.172)^2 \times 10$$

$$= 100.6W$$

## Calculation of $R_N$

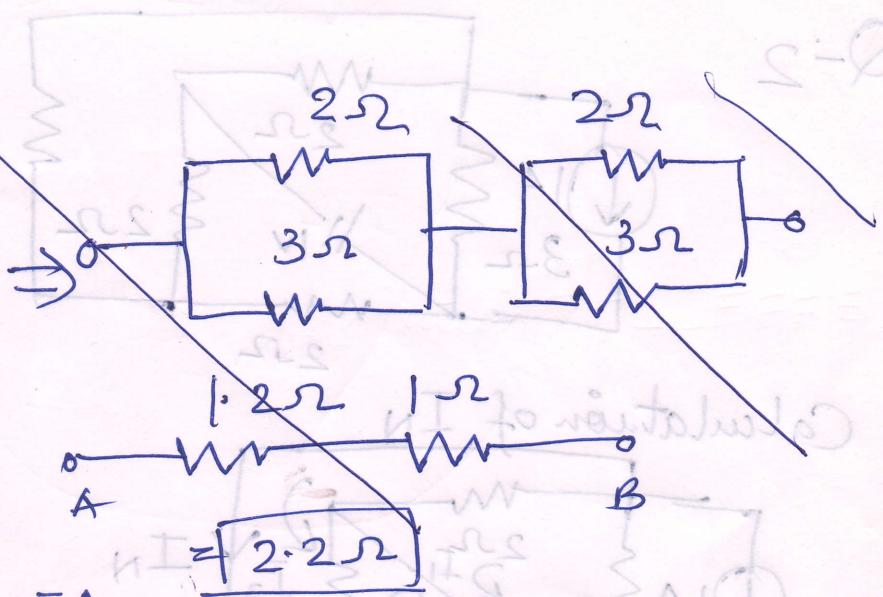
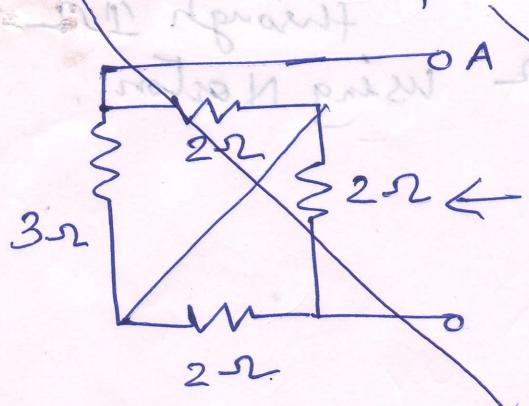


Q-2 (a)

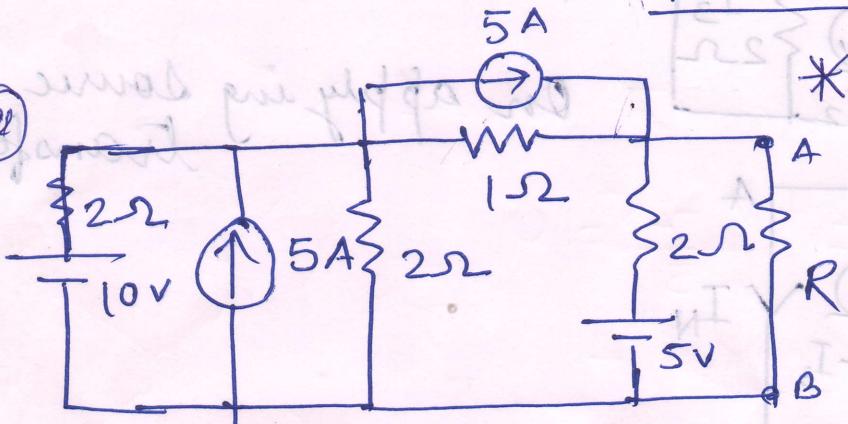



\* considering for 1Ω Resistor

## Calculation of $R_{th}$ .

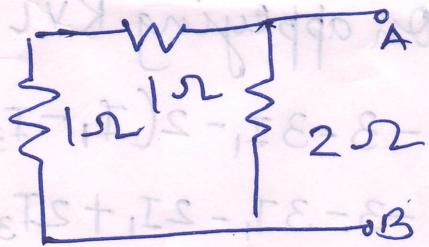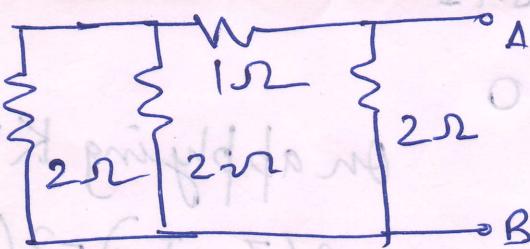


$$0 = (I_f - I_s) \cdot (1\Omega - 2\Omega)$$

$$0 = I_s + I_f - I_s - I_f$$

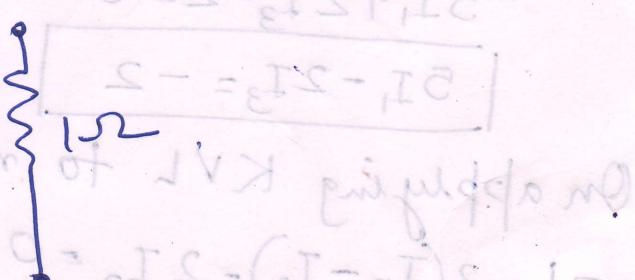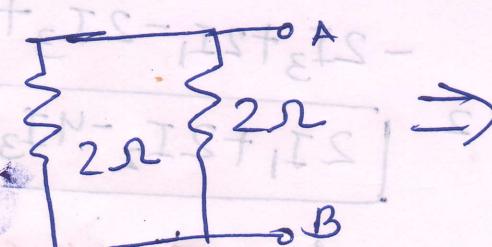






$$R_{th} = R_{AB} = 1\Omega$$

## Calculation of $V_{th}$

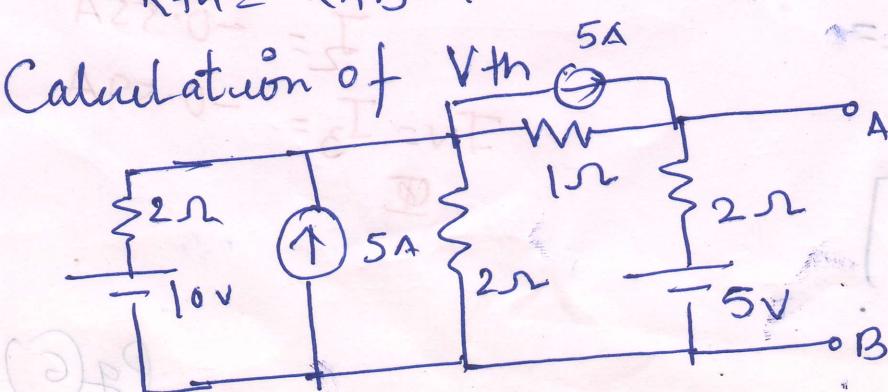

Pg(3)

By source transformation

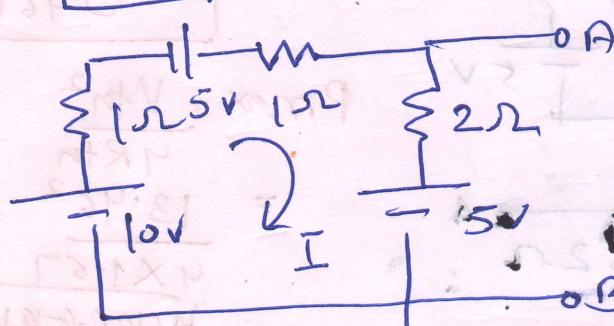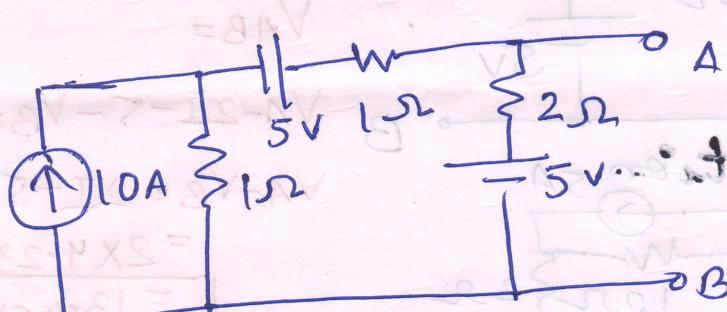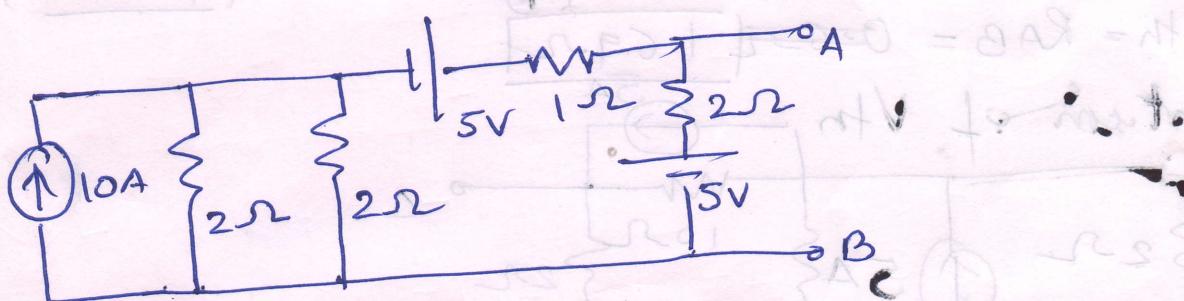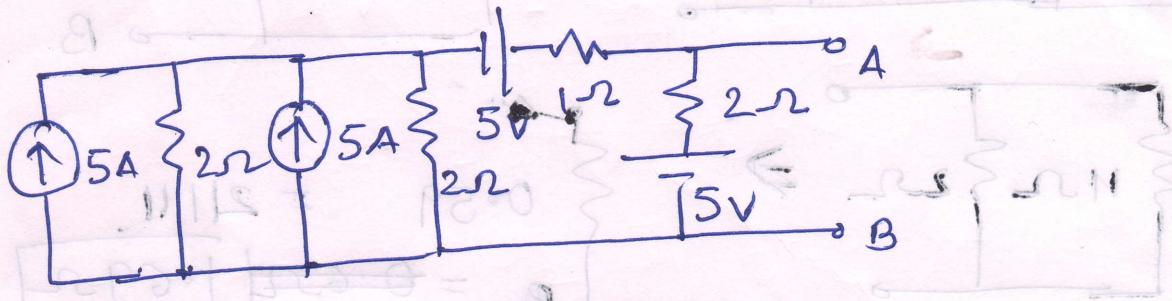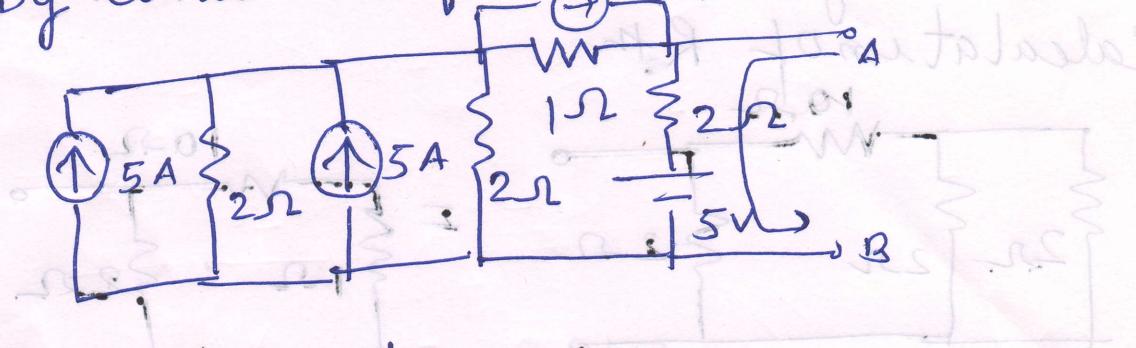

maximum power delivered

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{10 \times 10}{4 \times 1}$$

$$\boxed{25W}$$

$$5 - I - 2I - 5 + 10 - I = 0$$

$$-4I + 10 = 0$$




$$I = \frac{10}{4} = 5/2 = 2.5A.$$

$$V_A - 2I - 5 - V_B = 0$$

$$V_A - 2 \times 2.5 - 5 - V_B = 0$$

$$V_A - V_B = 10V$$

Calculation of  $R_{th}$

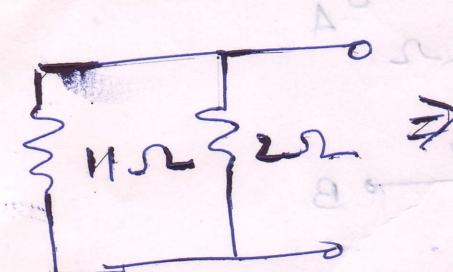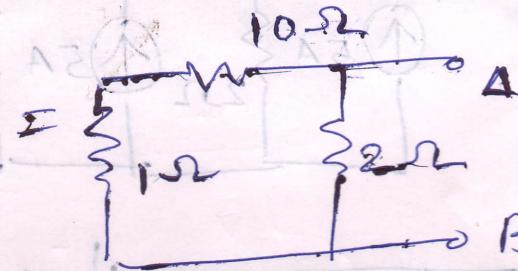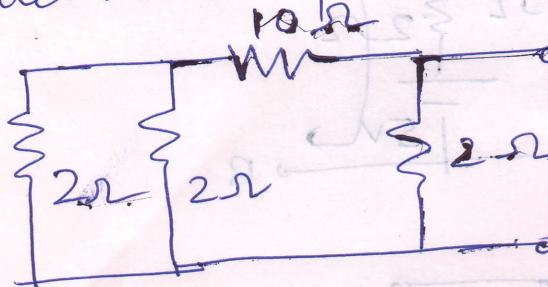


$$0.59 = \frac{211\text{mV}}{1.69\Omega}$$

$$= 0.659 \text{ mA}$$

$$R_{th} = R_{AB} = \frac{1.69\Omega}{5\text{A}}$$

Calculation of  $V_{th}$

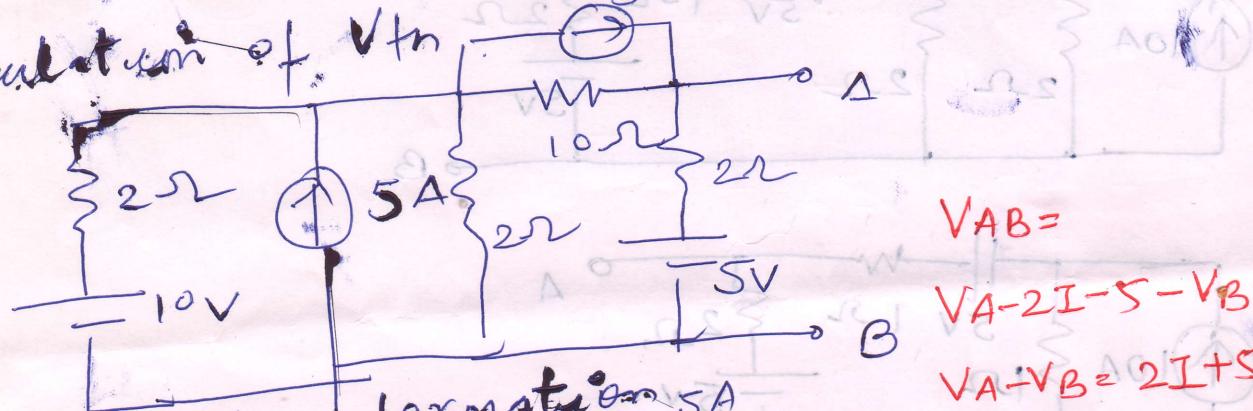

$$V_{AB} =$$


$$V_A - 2I - 5 - V_B = 0$$

$$V_A - V_B = 2I + 5$$

$$= 2 \times 4.23 + 5$$

$$= 13.46 \text{ V}$$



By Source transformation

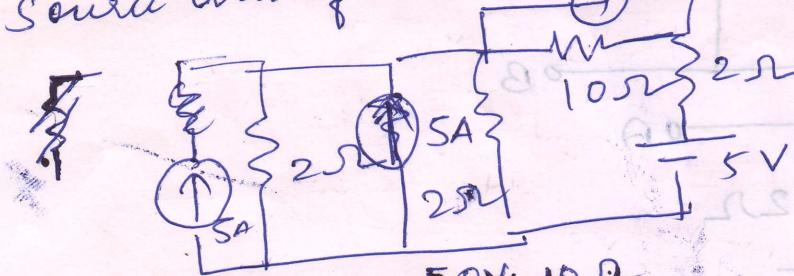

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

$$= \frac{13.46^2}{4 \times 1.67}$$

$$= 26.8 \text{ W}$$

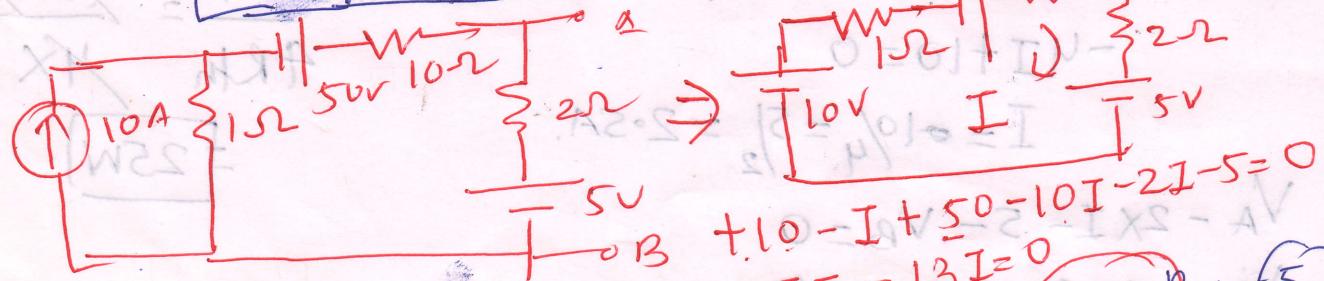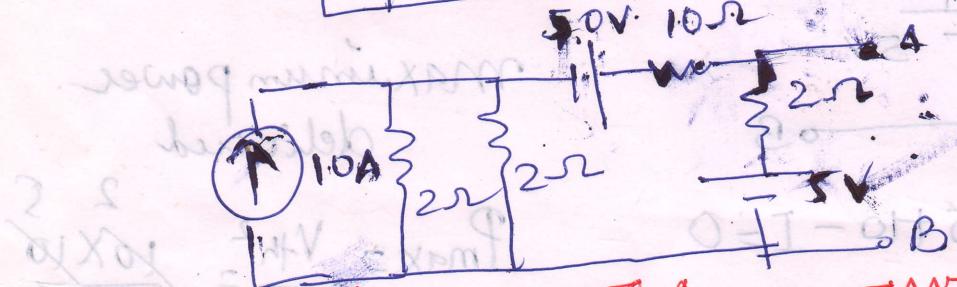

$$+10 - I + \frac{50}{10} - 10I - 2I - 5 = 0$$


$$55 - 13I = 0$$

$$I = 55/13$$

$$= 4.23 \text{ A}$$


Ans

Q-2

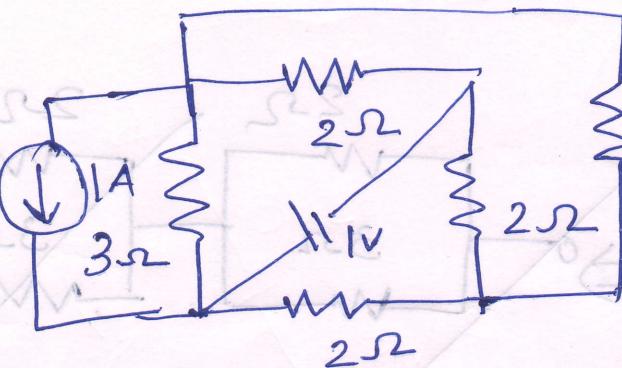

Current flowing through  $I_{12}$  using Norton.

Calculation of  $I_N$

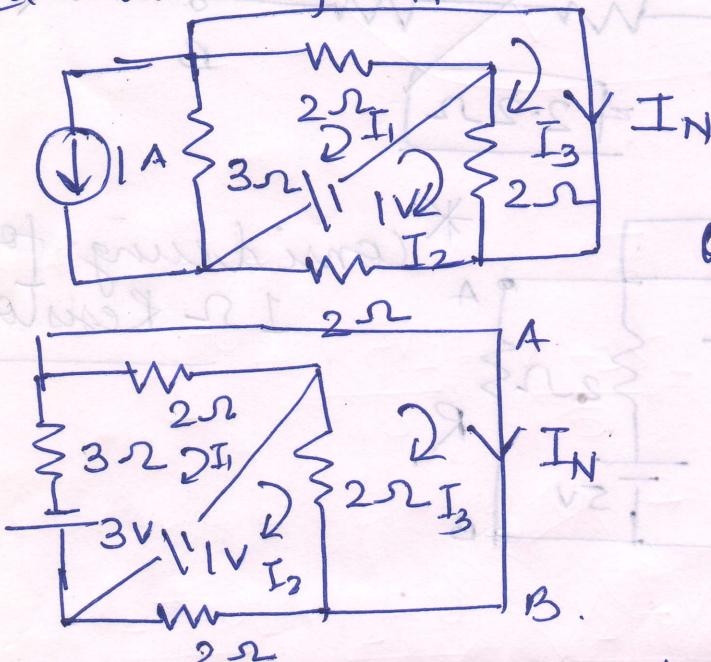

On applying Source transformation

On applying KVL to mesh 1

$$-3 - 3I_1 - 2(I_1 - I_3) + 1 = 0$$

$$-3 - 3I_1 - 2I_1 + 2I_3 + 1 = 0$$

$$-5I_1 + 2I_3 - 2 = 0$$

$$\boxed{5I_1 - 2I_3 = -2}$$

On applying KVL to mesh 2

$$-1 - 2(I_2 - I_3) - 2I_2 = 0$$

$$-1 - 2I_2 + 2I_3 - 2I_2 =$$

$$-4I_2 + 2I_3 = 1 = 0$$

$$\boxed{4I_2 - 2I_3 = -1}$$

On applying KVL to mesh 3

$$-2(I_3 - I_2) - 2(I_3 - I_2) = 0$$

$$-2I_3 + 2I_2 - 2I_3 + 2I_2 = 0$$

$$\boxed{2I_1 + 2I_2 - 4I_3 = 0}$$



On solving  $I_1 = -0.64A$

$$I_2 = -0.55A$$


$$I_N = I_3 = -0.59A$$

Q

Calculation of RN

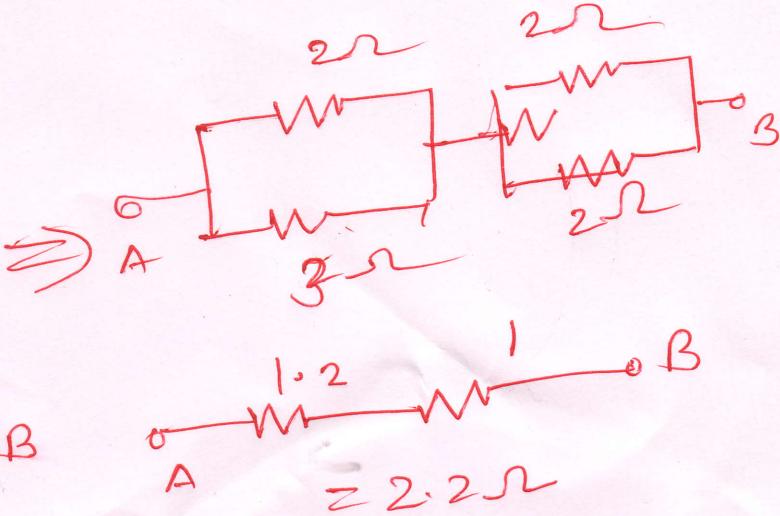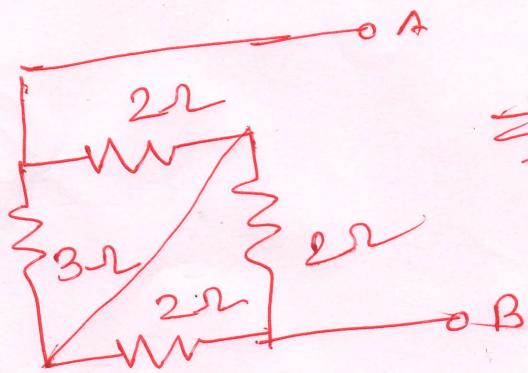

equivalent ckt-

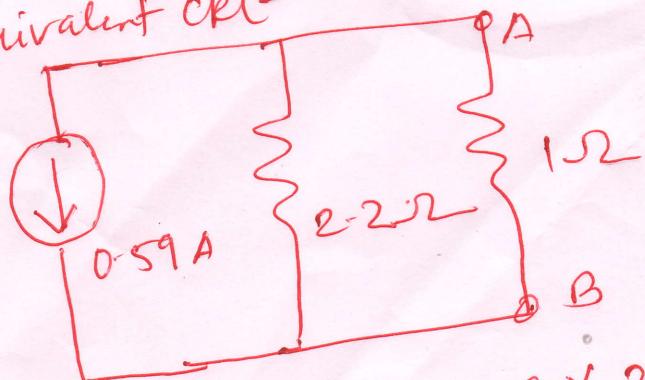

$$I_L = 0.59 \times \frac{2.2}{1+2.2} = 0.41A$$